 


FPGA Fundamentals


What is an FPGA?

- Field Programmable Gate Array.
- Contains:
 - Logic gates
 - Registers
 - Configurable Routing
 - Memory (RAMs, ROMs)
 - PLLs
 - Arithmetic & DSP
 - Hard IP Blocks
- Fully programmable.

Configurable Logic Block (CLB)



Simplified FPGA Architecture

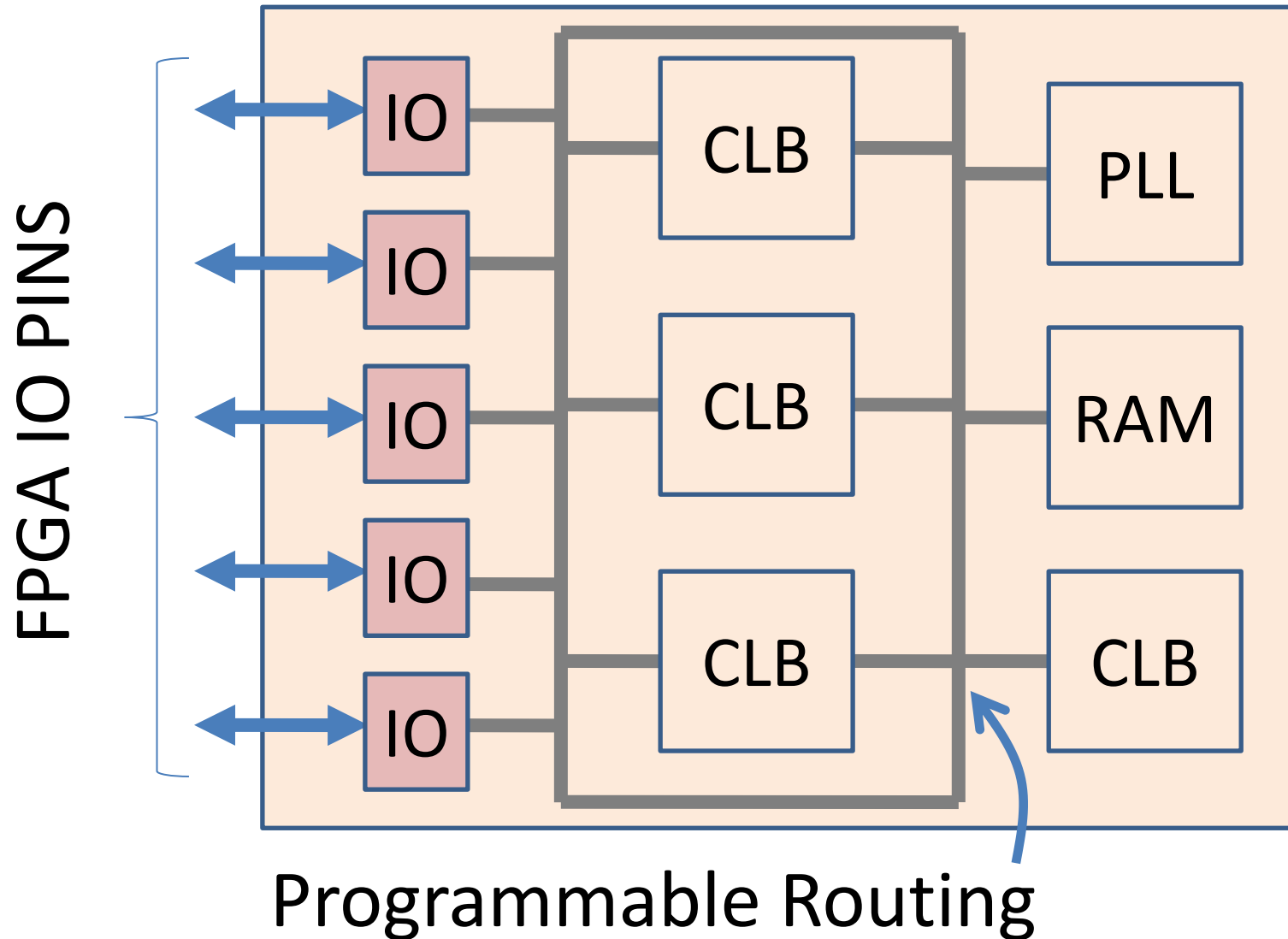

Why Use An FPGA?

- Used for implementing Digital Systems.
- Extremely Flexible.
 - No limit to timers, counters, peripherals etc.
 - Does not have a fixed hardware structure.
 - Change whole design without changing layout.
- Very fast.
- Parallel processing (Doesn't execute sequentially).
- Large bandwidth (Data width configurable).
- Intensive data processing (Video, DSP, FFT etc)

When Not To Use An FPGA


- In cost sensitive applications.
- Carrying out infrequent tasks that are sequential in nature (eg : search / sort algorithms).
- When speed and latency are not that important.

FPGA Programming

- Hardware Descriptive Languages (HDL)
- C/C++ using HLS (High Level Synthesis)
- Popular HDL Languages :

VHDL	Verilog
Strongly Typed	Weakly Typed
Deterministic	Only Deterministic If you Follow Rules Carefully.
Verbose	Concise
Non C Like Syntax	More C Like Syntax

Behavioural Vs RTL

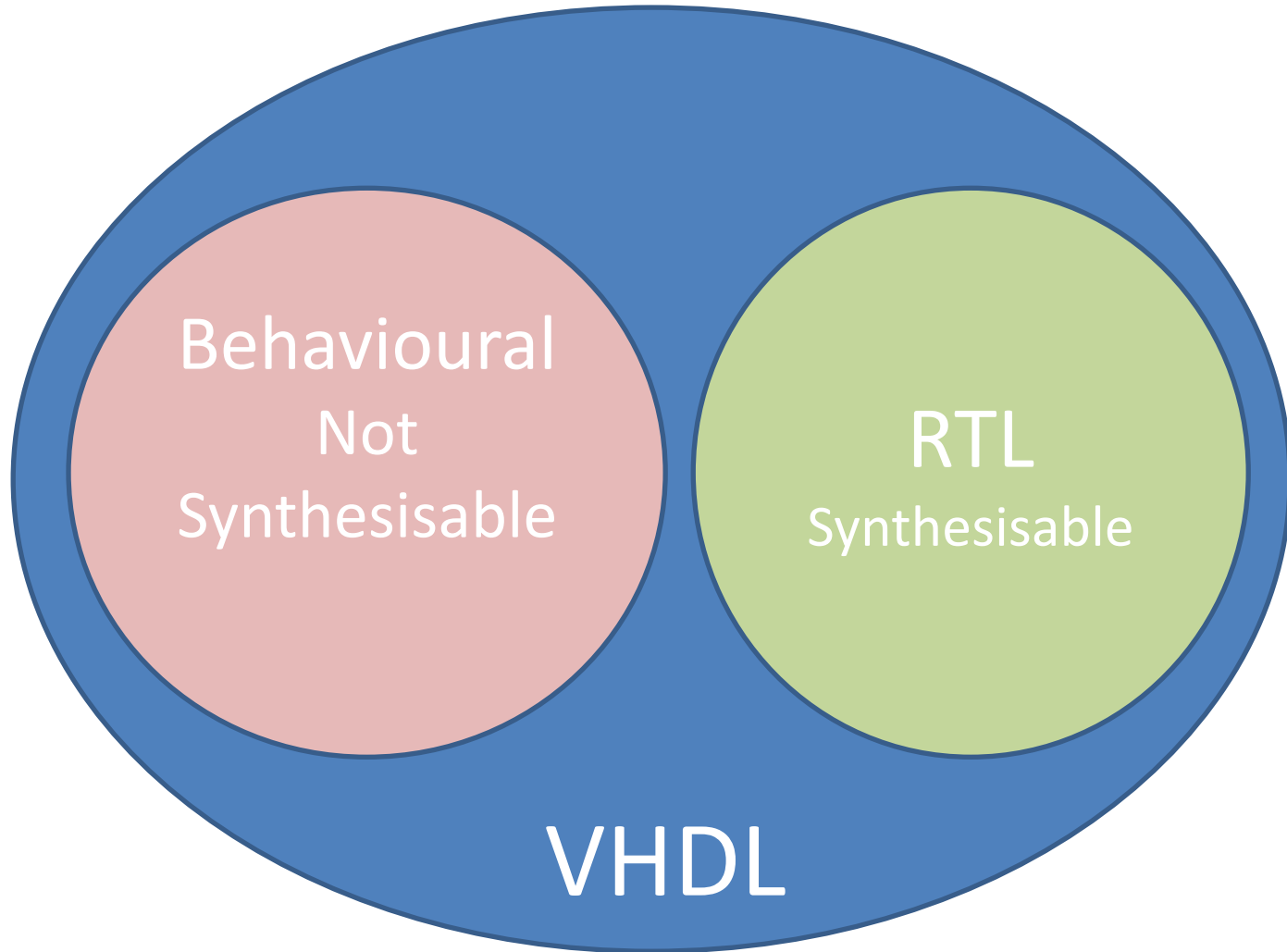

RTL (Register Transfer Level)

- Can be simulated, synthesised & implemented on an FPGA.
- Describes hardware in terms of registers and combinational logic that sits between them.
- Need to have an idea of the digital circuit.
- No explicit delays.
- All timing described in terms of clock edges.
- Used as input to a synthesis tool.

Behavioural


- Can only be simulated. Cannot be synthesised.
- Can have explicit delays,
- Uses an algorithm to describe functionality.
- Describes behaviour at a higher level.
- Used to build a verification model to simulate the behaviour of a system or module.
- Used for simulation purposes for example in writing test benches.

FPGA Design Flow

- Start from the **Design Specification**
- Use VHDL Editor To :
 - Write VHDL (RTL)
 - Write **Test-Bench** (RTL + Behavioural)
- **Simulate** to ensure correct behaviour.
- Write **Timing Constraints**.
- **Synthesis** tool to generate a netlist.
- **Implementation** tool to take netlist and perform placement, routing and optimisation.
- Make sure designs meets **Timing**. If not go back to VHDL code.
- Implementation creates a **binary file** used to configure the FPGA.

FPGA Design Flow

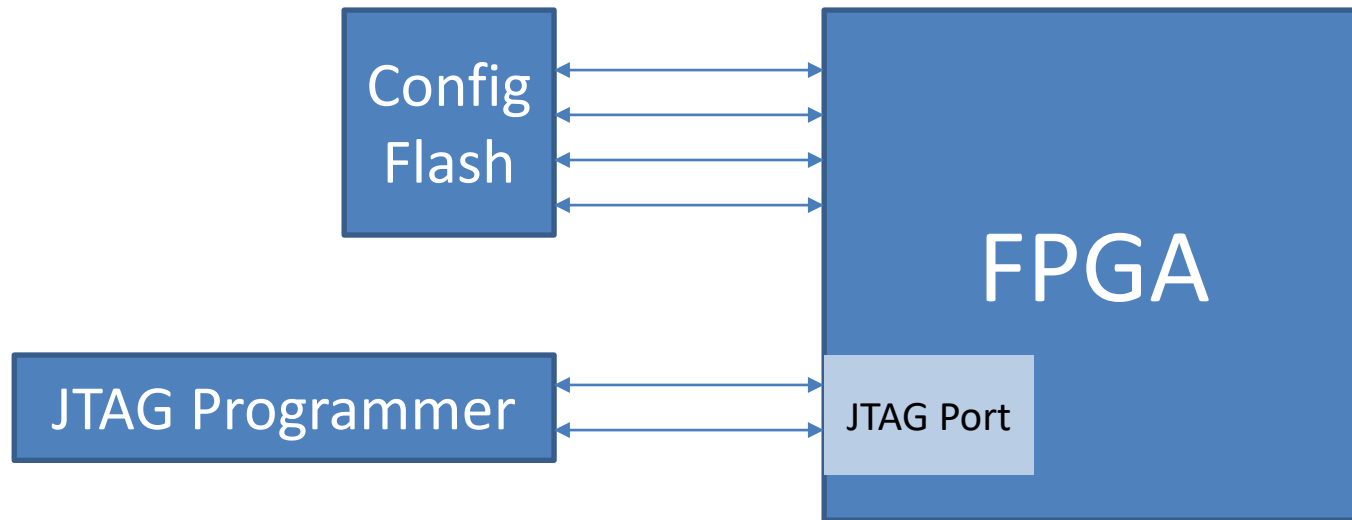- Program binary file into FPGA configuration flash (using JTAG for example)



Chapter Summary

- Configurable Logic Block (CLB)
- FPGA Architecture
- When to use an FPGA?
- What are FPGAs good at?
- When might you not use an FPGA?
- Overview of FPGA programming languages.
- Typical FPGA design flow.

Signals & Data Types I

Some Basics

- VHDL is NOT case sensitive.
 - OBJECT_NAME = object_name
- Reserved words – Keywords.
- Identifiers
 - Used to name objects in VHDL.
 - Cannot be a reserved word.

Signals

Signal Declaration Syntax :

signal signal_name : data_type;

signal signal_name : data_type := initial_value;

Signal Assignment Operator : \leq

Example Signal Assignment:

A \leq B;

Data Types – Std_logic

- Represents the value of a single data bit.
- Package - Std_Logic_1164.
- Can take the following values :
 - '1' or '0' – Logic high or low.
 - 'Z' – Tri-stated.
 - 'H' or 'L' – Weak high or low. (e.g: pull-up)
 - 'W' – Weak unknown.
 - 'U' – Un initialised.
 - 'X' – Unknown or cannot be determined.
 - '-' – Don't care.

Data Types – Std_logic

- Examples:
 - Input or Output of a logic gate.
 - Input or Output of a register / flip-flops.
 - A clock or reset signal.

Declaration :


```
signal A : std_logic;
```

```
signal B : std_logic := '0';
```

Assignments :

```
A <= B;
```

Data Types – Std_logic

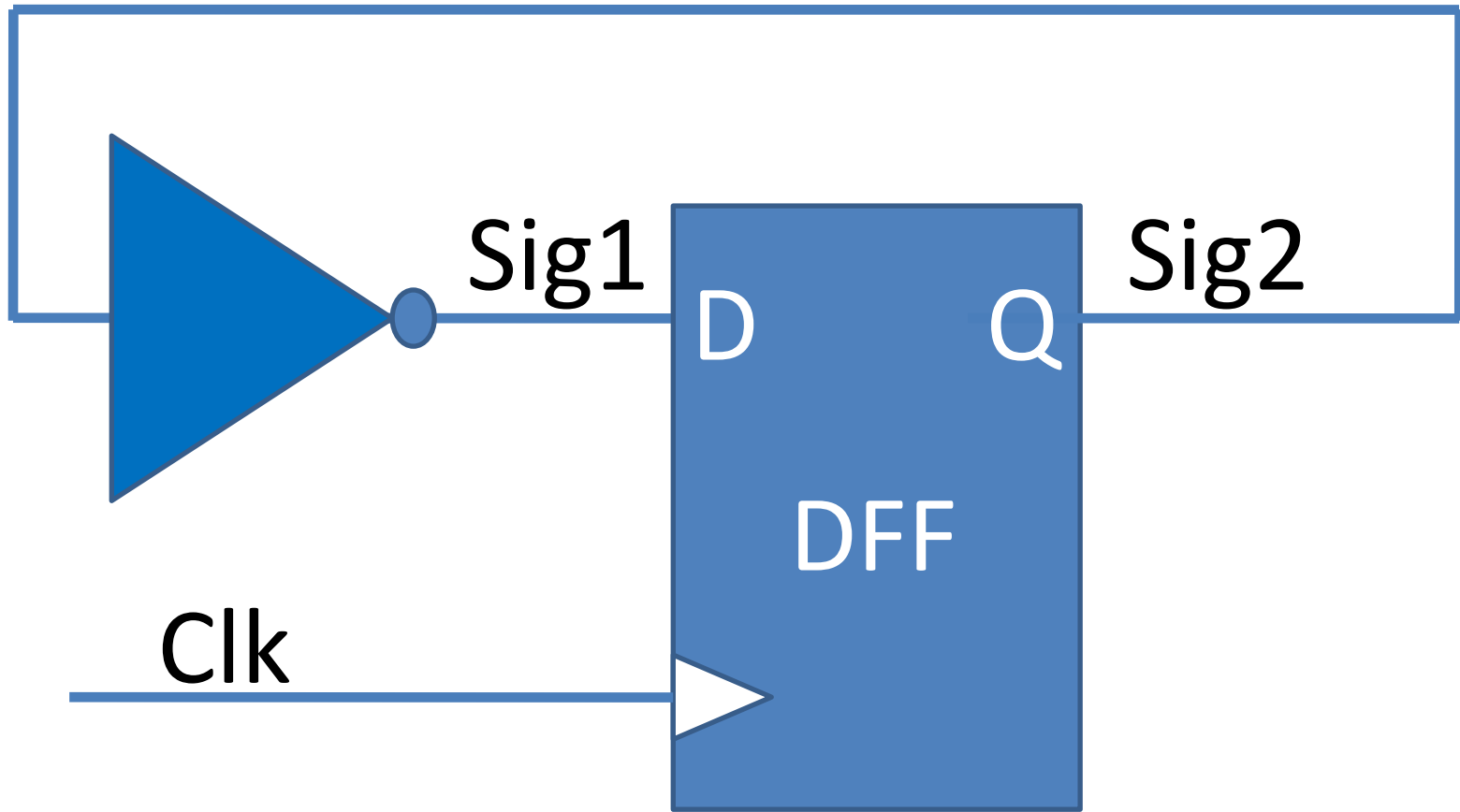

Sig1, Sig2 and Clk are **std_logic** signals used here to connect the logic devices together.

Data Types – Std_logic_vector


- Is an array of **std_logic** signals.
- Similar to an array of bits.
- Package - Std_Logic_1164.
- Examples:
 - Address or Data busses
 - Counter / Timer
 - Register

Data Types – Std_logic_vector

Declaration :

```
signal A : std_logic_vector(7 downto 0);
```
 
```
signal B : std_logic_vector(7 downto 0) := x"A1";
```



Bit 7	Bit 6	Bit 5	Bit 4	Bit 3	Bit 2	Bit 1	Bit 0
1	0	1	0	0	0	0	1

Data Types – Std_logic_vector

```
signal A : std_logic_vector(7 downto 0) ;
```

```
signal B : std_logic_vector(7 downto 0);
```

```
signal C : std_logic;
```

Assignments

```
A <= B;
```

```
A(7 downto 6) <= B(3 downto 2);
```

```
A(4) <= B(0);
```

```
C <= A(6);
```

Array Attributes

```
signal A : std_logic_vector(7 downto 0) ;
```

Array Attributes	Returned Value
A'left	7
A'right	0
A'length	8
A'range	7 downto 0

Array Attributes

```
signal A : std_logic_vector(7 downto 0) ;  
signal F : std_logic;
```

Using Attributes	Without Using Attributes
signal B : std_logic_vector(A'range) ;	signal B : std_logic_vector(7 downto 0) ;
signal C : std_logic_vector(A'left - 1 downto 0);	signal C : std_logic_vector(6 downto 0);
F <= A(A'right);	F <= A(0);
F <= A(A'left-2);	F <= A(5);

Data Types – Unsigned & Signed

- Represents a signed or unsigned value.
- A vector of bits similar to `std_logic_vector`.
- Takes the same values as the `std_logic` type.
- Package – **`numeric_std`**.
- Examples :
 - Counters.
 - Used for arithmetic operations.

Data Types – Unsigned & Signed

Declaration :

```
signal A : unsigned(7 downto 0);
```

```
signal B : signed(7 downto 0) := x"A1";
```

- Assignments:

- Must be same type (i.e both unsigned or both signed).
- Must be the same size.

Assignments :

$$Y \leq X;$$

Data Types – integer

- Represents an integer value.
- Built into VHDL so no Package needed.
- At least covers the range : -2^{31} to $+2^{31}-1$
- Examples :
 - Counters
 - Indices

Data Types – integer

Declaration :

`signal A : integer;`
`signal B : integer := 2;`
`signal C : integer range 0 to 255;`
`signal D : integer range -128 to 127 := 35;`

} Not recommended!

Assignments :

`Y <= X;`

Data Types – Boolean

- Represents a value that can be true or false.
- Built into VHDL language.

Declaration :

```
signal A : boolean;
```

```
signal B : boolean := true;
```

Enumerated Types

Allowed Values : Red, Amber and Green

VHDL Type Declaration

```
type TrafficLight is (red, amber, green);
```

VHDL Signal Declaration

```
signal my_signal : TrafficLight;
```

Signal Assignment

```
my_signal <= red;
```

Enumerated Types - Encoding

00 = Red

01 = Amber

10 = Green

11 = Unused

Enumerated Types

- VHDL supports enumerated types.
- Allow us to create our own data types.
- Defined by listing all possible values.
- Example :
 - Std_logic
 - Used for state machine state encoding.

Enumerated Types

Declare New Enumerated Type

```
type SMType is (IDLE, DO_WORK, ASSERT_DONE);
```

Declare State Machine Signal

```
signal SMState : SMType;
```

Example Assignments

```
SMState <= IDLE;
```

```
SMState <= DO_WORK;
```

Enumerated Types

- SMState signal will be implemented using 2 bits on the FPGA :

00 = IDLE

01 = DO_WORK

10 = ASSERT_DONE

11 = Unused

Arrays

- Array = Collection of signals of the same type.
- `std_logic_vector` is an array of `std_logic` elements.
- We can define our own array types.
`type myArrayType is array (0 to 3) of integer;`

Arrays

```
signal myArray : myArrayType ;
```

```
myArray(0) <= 13;
```

```
myArray(1) <= 14
```

```
myArray(2) <= 15;
```

```
myArray(3) <= 16
```

Index 0	Index 1	Index 2	Index 3
13	14	15	16

Unconstrained Array Type

- Unconstrained array type **DOES NOT** specify number of elements.
- Number of elements must be declared when creating the signal!

`type ABC is array (integer range <>) of integer;`

Array range is not defined.

`signal Sig1: ABC(0 to 7);`

`signal Sig2: ABC(1 to 16);`

Array index has an integer type

Summary

- Signals are like wires.
- Used to connect things together.
- Data types specify what values a signal can carry.
- Define our own data types.
- Define our own array types.

Signals & Data Types II

More On Enumerated Types

Defined In Package Standard:

```
type bit is ('0', '1');
```

```
type boolean is (false, true);
```

```
type CHARACTER is (all values in the ascii table!);
```

```
type SEVERITY_LEVEL is (NOTE, WARNING, ERROR, FAILURE);
```

Defined In Package STD_LOGIC_1164:

```
type std_ulogic is ('U', 'X', '0', '1', 'Z', 'W', 'L', 'H', '-');
```

!!! Note : std_logic is a subtype of std_ulogic !!!

Subtypes

- VHDL subtypes are subsets of the base type.

Examples From Standard Package:

```
subtype NATURAL is INTEGER range 0 to INTEGER'HIGH;
```

```
subtype POSITIVE is INTEGER range 1 to INTEGER'HIGH;
```

Declaring Signals Using Subtypes:

```
signal NaturalSignal : natural;
```

```
signal PositiveSignal : positive;
```

Subtypes

- VHDL subtypes are subsets of the base type.

User Defined Subtypes:

```
subtype uint8_t is INTEGER range 0 to 255;
```

```
subtype MyVector8 is std_logic_vector(7 downto 0);
```

Declaring Signals Using Subtypes:

```
signal RxChar : uint8_t;
```

```
signal DataBus : MyVector8;
```

More On Array Types

Examples of Array Types in the Standard Package:

`type STRING is array (POSITIVE range <>) of CHARACTER;`

`type BOOLEAN_VECTOR is array (NATURAL range <>) of BOOLEAN;`

`type BIT_VECTOR is array (NATURAL range <>) of BIT;`


`type INTEGER_VECTOR is array (NATURAL range <>) of INTEGER;`

Signal Declarations

`signal MyCharArray : string(1 to 10);`

`signal MyBoolArray : boolean_vector(7 downto 0);`

`signal MyBitArray : bit_vector(15 downto 8);`



Using a Natural array index means that the element indices cannot be negative.

Creating Your Own Array Types

User Defined Data Type:

```
type TLightType is (RED, AMBER, GREEN);
```

User Defined Array Type:

```
type TLightArray is array (NATURAL range <>) of TLightType ;
```

Signal Declarations

```
signal MyTrafficLight: TLightArray(1 to 10);
```


Signal Assignments

```
MyTrafficLight(1) <= red;
```

```
MyTrafficLight(10) <= green;
```

Record Type

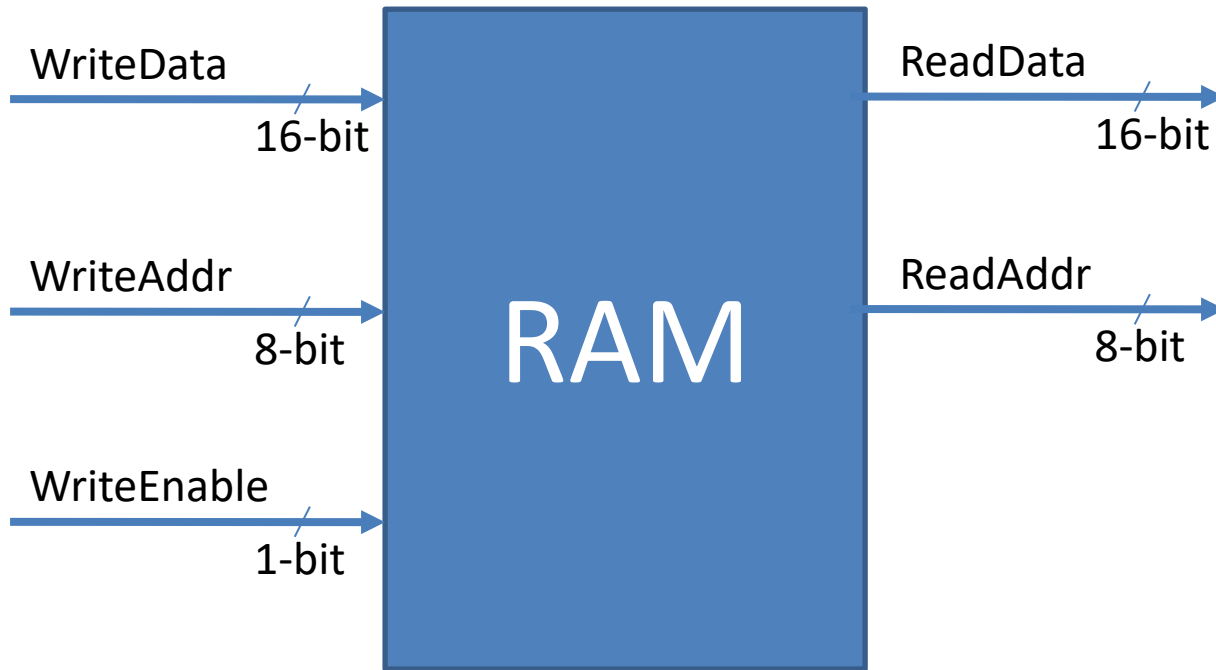- Record Type = A type that is a collection of elements (of any data type).



Record Type

```
signal WriteData      : std_logic_vector(15 downto 0);  
signal ReadData       : std_logic_vector(15 downto 0);  
signal WriteAddr      : std_logic_vector(7  downto 0);  
signal ReadAddr       : std_logic_vector(7  downto 0);  
signal WriteEnable    : std_logic;
```

Records

Step 1 : Create the new record type :

```
type MyRAMType is record
    signal WriteData    : std_logic_vector(15 downto 0);
    signal ReadData     : std_logic_vector(15 downto 0);
    signal WriteAddr     : std_logic_vector(7 downto 0);
    signal ReadAddr     : std_logic_vector(7 downto 0);
    signal WriteEnable   : std_logic;
end record;
```

Records

Step 2 : Declare our new signal

```
signal RAM_IO : MyRAMType;
```

Examples of Signal Assignments

```
RAM_IO.WriteData <= x"8000";
```

```
RAM_IO.WriteAddr <= x"01";
```

```
RAM_IO.WriteEnable <= '1';
```


Summary

- Enumerated types
- Subtypes
- Array types
- Record Types

Constants

Constants

Constant Declarations:

constant name : type := initial_value;

Example Signal Assignment:

MySignal <= MyConstant;

Summary

- Constants must be initialised during declaration.
- Once declared, its value cannot be changed.
- Use constants as much as possible:
 - Makes code more readable.
 - Easier to maintain.

Operators

VHDL Operators

Not	- inversion	+	- addition
And	- and function	-	- subtraction
Nand	- not and function	+	- plus sign
Or	- or function	-	- minus sign
Nor	- not-or function	*	- multiplication
Xor	- exclusive or function	/	- division
Xnor	- exclusive nor function	Mod	- modulo arithmetic
=	- equality	Rem	- remainder
/=	- inequality	**	- exponential
>=	- greater than or equal	Abs	- absolute value
>	- greater than	&	- concatenation
<=	- less than or equal		
<	- less than		
Sll	- shift left logical		
Srl	- shift right logical		
Rot	- rotate left		
Ror	- rotate right		
Sla	- shift left arithmetic		
Sra	- shift right arithmetic		

Boolean Operators

Operator	Operation
Not	Invert
And	And Gate
Nand	Inverted And Gate
Or	Or Gate
Nor	Inverted Or Gate
Xor	Exclusive or Gate
Xnor	Inverted exclusive or gate

Boolean Operators

Libraries:

- Std_Logic_1164

Can Be Used With :

- Bit
- Boolean
- Arrays of the above types.

Boolean Operators

Examples :

C <= A and B; -- All signals std_logic type

Z <= X xor Y; -- All signals Boolean type

if Sig1 = "1101" or Sig2 = true then
-- Code to execute when conditions are true
end if;

Boolean Operators

```
signal P : std_logic_vector(3 downto 0);
```

```
signal Q : std_logic_vector(3 downto 0);
```

```
signal R : std_logic_vector(3 downto 0);
```

```
R <= P or Q;
```

Boolean Operators

```
signal P : std_logic_vector(3 downto 0);
```

```
signal Q : std_logic_vector(3 downto 0);
```

```
signal R : std_logic_vector(3 downto 0);
```

```
R <= P or Q;
```



```
R(0) <= P(0) or Q(0);
```

```
R(1) <= P(1) or Q(1);
```

```
R(2) <= P(2) or Q(2);
```

```
R(3) <= P(3) or Q(3);
```

Comparison Operators

Operator	Operation
=	Equality
/=	Inequality
>=	Greater than or equal
<=	Less than or equal
>	Greater than
<	Less than

Comparison Operators

Notes:

- Used to compare signals.
- Data types of the compared signals must match.
- Comparison operators return a Boolean result.

Libraries :

- Std_logic_1164

Can Be Used With

- Most data types support all 6 operators.
- All types support the = and /= operators

Comparison Operators

Examples :

`Y <= (X > "0011");` -- Y is Boolean, X is a 4-bit vector

`if Sig1 > 128 then` – Sig1 is an integer type
-- Code to execute when condition is true
`end if;`

Shift Operators

Operator	Operation	Notes
SLL	Shift Left Logical	Shifts the array discarding bits that are shifted off one end and fills the other end with '0'.
SRL	Shift Right Logical	

Libraries:

- Std_logic_1164

Can Be Used With:

- std_logic_vector and bit_vectors.

SLL Example

```
signal X : std_logic_vector(3 downto 0) := "1011";
```

```
signal Y : std_logic_vector(3 downto 0);
```

```
Y <= X sll 1;
```

Number of Shifts

Step 1 :



← X

Step 2 :



Step 3 :



Step 4 :



← Y

SRL Example

```
signal X : std_logic_vector(3 downto 0) := "1011";
```

```
signal Y : std_logic_vector(3 downto 0);
```

```
Y <= X srl 2;
```

Number of Shifts

Step 1 :

1	0	1	1
---	---	---	---

 ← X

Step 2 :

?	?	1	0	1	1
---	---	---	---	---	---

Step 3 :

0	0	1	0	1	1
---	---	---	---	---	---

Step 4 :

0	0	1	0
---	---	---	---

 ← Y

Rotate Operators

Operator	Operation	Notes
ROL	Rotate Left	Take elements off one end of the array and shifts them in at the other end.
ROR	Rotate Right	

Libraries:

- Std_logic_1164

Can Be Used With:

- `std_logic_vector` and `bit_vectors`.

ROL Example

```
signal X : std_logic_vector(3 downto 0) := "1011";
```

```
signal Y : std_logic_vector(3 downto 0);
```


```
Y <= X rol 1;
```

Number of Shifts

Step 1 :



Step 2 :

 

Step 3 :



Arithmetic Operators

Operator	Meaning
+	Addition / Positive sign
-	Subtraction / Negative sign
*	Multiplication
/	Division
Mod	Modulo arithmetic
Rem	Remainder after division
**	Exponential
Abs	Absolute value

Arithmetic Operators

Libraries:

- `numeric_std`

Can be used with :

- Unsigned Types
- Signed Types
- Integer Types

Arithmetic Operators

1. $C \leq A + B$; -- All signals are unsigned bit vectors
2. $C \leq A - B$; -- All signals are integers
3. $C \leq 2^{**} 8$; -- All signals are integers
4. $C \leq (C+1) \bmod 16$ -- All signals are integers

Concatenation Operator

Operator	Meaning
&	Concatenation Operator

Libraries:

- Std_logic_1164
- Numeric_std

Can Be Used With:

- std_logic_vector and bit_vectors.
- Signed and unsigned.

Concatenation Operators

Signal A : `std_logic_vector(3 downto 0) := "0011";`

Signal B : `std_logic_vector(3 downto 0) := "1111";`

Signal C : `std_logic_vector(4 downto 0);`

Signal D : `std_logic_vector(7 downto 0);`

`C <= A & '0';` -- C will be "00110"

`C <= '1' & A;` -- C will be "10011"

`D <= A & B;` -- D will be "00111111"

Operator Precedence

Operator
Abs, not, **
Mod, rem, *, /
+, - (signs)
+, - , &
Sll, srl, rol, ror
And, or, nand, nor, xor, xnor

Operator Precedence

VHDL Statement	Evaluated As
$C \leq 2 * 3 + 4;$	$C \leq (2 * 3) + 4;$
$C \leq A \text{ Sll } 2 + 4;$	$C \leq A \text{ Sll } (6);$
$C \leq -A * B;$	$C \leq -(A * B);$

Operator Precedence

Incorrect Statements	Corrected
$M \leq A \text{ and } B \text{ or } C;$	$M \leq (A \text{ and } B) \text{ or } C;$ $M \leq A \text{ and } (B \text{ or } C);$
$M \leq A \text{ nand } B \text{ nand } C;$	$M \leq (A \text{ nand } B) \text{ nand } C;$ $M \leq A \text{ nand } (B \text{ nand } C);$

$(A \text{ and } B) \text{ or } C \neq A \text{ and } (B \text{ or } C)$

$(A \text{ nand } B) \text{ nand } C \neq A \text{ nand } (B \text{ nand } C)$


!! Use brackets as much as possible to avoid confusion !!

Summary


- Boolean operators
- Comparison operators
- Shift operators
- Arithmetic operators
- Concatenation operator

Structure of a VHDL File

VHDL File Structure

 

VHDL File Structure

 


VHDL File




File extension is .vhd


VHDL File Structure

 


VHDL File Structure

 


VHDL File Structure

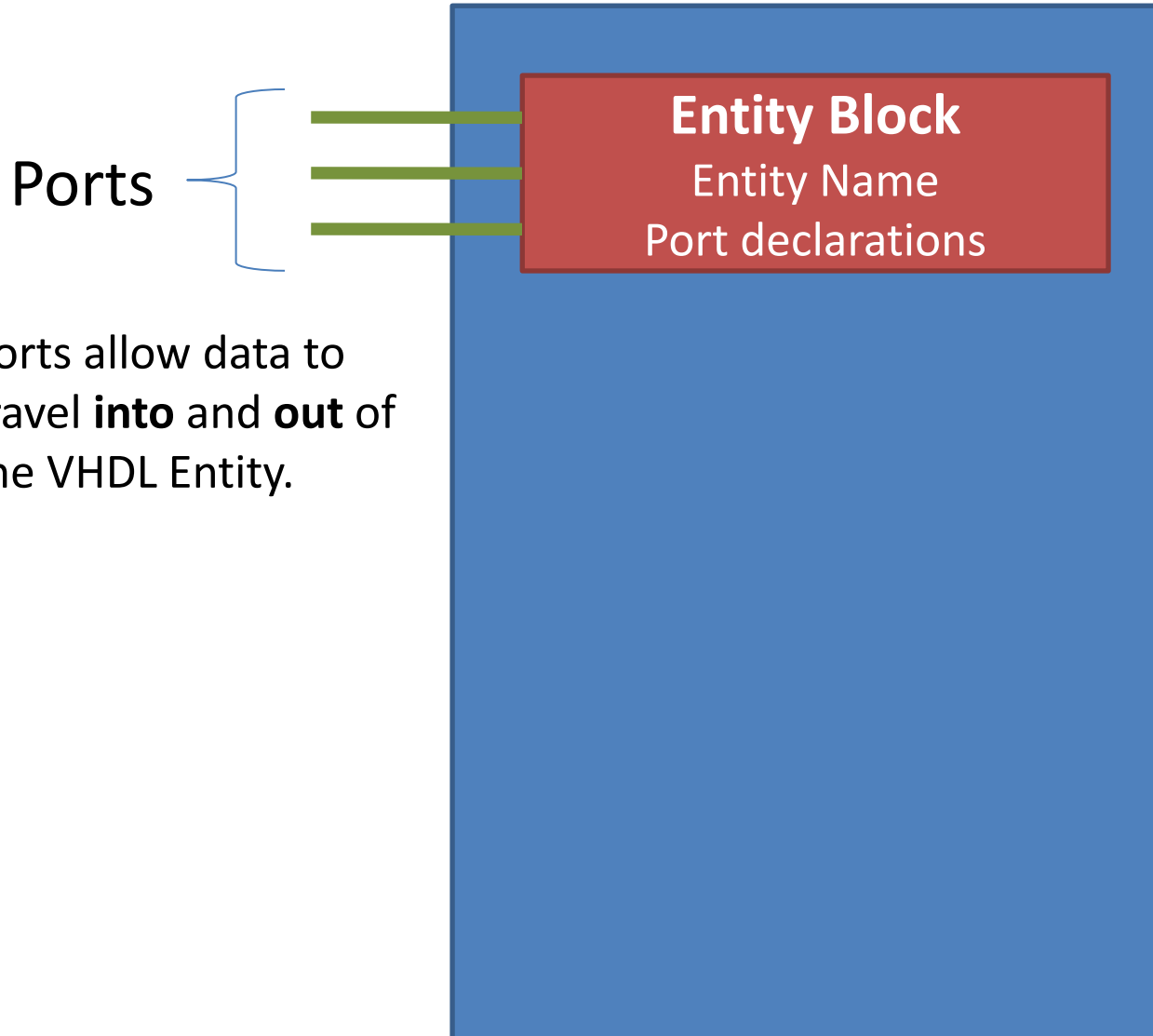


VHDL File Structure

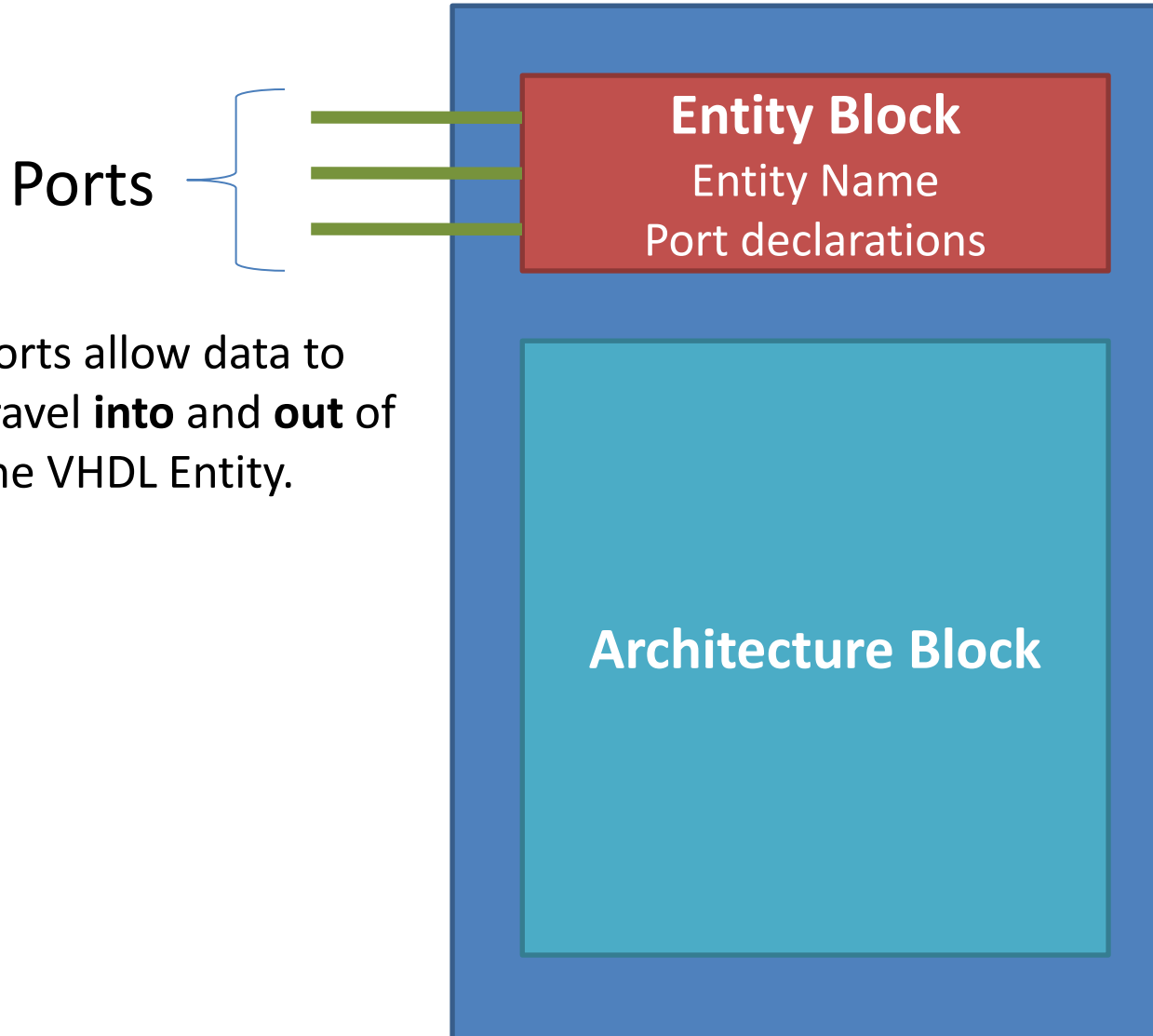


VHDL File Structure

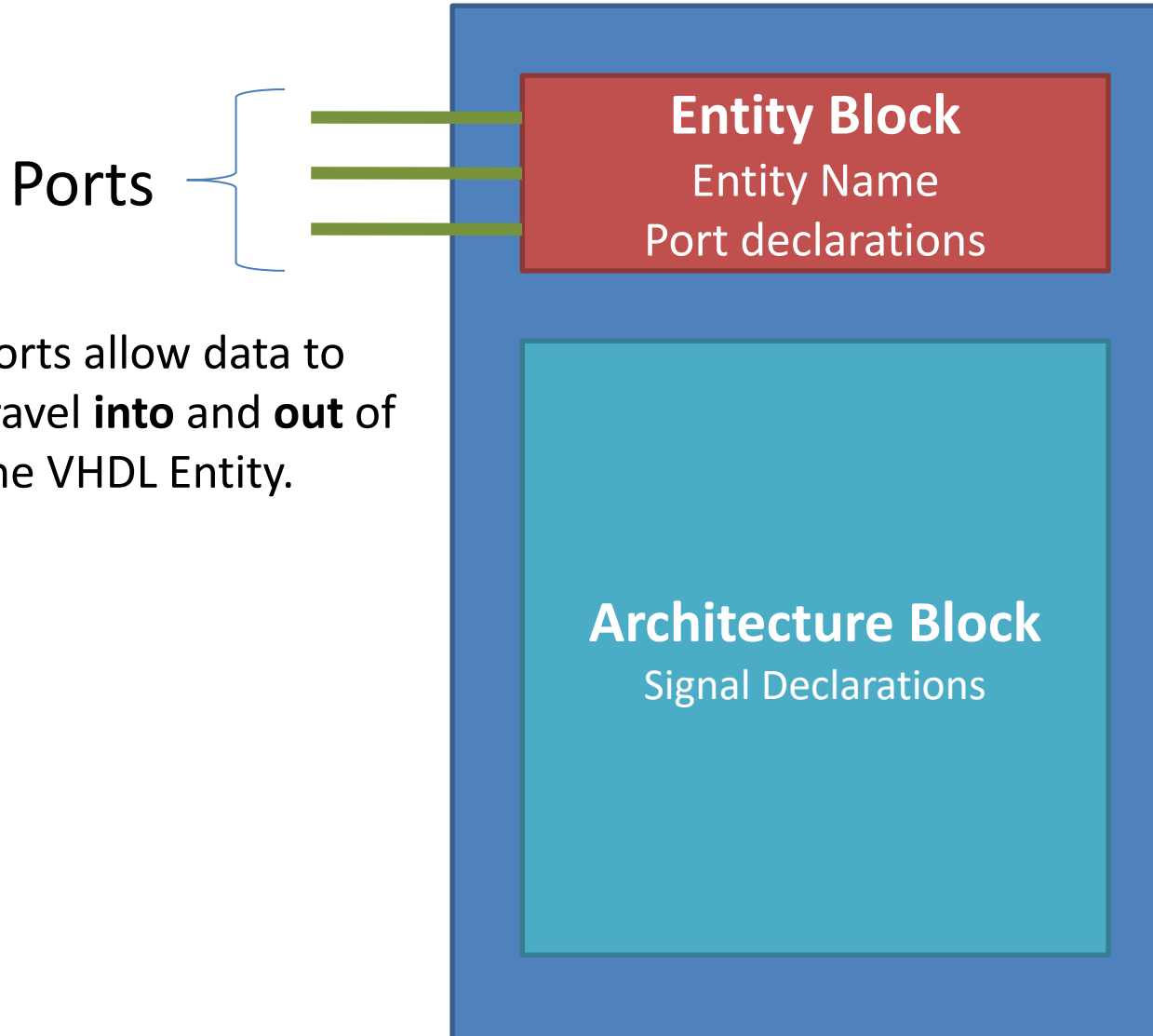


VHDL File Structure

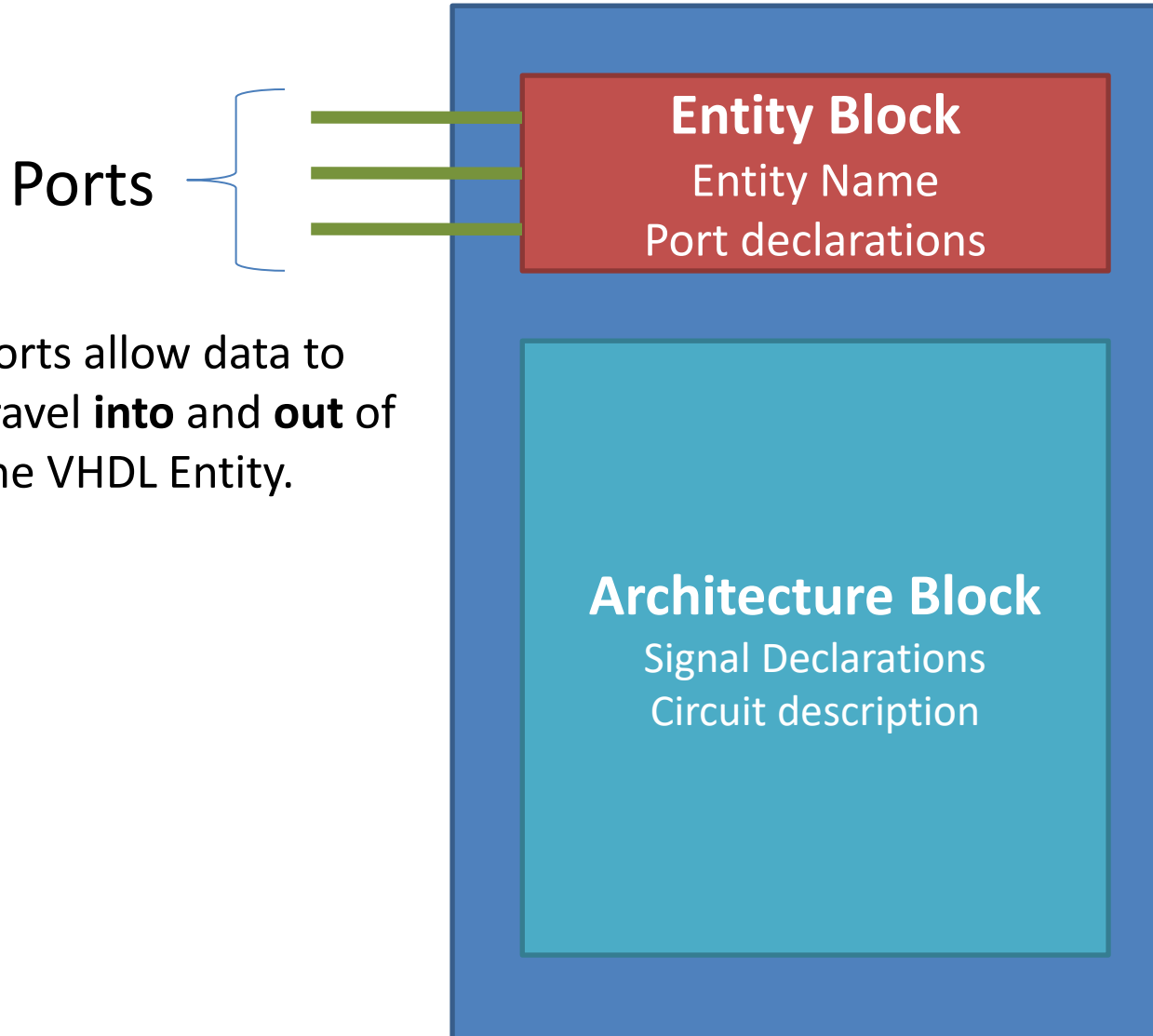


VHDL File Structure

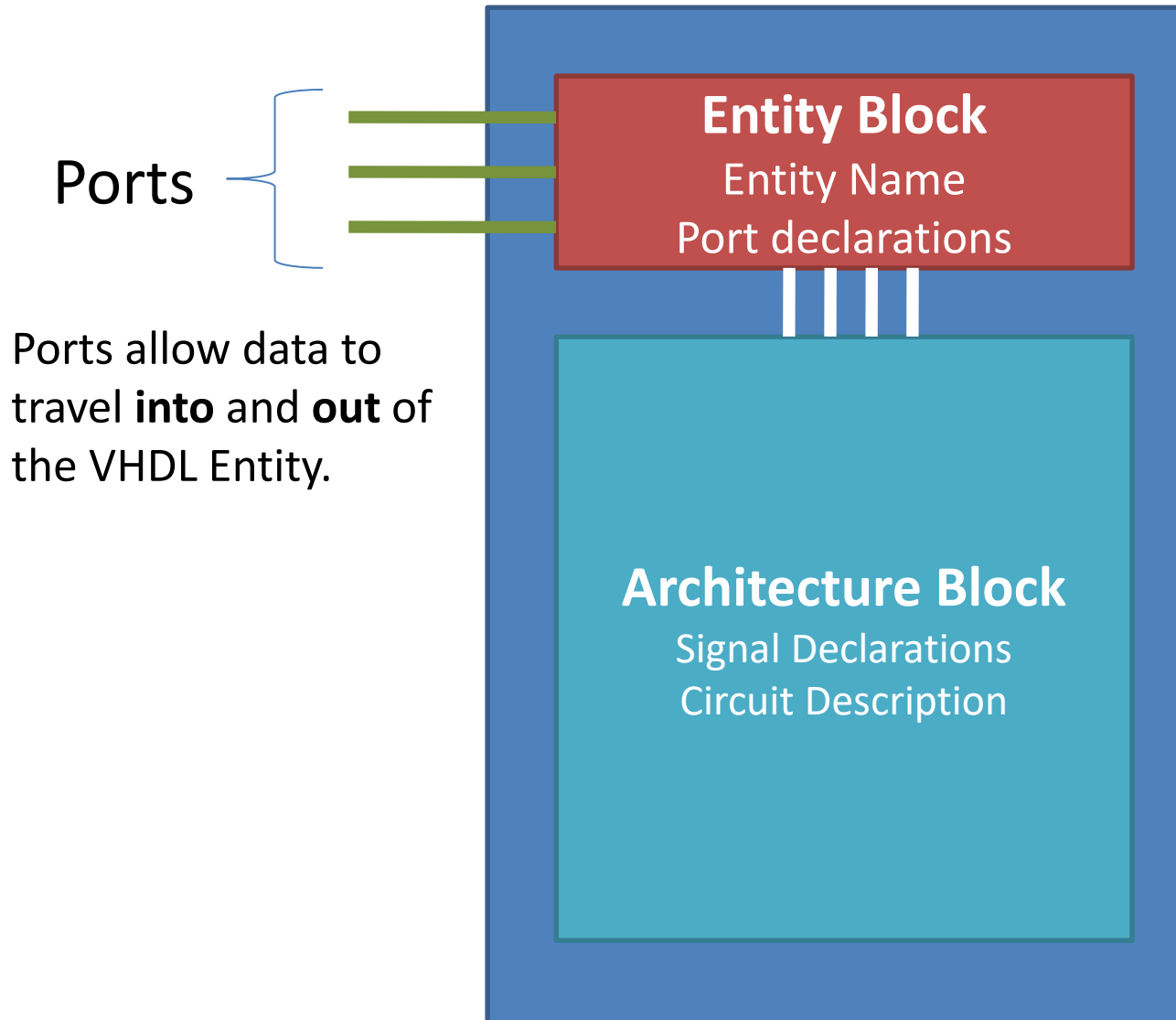


VHDL File Structure

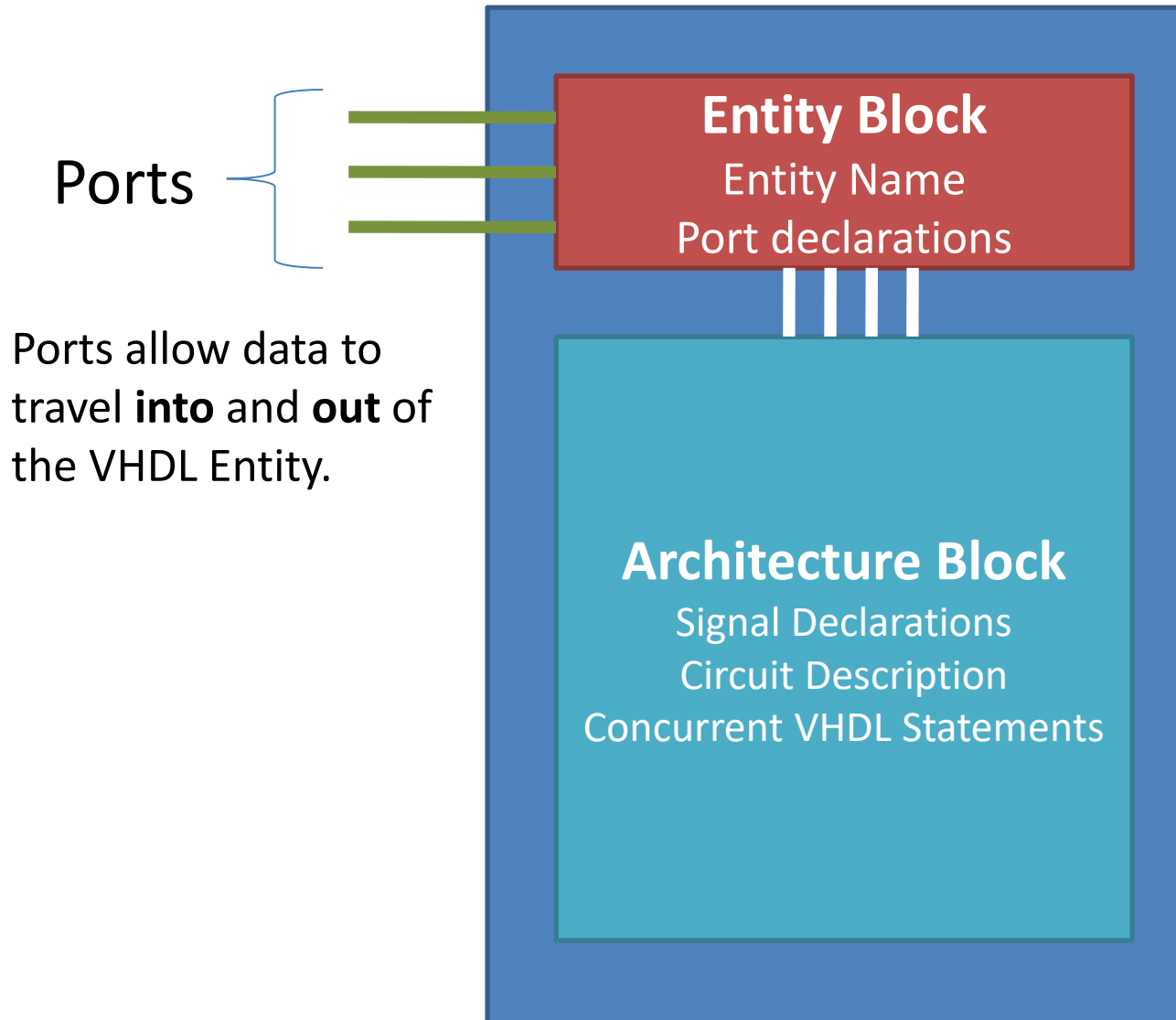


VHDL File Structure

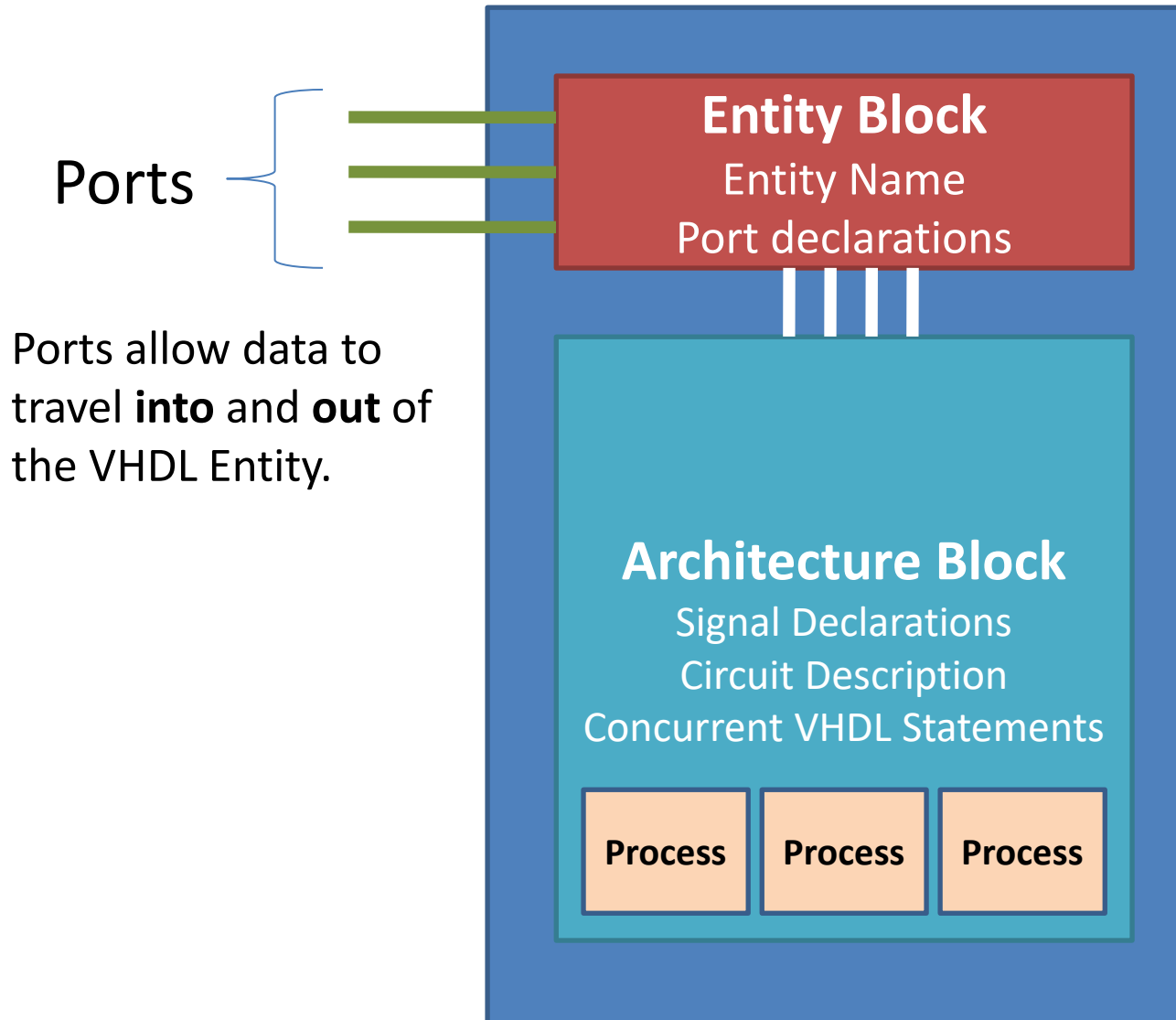

VHDL File Structure

 

VHDL File Structure

 

VHDL File Structure




The diagram illustrates the structure of a VHDL file. It consists of a large blue rectangle representing the entire file. Inside the top portion of this rectangle is a smaller red rectangle representing the 'Entity Block'. The red rectangle contains the text: 'Entity Block', 'Entity Name = MyEntity', and 'Ports (A,B,C,Y)'. The remaining space within the blue rectangle is empty, representing the architecture and other declarations.

Entity Block


Entity Name = MyEntity

Ports (A,B,C,Y)


VHDL File Structure

 


VHDL File Structure

 


VHDL File Structure

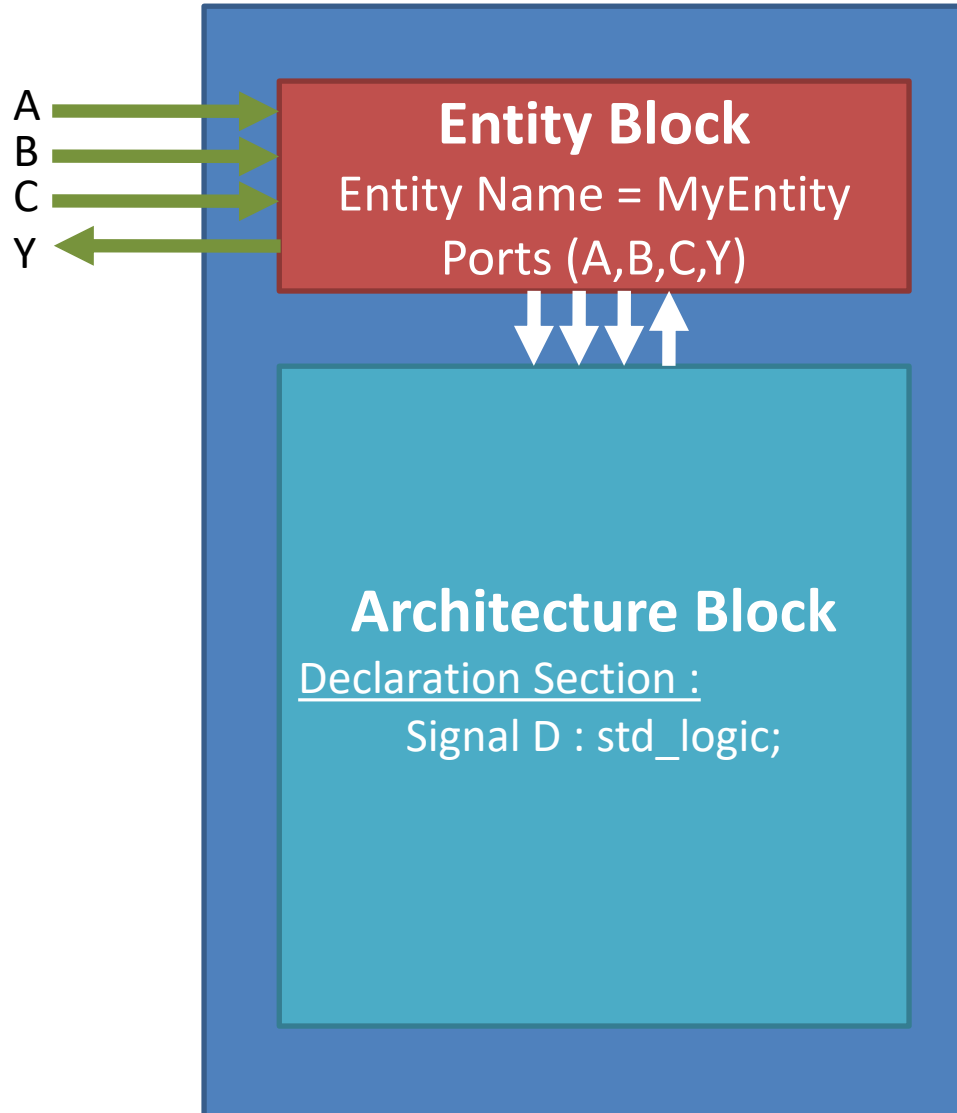


VHDL File Structure

 

VHDL File Structure

 

VHDL File Structure

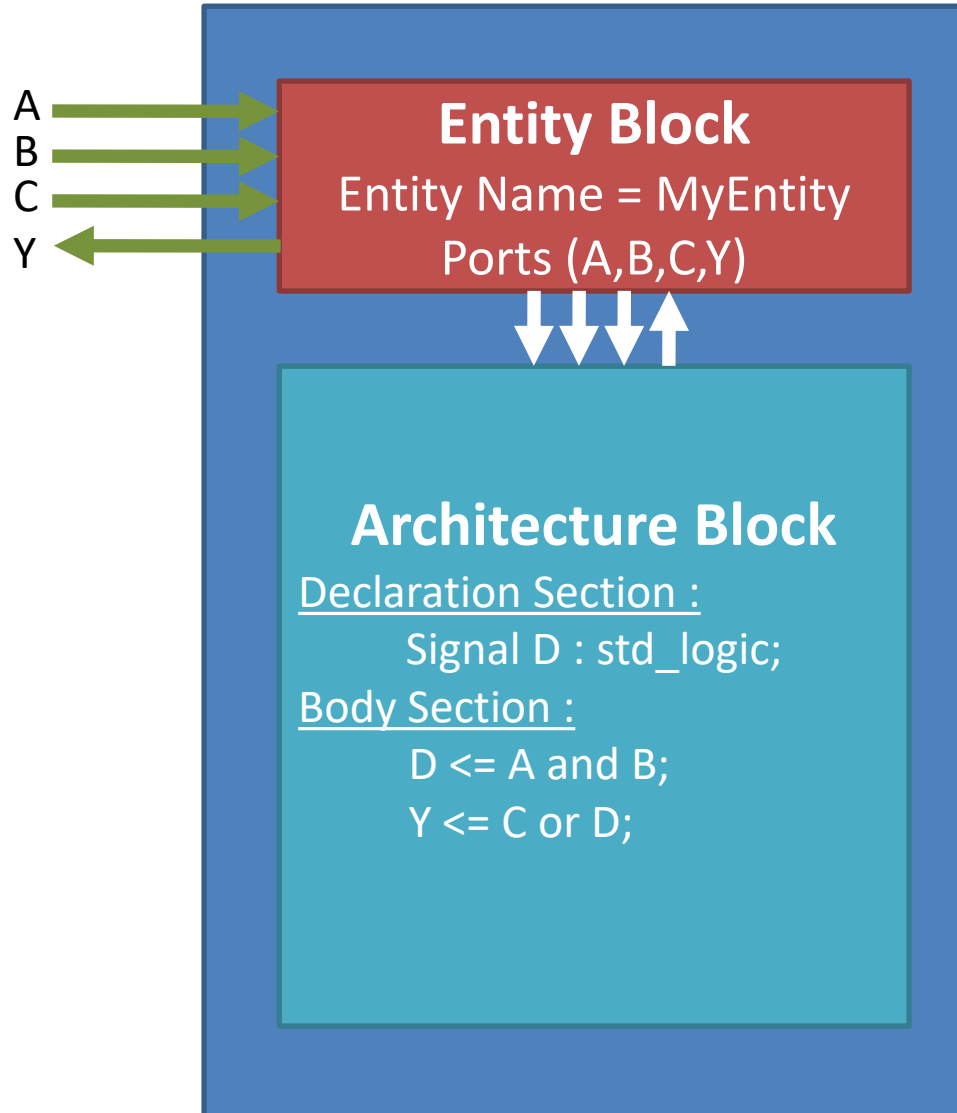

Entity Code

entity MyEntity is

end entity;

Entity Code

entity MyEntity is

port (

);

end entity;

Entity Code

```
entity MyEntity is
  port (
    A : in std_logic;
    B : in std_logic;
    C : in std_logic;
    Y : out std_logic
  );
end entity;
```

Entity Code

```
entity MyEntity is
  port (
    A : in std_logic;
    B : in std_logic;
    C : in std_logic;
    Y : out std_logic
  );
end entity;
```

Architecture Code

```
architecture MyArchitecture of MyEntity is
```

```
    -- Section 1
```

```
begin
```

```
    -- Section 2
```

```
end architecture;
```

Architecture Code

```
architecture MyArchitecture of MyEntity is
```

```
    signal D : std_logic;
```

```
begin
```

```
end architecture;
```

Architecture Code

```
architecture MyArchitecture of MyEntity is
```

```
    signal D : std_logic;
```

```
begin
```

```
    D <= A and B;
```

```
end architecture;
```


Architecture Code

```
architecture MyArchitecture of MyEntity is
```

```
    signal D : std_logic;
```

```
begin
```

```
    D <= A and B;
```

```
    Y <= C or D;
```

```
end architecture;
```

```
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity MyEntity is  
    port (  
        A : in std_logic;  
        B : in std_logic;  
        C : in std_logic;  
        Y : out std_logic  
    );  
end entity;
```

```
architecture MyArchitecture of MyEntity is  
    signal D : std_logic;  
begin  
    D <= A and B;  
    Y <= C or D;  
end architecture;
```

```
library ieee;  
use ieee.std_logic_1164.all;
```



```
entity MyEntity is  
  port (  
    A : in std_logic;  
        B : in std_logic;  
        C : in std_logic;  
        Y : out std_logic  
  );  
end entity;
```

```
architecture MyArchitecture of MyEntity is  
  signal D : std_logic;  
begin  
  D <= A and B;  
  Y <= C or D;  
end architecture;
```

Summary

- Overview of a VHDL file
- Entity Declaration
 - Define Entity name
 - Port Declaration
- Architecture Declaration
 - Declarative Part Of Architecture.
 - Body of Architecture.

Summary

- Overview of a VHDL file
- Entity Declaration
 - Define Entity name
 - Port Declaration
- Architecture Declaration
 - Declarative Part Of Architecture.
 - Body of Architecture.

The VHDL Process Block

Process Block

- Written inside the Architecture Body
- Can have multiple process blocks

Process Block Syntax

```
process_name : process (sensitivity_list)
    -- Declarative Section
begin
    -- Body Section
end process;
```


Process Block Syntax

```
process_name : process (sensitivity_list)
    -- Declarative Section
begin
    -- Body Section
end process;
```

Process Block – Sensitivity List

- Is a list of signals

Process Block – Sensitivity List

- Is a list of signals
- The process waits for one of the signals in this list to CHANGE state before running.

Process Block – Sensitivity List

- Is a list of signals
- The process waits for one of the signals in this list to CHANGE state before running.
- Process Block runs only when a signal in the sensitivity list changes state.

Process Block – Sensitivity List

- Is a list of signals
- The process waits for one of the signals in this list to CHANGE state before running.
- Process Block runs only when a signal in the sensitivity list changes state.
- The process block is run once at time 0.

Process - Example

```
TestProcess1: process(Sig1)
begin
    Sig2 <= Sig1;
end process;
```

Process - Example

```
AND_GATE : process(A, B)
```

```
begin
```

```
    C <= A and B;
```

```
end process;
```

Process - Example

```
AND_GATE : process(A, B)
```

```
begin
```

```
    C <= A and B;
```

```
end process;
```


Incomplete Sensitivity List

```
AND_GATE : process(A)
```


```
begin
```

```
  C <= A and B;
```


```
end process;
```

Missing signal B

When A Changes

 

When B Changes

 

Incomplete Sensitivity List

```
AND_GATE : process(A)
```

```
begin
```

```
  C <= A and B;
```


```
end process;
```

Missing signal B

When A Changes




When B Changes

 

Registered Process

- Used to implement registers (or flip-flops).
- Sensitivity list can **only** contain :
 - A Clock signal (Compulsory)
 - A Reset signal (Optional)
- Checks for the clock rising or falling edge.

Flip Flop Circuit

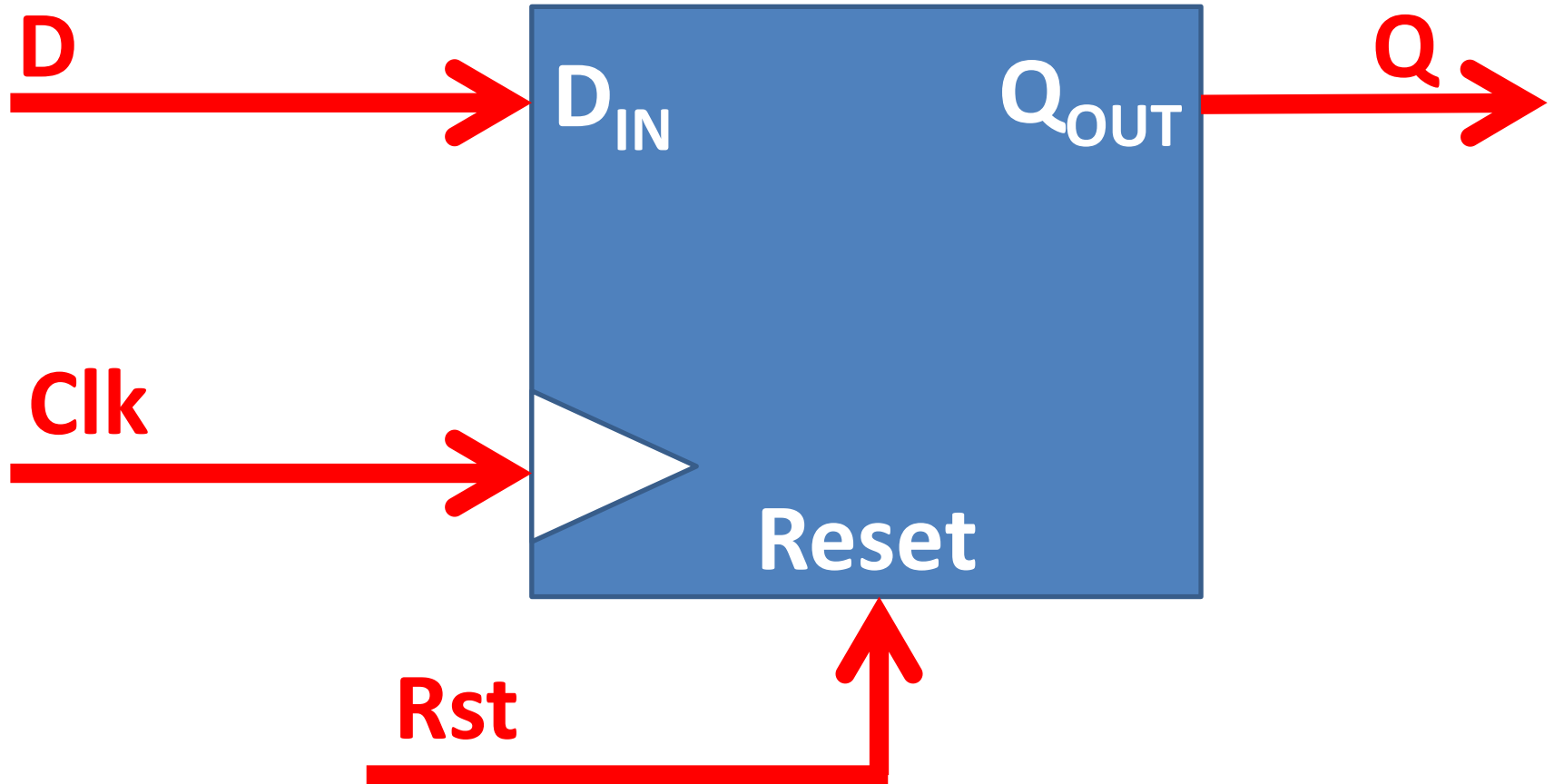

Registered Process

```
TestProcess : process(Rst, Clk)
```

```
begin
```

```
end process;
```

Registered Process

```
TestProcess : process(Rst, Clk)
```

```
begin
```

```
    if Rst = '1' then
```

```
end process;
```

Registered Process

```
TestProcess : process(Rst, Clk)
```

```
begin
```

```
    if Rst = '1' then
```

```
        Q <= '0';
```

```
end process;
```

Registered Process

```
TestProcess : process(Rst, Clk)
```

```
begin
```

```
    if Rst = '1' then
```

```
        Q <= '0';
```

```
    elsif rising_edge(Clk) then
```

```
end process;
```


Registered Process

```
TestProcess : process(Rst, Clk)
```

```
begin
```

```
    if Rst = '1' then
```

```
        Q <= '0';
```

```
    elsif rising_edge(Clk) then
```

```
        Q <= D;
```

```
end process;
```

Registered Process

```
TestProcess : process(Rst, Clk)
```

```
begin
```

```
  if Rst = '1' then
```

```
    Q <= '0';
```

```
  elsif rising_edge(Clk) then
```

```
    Q <= D;
```

```
  end if
```

```
end process;
```

More on Registered Processes

- Signals driven by a registered process are always outputs of flip flops.

More on Registered Processes

- Signals driven by a registered process are always outputs of flip flops.

```
TestProcess2 : process(Reset, Clock)
```

```
begin
```

```
  if Reset = '1' then
```

```
    Out1 <= '0';
```

```
    Out2 <= '0';
```

```
    Out3 <= '0';
```

```
  elsif rising_edge(Clock) then
```

```
    Out1 <= A;
```

```
    Out2 <= A and B;
```

```
    Out3 <= A or B;
```

```
  end if;
```

```
end process;
```

Clocked Section

A signal assigned here
will create a flip flop.

More on Registered Processes

- Signals driven by a registered process are always outputs of flip flops.

```
TestProcess2 : process(Reset, Clock)
```

```
begin
```

```
  if Reset = '1' then
```

```
    Out1 <= '0';
```

```
    Out2 <= '0';
```

```
    Out3 <= '0';
```

```
  elsif rising_edge(Clock) then
```

```
    Out1 <= A;
```

```
    Out2 <= A and B;
```

```
    Out3 <= A or B;
```


```
  end if;
```

```
end process;
```

Clocked Section


A signal assigned here
will create a flip flop.

More on Registered Processes

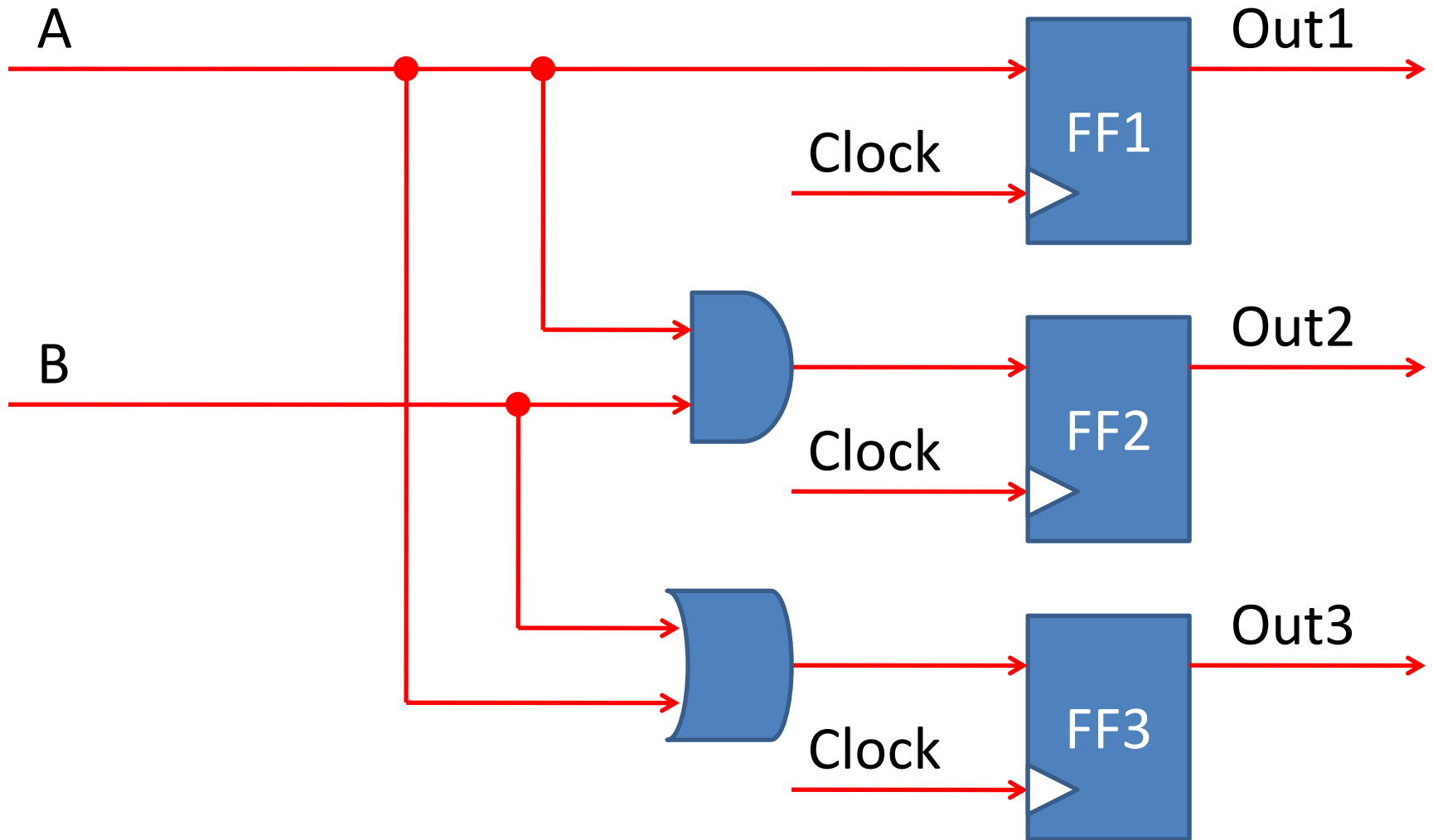


More on Registered Processes
 
```
TestProcessGeneral : process(Reset, Clock)
begin
    if Reset = '1' then
        Y <= '0';
    elsif rising_edge(Clock) then
        Y <= Function(X1, X2, X3,... XN);
    end if;
end process;
```




More on Registered Processes
 
```
TestProcessGeneral : process(Reset, Clock)
begin
    if Reset = '1' then
        Y <= '0';
    elsif rising_edge(Clock) then
        Y <= Function(X1, X2, X3,... XN);
    end if;
end process;
```



More on Registered Processes
 
```
TestProcessGeneral : process(Reset, Clock)
begin
    if Reset = '1' then
        Y <= '0';
    elsif rising_edge(Clock) then
        Y <= Function(X1, X2, X3,... XN);
    end if;
end process;
```



Comments

- **rising_edge()** -> Is a function found in the std_logic_1164 Package.
- **falling_edge()**

Comments

```
if Condition1 then
    -- Statement Group 1
elseif Condition2 then
    -- Statement Group 2
else
    -- Statement Group 3
end if;
```

More on the IF Statement

- If statements must be written inside process block

```
if Condition1 then
    -- Statement Group 1
else
    -- Statement Group 2
end if;
```

```
if Condition2 then
    -- Statement Group 3
end if;
```

Sensitivity List

- What goes in a sensitivity list?

Combinational Process	Registered Process
<u>All</u> signals read within the process.	<u>Only</u> Clock and reset.

Sensitivity List

- What goes in a sensitivity list?

Combinational Process	Registered Process
<u>All</u> signals read within the process.	<u>Only</u> Clock and reset.

- Sensitivity list can be empty:
 - Only used in simulation!
 - Then must have wait statements.
 - Not synthesisable.

More on Processes

Example 1

Process A
Sig1<= '0';

Process B
Sig1 <= '0';

More on Processes

Example 1

Process A
Sig1<= '0';

Process B
Sig1 <= '0';



More on Processes

Example 2

Process A
Sig1<= '0';

Process B
Sig2 <= '0';



More on Processes

Example 3

Process A
Sig1 <= X;

Process B
Sig2 <= X;





Summary

- What is a process?
- Combinational & Registered Processes.
- Writing a basic process in VHDL.
- Sensitivity list.
- If statement
- rising_edge() & falling_edge() functions.
- Hardware visualisation of a process.

Component Instantiation

VHDL File

  

Entity A

A

B

C

TopLevelEntity

X




Y

Entity A

A

B

C

  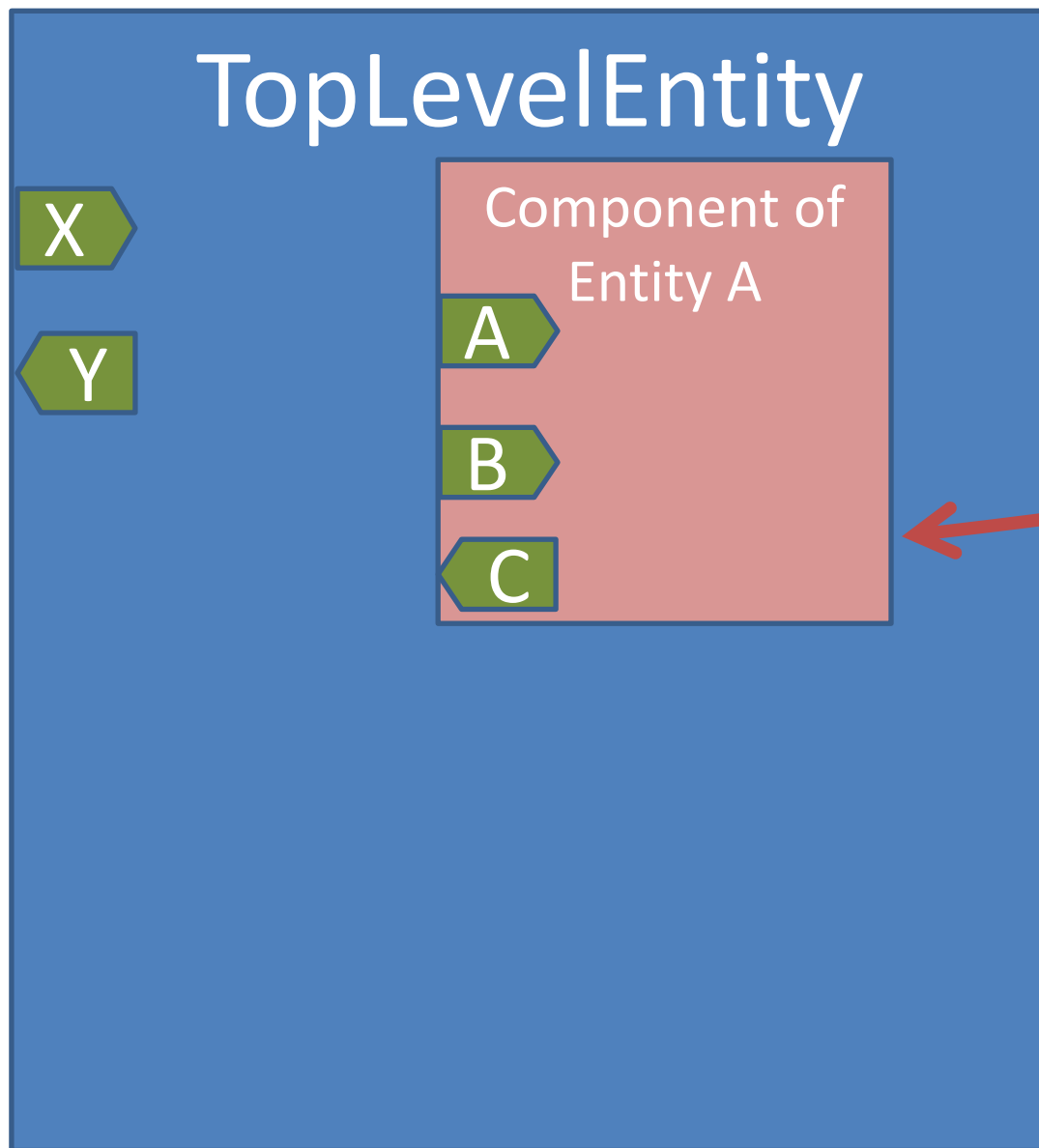

TopLevelEntity

X

Y

Component of
Entity A

A

B




C

Entity A


A

B


C

  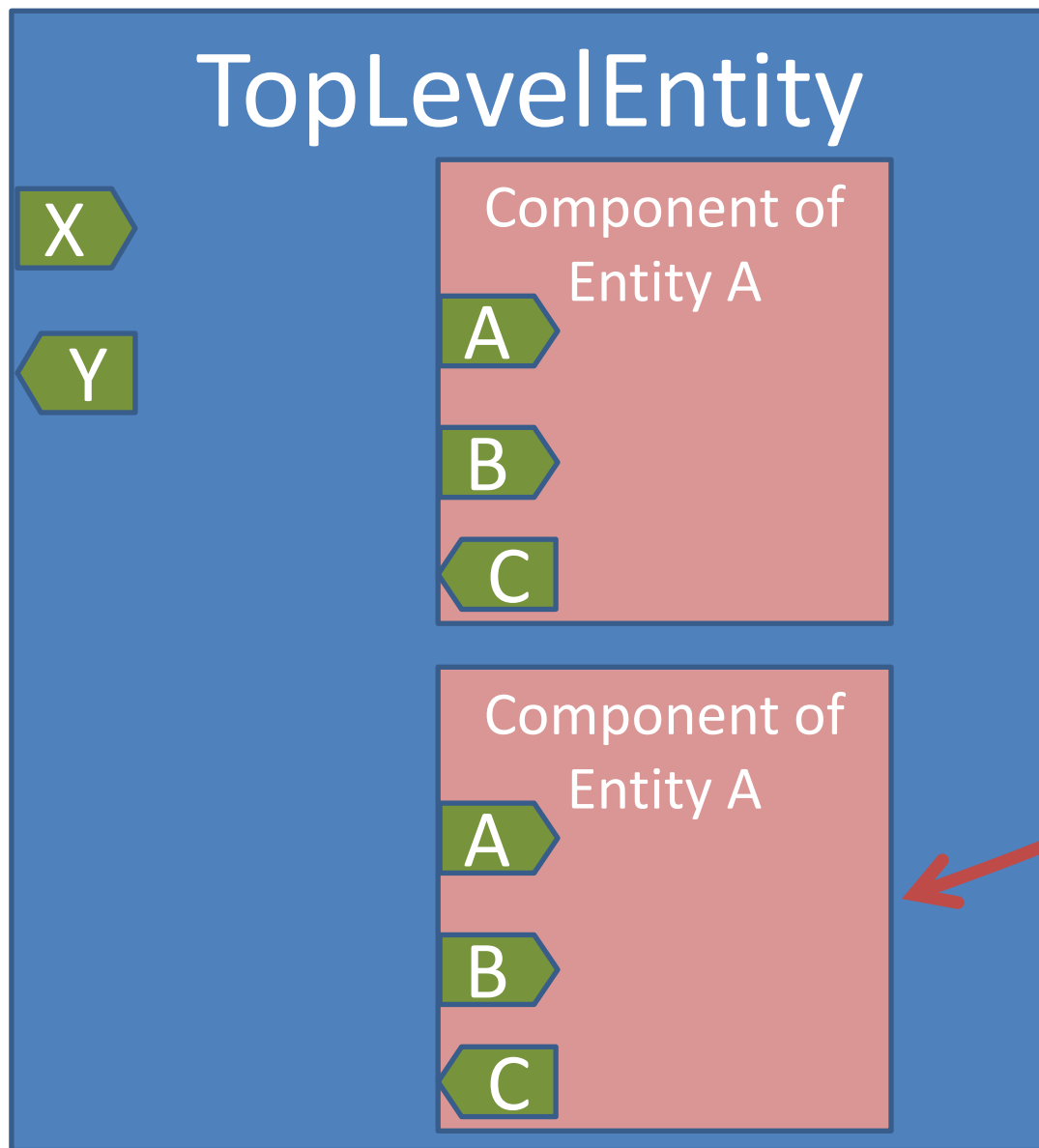


TopLevelEntity

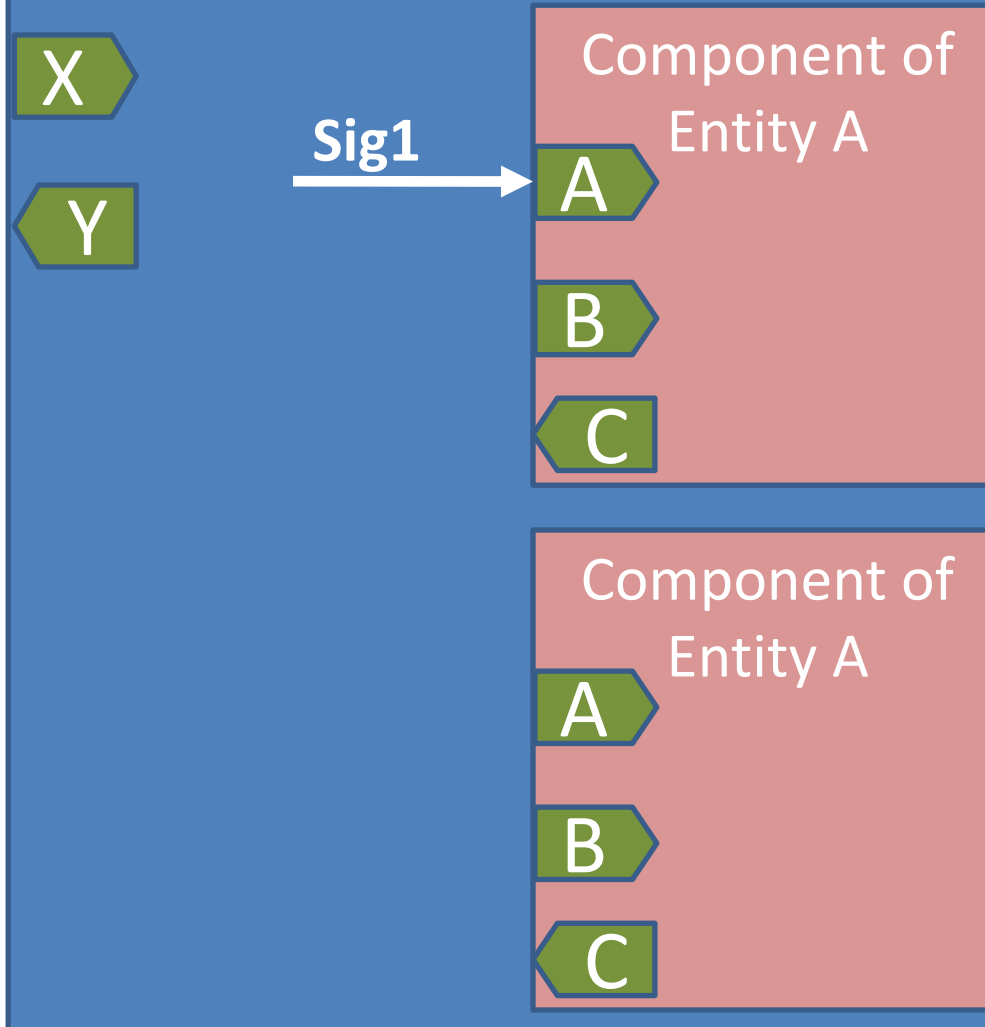

TopLevelEntity

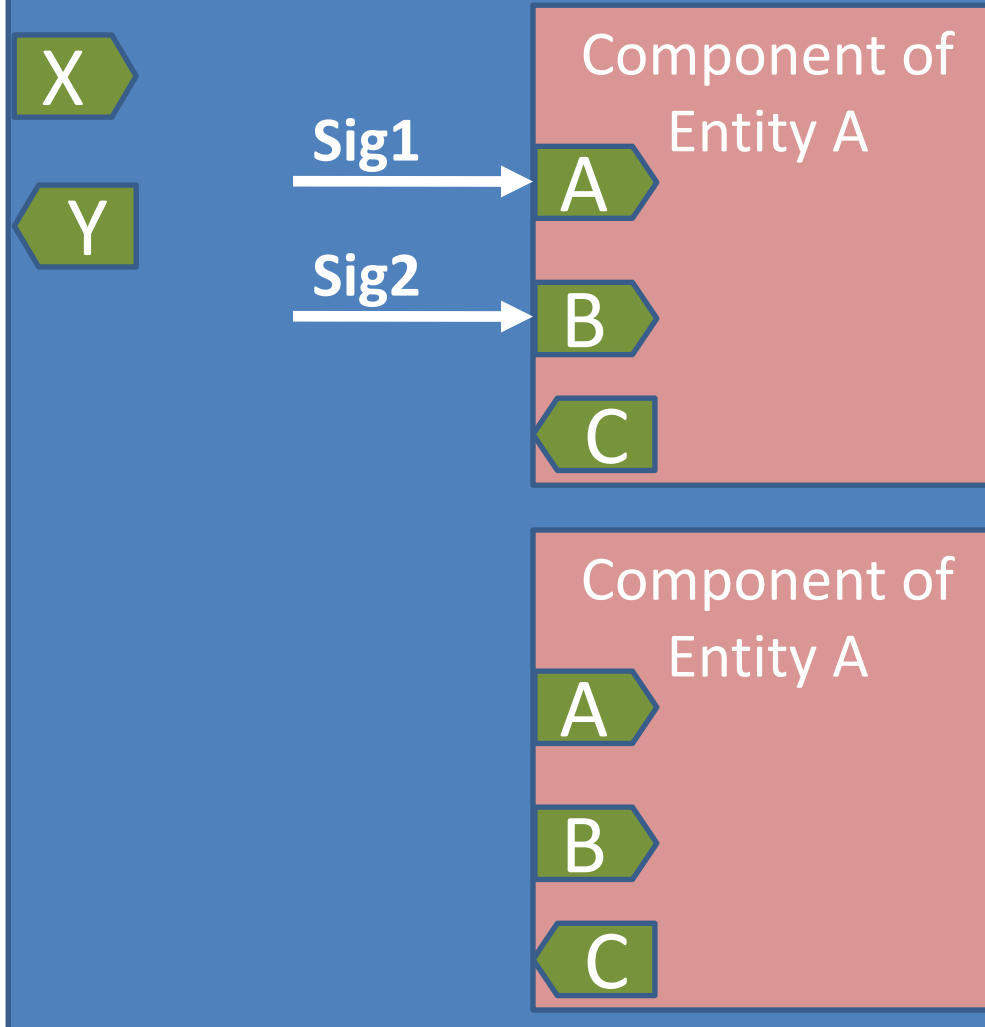

TopLevelEntity

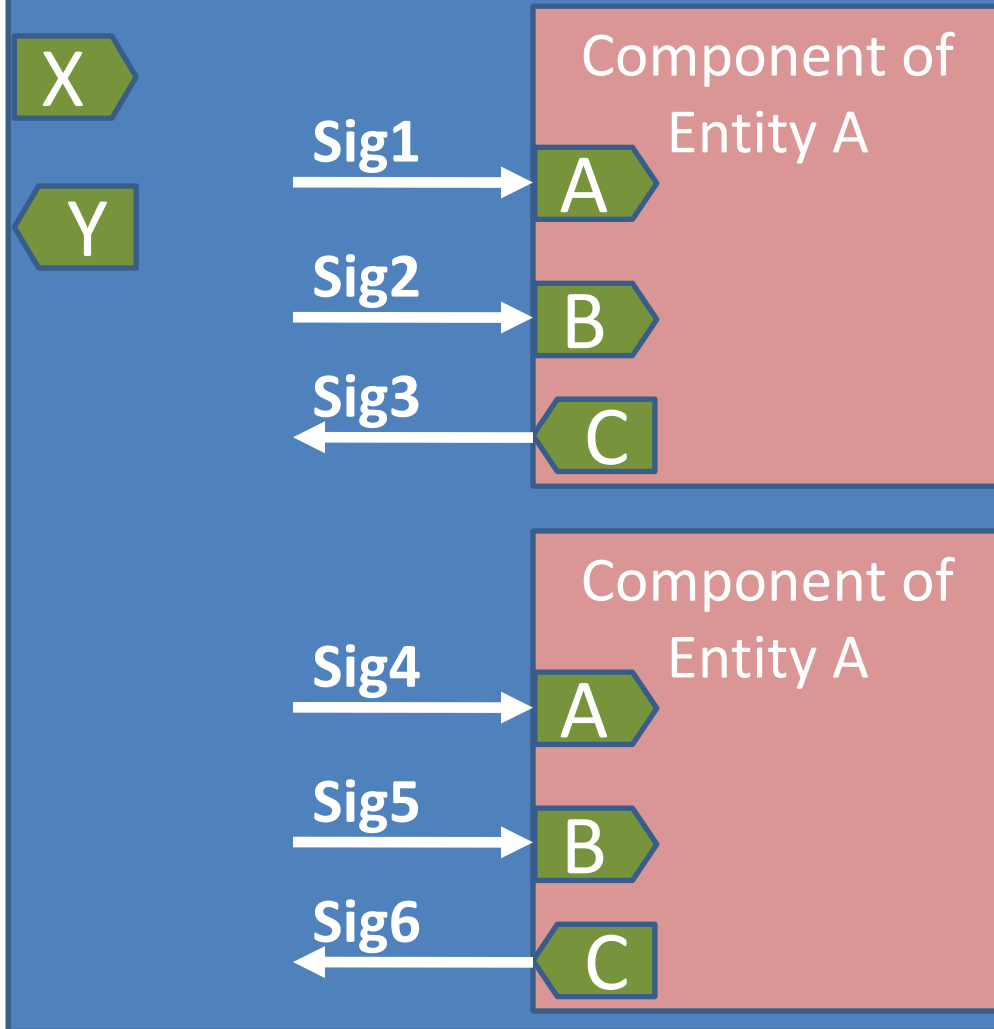

VHDL File Template

-- Declare your VHDL libraries & packages up here.

entity EntityName is

port

(

-- Declare your modules's IO ports here!

);

end entity;

architecture ArchitectureName of EntityName is

-- Declare your internal signals & constants here

begin

-- Define your module's behaviour here!

end architecture;

VHDL Entity A



VHDL Entity A

```
entity EntityA is
```

```
end entity;
```


VHDL Entity A

```
entity EntityA is
  port
  (
    A : in  integer range 0 to 255;
    B : in  integer range 0 to 255;
    C : out integer range 0 to 511
  );
end entity;
```

VHDL Entity A

```
entity EntityA is
```

```
  port
```

```
  (
```

```
    A : in  integer range 0 to 255;
```

```
    B : in  integer range 0 to 255;
```

```
    C : out integer range 0 to 511
```

```
  );
```

```
end entity;
```

```
architecture rtl of EntityA is
```

VHDL Entity A

```
entity EntityA is
  port
  (
    A : in  integer range 0 to 255;
    B : in  integer range 0 to 255;
    C : out integer range 0 to 511
  );
end entity;

architecture rtl of EntityA is
begin
```

VHDL Entity A

```
entity EntityA is
```

```
  port
```

```
  (
```

```
    A : in  integer range 0 to 255;
```

```
    B : in  integer range 0 to 255;
```

```
    C : out integer range 0 to 511
```

```
  );
```

```
end entity;
```

```
architecture rtl of EntityA is
```

```
begin
```

```
  C <= A + B; -- Perform the addition operation.
```

```
end architecture;
```

```
entity TopLevelEntity is
  port
  (
    X : in  integer range 0 to 255;
    Y : out integer range 0 to 255
  );
end entity;
```

```
entity TopLevelEntity is
  port
  (
    X : in  integer range 0 to 255;
    Y : out integer range 0 to 255
  );
end entity;

architecture rtl of TopLevelEntity is
```

```
entity TopLevelEntity is
  port
  (
    X : in  integer range 0 to 255;
    Y : out integer range 0 to 255
  );
end entity;
```

```
architecture rtl of TopLevelEntity is
```

```
  signal Sig1, Sig2, Sig4, Sig5 : integer range 0 to 255;
  signal Sig3, Sig6 : integer range 0 to 511;
```

```
entity TopLevelEntity is
  port
  (
    X : in  integer range 0 to 255;
    Y : out integer range 0 to 255
  );
end entity;
```

```
architecture rtl of TopLevelEntity is
```

```
  signal Sig1, Sig2, Sig4, Sig5 : integer range 0 to 255;
  signal Sig3, Sig6 : integer range 0 to 511;
```

```
  component EntityA is
  port
  (
    A : in  integer range 0 to 255;
    B : in  integer range 0 to 255;
    C : out integer range 0 to 511
  );
end component ;
```



```
entity TopLevelEntity is
  port
  (
    X : in  integer range 0 to 255;
    Y : out integer range 0 to 255
  );
end entity;
```

```
architecture rtl of TopLevelEntity is
```

```
  signal Sig1, Sig2, Sig4, Sig5 : integer range 0 to 255;
  signal Sig3, Sig6 : integer range 0 to 511;
```

```
  component EntityA is
  port
  (
    A : in  integer range 0 to 255;
    B : in  integer range 0 to 255;
    C : out integer range 0 to 511
  );
  end component ;
```

```
begin
```

```
entity TopLevelEntity is
  port
  (
    X : in  integer range 0 to 255;
    Y : out integer range 0 to 255
  );
end entity;
```

```
architecture rtl of TopLevelEntity is
```

```
  signal Sig1, Sig2, Sig4, Sig5 : integer range 0 to 255;
  signal Sig3, Sig6 : integer range 0 to 511;
```

```
  component EntityA is
  port
  (
    A : in  integer range 0 to 255;
    B : in  integer range 0 to 255;
    C : out integer range 0 to 511
  );
  end component ;
```

```
begin
```

```
  Instance1
```

```
entity TopLevelEntity is
  port
  (
    X : in  integer range 0 to 255;
    Y : out integer range 0 to 255
  );
end entity;
```


```
architecture rtl of TopLevelEntity is
```

```
  signal Sig1, Sig2, Sig4, Sig5 : integer range 0 to 255;
  signal Sig3, Sig6 : integer range 0 to 511;
```

```
  component EntityA is
  port
  (
    A : in  integer range 0 to 255;
    B : in  integer range 0 to 255;
    C : out integer range 0 to 511
  );
end component ;
```

```
begin
```

```
  Instance1 : EntityA
```

 

```
entity TopLevelEntity is
  port
  (
    X : in  integer range 0 to 255;
    Y : out integer range 0 to 255
  );
end entity;
```

```
architecture rtl of TopLevelEntity is
```

```
  signal Sig1, Sig2, Sig4, Sig5 : integer range 0 to 255;
  signal Sig3, Sig6 : integer range 0 to 511;
```

```
  component EntityA is
    port
    (
      A : in  integer range 0 to 255;
      B : in  integer range 0 to 255;
      C : out integer range 0 to 511
    );
  end component ;
```

```
begin
```

```
  Instance1 : EntityA
  port map
```

```
entity TopLevelEntity is
  port
  (
    X : in  integer range 0 to 255;
    Y : out integer range 0 to 255
  );
end entity;
```

```
architecture rtl of TopLevelEntity is
```

```
  signal Sig1, Sig2, Sig4, Sig5 : integer range 0 to 255;
  signal Sig3, Sig6 : integer range 0 to 511;
```

```
  component EntityA is
    port
    (
      A : in  integer range 0 to 255;
      B : in  integer range 0 to 255;
      C : out integer range 0 to 511
    );
  end component ;
```

```
begin
```

```
  Instance1 : EntityA
  port map
  (
    A
    B
    C
  );
```

```
entity TopLevelEntity is
  port
  (
    X : in  integer range 0 to 255;
    Y : out integer range 0 to 255
  );
end entity;
```

```
architecture rtl of TopLevelEntity is
```

```
  signal Sig1, Sig2, Sig4, Sig5 : integer range 0 to 255;
  signal Sig3, Sig6 : integer range 0 to 511;
```

```
  component EntityA is
    port
    (
      A : in  integer range 0 to 255;
      B : in  integer range 0 to 255;
      C : out integer range 0 to 511
    );
  end component ;
```

```
begin
```

```
  Instance1 : EntityA
  port map
  (
    A => Sig1,
    B => Sig2,
    C => Sig3
  );
```

```
entity TopLevelEntity is
  port
  (
    X : in  integer range 0 to 255;
    Y : out integer range 0 to 255
  );
end entity;
```

```
architecture rtl of TopLevelEntity is
```

```
  signal Sig1, Sig2, Sig4, Sig5 : integer range 0 to 255;
  signal Sig3, Sig6 : integer range 0 to 511;
```

```
  component EntityA is
    port
    (
      A : in  integer range 0 to 255;
      B : in  integer range 0 to 255;
      C : out integer range 0 to 511
    );
  end component ;
```

```
begin
```

```
  Instance1 : EntityA
  port map
  (
    A => Sig1,
    B => Sig2,
    C => Sig3
  );
```

```
  Instance2 : EntityA
  port map
  (
    A => Sig4,
    B => Sig5,
    C => Sig6
  );
```

```
end architecture;
```

```
entity TopLevelEntity is
  port
  (
    X : in  integer range 0 to 255;
    Y : out integer range 0 to 255
  );
end entity;
```

```
architecture rtl of TopLevelEntity is
```

```
  signal Sig1, Sig2, Sig4, Sig5 : integer range 0 to 255;
  signal Sig3, Sig6 : integer range 0 to 511;
```

```
  component EntityA is
    port
    (
      A : in  integer range 0 to 255;
      B : in  integer range 0 to 255;
      C : out integer range 0 to 511
    );
  end component ;
```

```
begin
```

```
  Instance1 : EntityA
  port map
  (
    A => Sig1,
    B => Sig2,
    C => Sig3
  );
```

```
  Instance2 : EntityA
  port map
  (
    A => Sig4,
    B => Sig5,
    C => Sig6
  );
```

```
end architecture;
```


VHDL File Template

-- Declare your VHDL libraries & packages up here.

entity EntityName is

port

(

-- Declare your modules's IO ports here!

);

end entity;

architecture ArchitectureName of EntityName is

-- Declare your internal signals & constants here

-- Declare components

begin

-- Define your module's behaviour here!

end architecture;

VHDL Concurrent Statements

VHDL Statements

Concurrent VHDL Statements :

- Can only be used inside the **Architecture** Block.

Sequential VHDL Statements :

- Can only be used inside the **Process** Block.

Concurrent VHDL Statements

- Process Block
- Component Instantiation
- Concurrent Signal Assignments (using `<=`)
- Conditional Signal Assignment (When – Else)
- Selected Signal Assignment (With – Select)
- Generate

Concurrent VHDL Statements

- Process Block
- Component Instantiation
- Concurrent Signal Assignments (using `<=`)
- Conditional Signal Assignment (When – Else)
- Selected Signal Assignment (With – Select)
- Generate

A <= B;

Concurrent VHDL Statements

- Process Block
- Component Instantiation
- Concurrent Signal Assignments
- Conditional Signal Assignment (When – Else)
- Selected Signal Assignment (With – Select)
- Generate

When-Else

architecture RTL of MyEntity is

```
A <= "1000" when B = "00" else  
      "0100" when B = "01" else  
      "0010" when B = "10" else  
      "0001";
```

end architecture;

With-Select

architecture RTL of MyEntity is

with B select

A <= "1000" when "00",
 "0100" when "01",
 "0010" when "10",
 "0001" when others;

end architecture;

Generate Statement

- Replicate hardware (for generate)

Generate Statement

- Replicate hardware (for generate)
- Conditional hardware (if generate)

Generate Statement

- Can be used to create :
 - Component instances
 - Signal Assignments
 - Process Blocks

For Generate Syntax

```
Label: for parameter in range generate  
    -- Hardware to Generate  
end generate;
```

For Generate Syntax

```
Label: for parameter in range generate  
    -- Hardware to Generate  
end generate;
```

For Generate Example 1

```
Signal InputSignal    : std_logic_vector(15 downto 0);
```

For Generate Example 1

```
Signal InputSignal    : std_logic_vector(15 downto 0);  
Signal EvenBits       : std_logic_vector(7  downto 0);  
Signal OddBits        : std_logic_vector(7  downto 0);
```

For Generate Example 1

```
Signal InputSignal    : std_logic_vector(15 downto 0);  
Signal EvenBits       : std_logic_vector(7  downto 0);  
Signal OddBits        : std_logic_vector(7  downto 0);
```

```
EvenBits(0) <= InputSignal(0);  
EvenBits(1) <= InputSignal(2);  
EvenBits(2) <= InputSignal(4);
```

```
.....
```


For Generate Example 1

```
Signal InputSignal    : std_logic_vector(15 downto 0);  
Signal EvenBits       : std_logic_vector(7  downto 0);  
Signal OddBits        : std_logic_vector(7  downto 0);
```

```
OddBits(0) <= InputSignal(1);  
OddBits(1) <= InputSignal(3);  
OddBits(2) <= InputSignal(5);
```

```
.....
```

For Generate Example 1

```
Signal InputSignal    : std_logic_vector(15 downto 0);  
Signal EvenBits       : std_logic_vector(7  downto 0);  
Signal OddBits        : std_logic_vector(7  downto 0);
```

Example1: **for** count **in** 0 **to** 7 **generate**

For Generate Example 1

```
Signal InputSignal    : std_logic_vector(15 downto 0);  
Signal EvenBits       : std_logic_vector(7  downto 0);  
Signal OddBits        : std_logic_vector(7  downto 0);
```

Example1: **for** count **in** 0 **to** 7 **generate**

```
    EvenBits (count) <= InputSignal(2*count);
```

For Generate Example 1

```
Signal InputSignal    : std_logic_vector(15 downto 0);  
Signal EvenBits       : std_logic_vector(7  downto 0);  
Signal OddBits        : std_logic_vector(7  downto 0);
```

Example1: **for** count **in** 0 **to** 7 **generate**

EvenBits (count) <= InputSignal(2*count);

OddBits (count) <= InputSignal(2*count+1);

For Generate Example 1

```
Signal InputSignal    : std_logic_vector(15 downto 0);  
Signal EvenBits       : std_logic_vector(7  downto 0);  
Signal OddBits        : std_logic_vector(7  downto 0);
```

```
Example1: for count in 0 to 7 generate  
    EvenBits (count) <= InputSignal(2*count);  
    OddBits  (count) <= InputSignal(2*count+1);  
end generate;
```

For Generate Example 2

For Generate Example 2

Example2: for n in 0 to 19 generate

end generate;

For Generate Example 2

Example2: for n in 0 to 19 generate

MyComponent : EntityA

port map

(

A => Signal1,

B => Signal2,

C => Sum

);

end generate;

For Generate Example 2

Example2: for n in 0 to 19 generate

MyComponent : EntityA

port map

(

A => Signal1(n),

B => Signal2(n),

C => Sum(n)


);

end generate;


For Generate Example 2




For Generate Example 2

 


For Generate Example 2

 







For Generate Example 2

 

For Generate Example 2

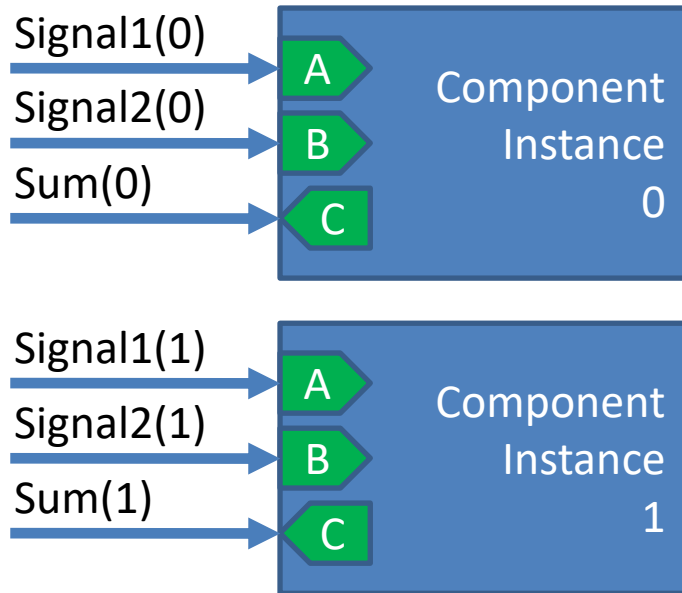

For Generate Example 2

      

For Generate Example 2

type Integer8x20 is array (0 to 19) of integer range 0 to 255;

For Generate Example 2

type Integer8x20 is array (0 to 19) of integer range 0 to 255;

type Integer9x20 is array (0 to 19) of integer range 0 to 511;

For Generate Example 2

type Integer8x20 is array (0 to 19) of integer range 0 to 255;

type Integer9x20 is array (0 to 19) of integer range 0 to 511;

Signal Signal1 : Integer8x20;

For Generate Example 2

type Integer8x20 is array (0 to 19) of integer range 0 to 255;

type Integer9x20 is array (0 to 19) of integer range 0 to 511;

Signal Signal1 : Integer8x20;

Signal Signal2 : Integer8x20;

For Generate Example 2

type Integer8x20 is array (0 to 19) of integer range 0 to 255;

type Integer9x20 is array (0 to 19) of integer range 0 to 511;

Signal Signal1 : Integer8x20;

Signal Signal2 : Integer8x20;

Signal Sum : Integer9x20;

If Generate

- Generates hardware IF given condition is met.
- Condition must evaluate to a constant
- Cannot use signals or variables in condition
- Can test for multiple conditions.

If Generate Syntax

```
Label : if condition1 generate
-- Hardware to generate on condition 1.
elseif condition2 generate
-- Hardware to generate on condition 2.
else generate
-- Hardware to generate if all conditions false.
end generate;
```

If Generate Example

```
Example : if ASSIGN_TO_Y generate  
    Y <= X;  
else generate  
    Z <= X;  
end generate;
```

If Generate Example

Example : **if** ENABLE_REGISTER **generate**

Reg : **process** (clk)

begin

if rising_edge(clk) **then**

Y <= X;

end if;

end process;

else generate

Y <= X;

end generate;

This section of code will be implemented if ENABLE_REGISTER is TRUE.

This section of code will be implemented if ENABLE_REGISTER is false.

Concurrent VHDL Statements

- Process Block
- Component Instantiation
- Concurrent Signal Assignments (using `<=`)
- Conditional Signal Assignment (When – Else)
- Selected Signal Assignment (With – Select)
- Generate

VHDL Statements

Sequential Statements

- Can only be used inside **Process Blocks**.
- Sequential Assignment
- If statements
- Case statements
- For loops
- Wait

Sequential Statements

- Can only be used inside **Process Blocks**.
- Sequential Assignment
- If statements
- Case statements
- For loops
- Wait

$Y \leq X;$

Sequential Statements

- Can only be used inside **Process Blocks**.
- Sequential Assignment
- If statements
- Case statements
- For loops
- Wait

If Statement - Template

```
if Condition1 then
    -- Code Section 1
elseif Condition2 then
    -- Code Section 2
elseif Condition3 then
    -- Code Section 3
else
    -- Code Section 4
end if;
```

If Statement - Combinational

```
MyProcess : process(Sel, A, B, C, D)
```

```
begin
```

```
  if Sel = "00" then
```

First condition



```
    Out <= A;
```

```
  elsif Sel = "10" then
```

Second condition



```
    Out <= B;
```

```
  elsif Sel = "10" then
```

Third condition



```
    Out <= C;
```


```
  else
```

```
    Out <= D;
```


```
  end if;
```

```
end process;
```


If Statement - Hardware

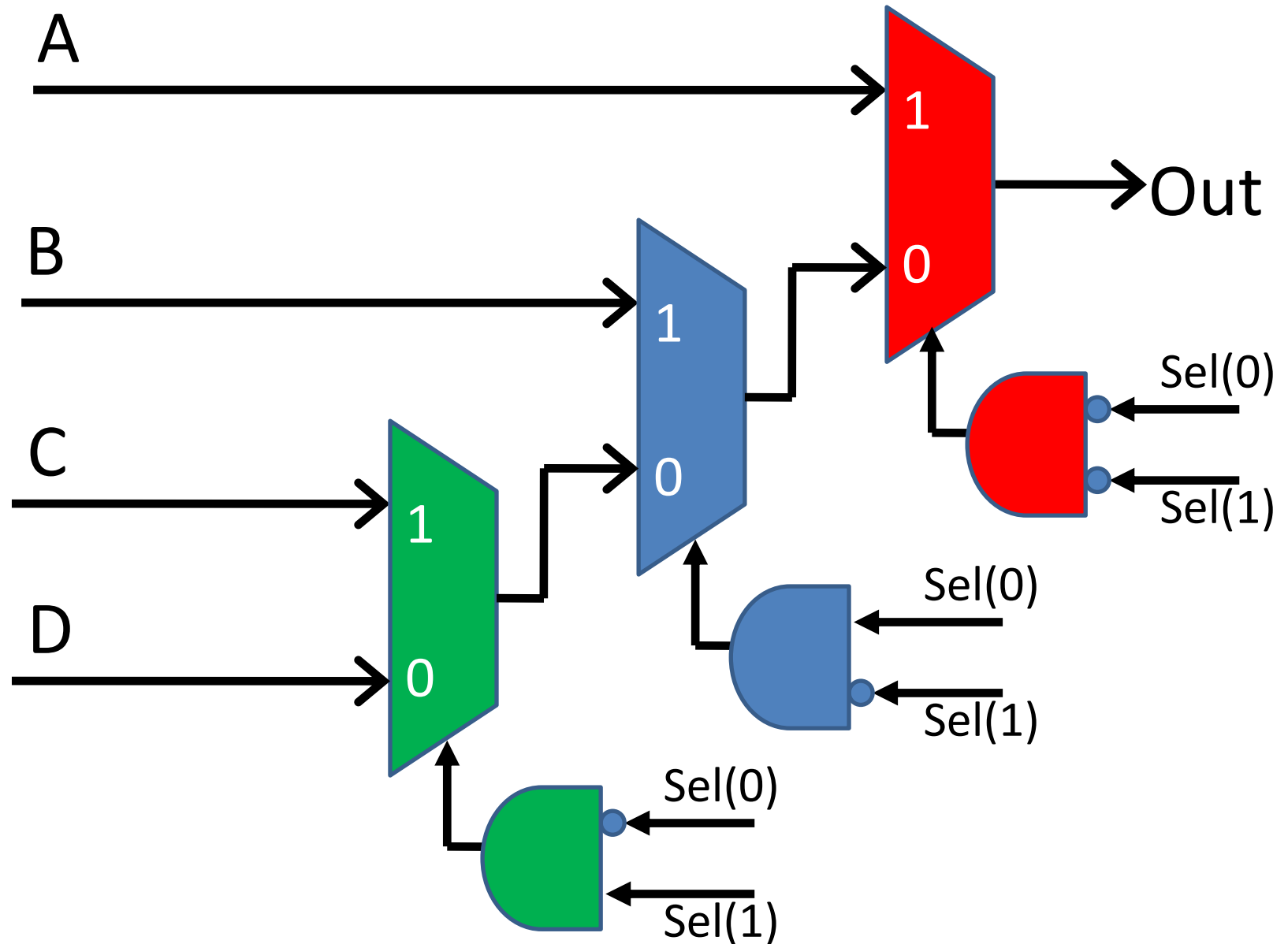


If Statement – 1st Condition

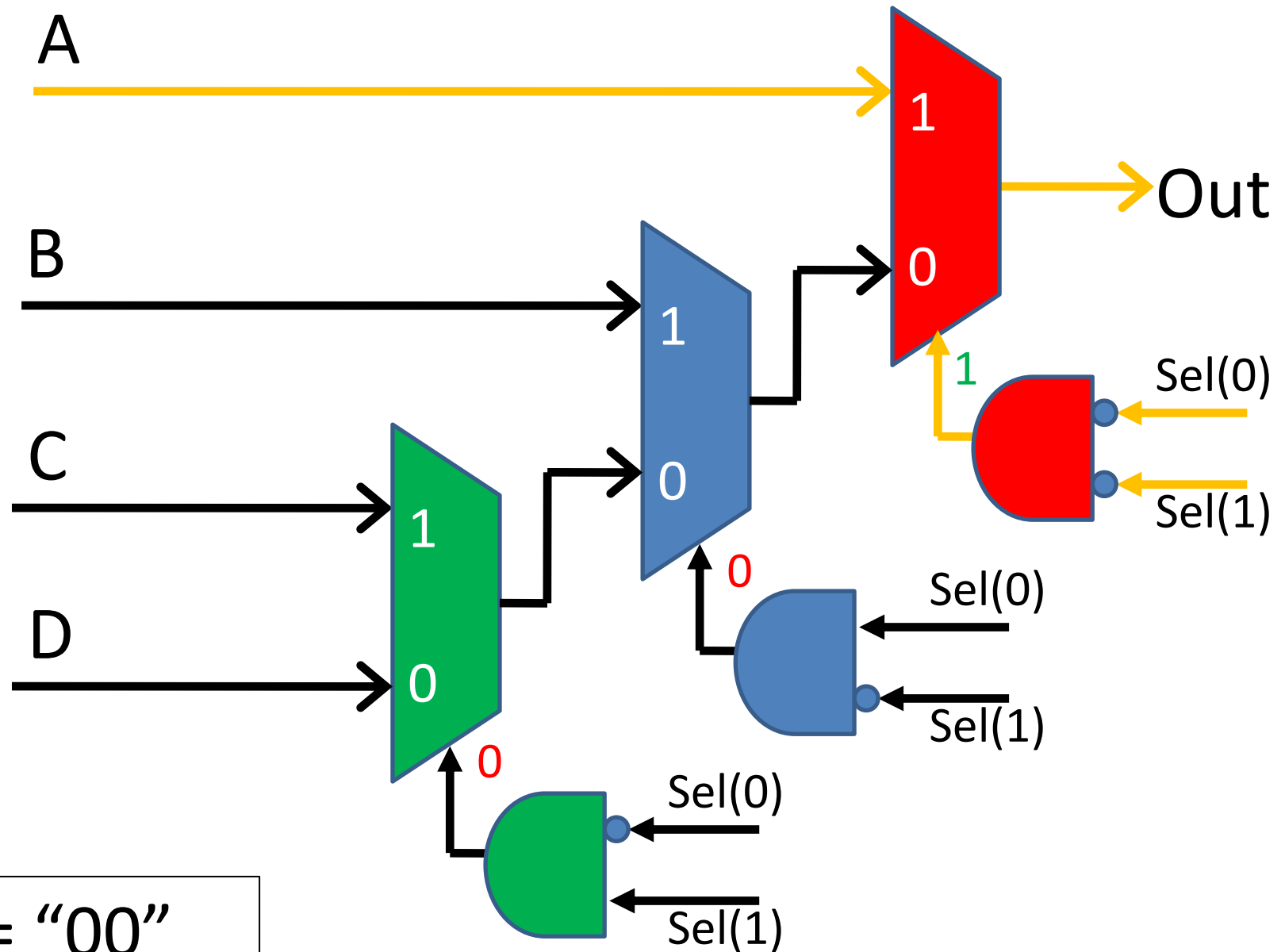

If Statement – 2nd Condition

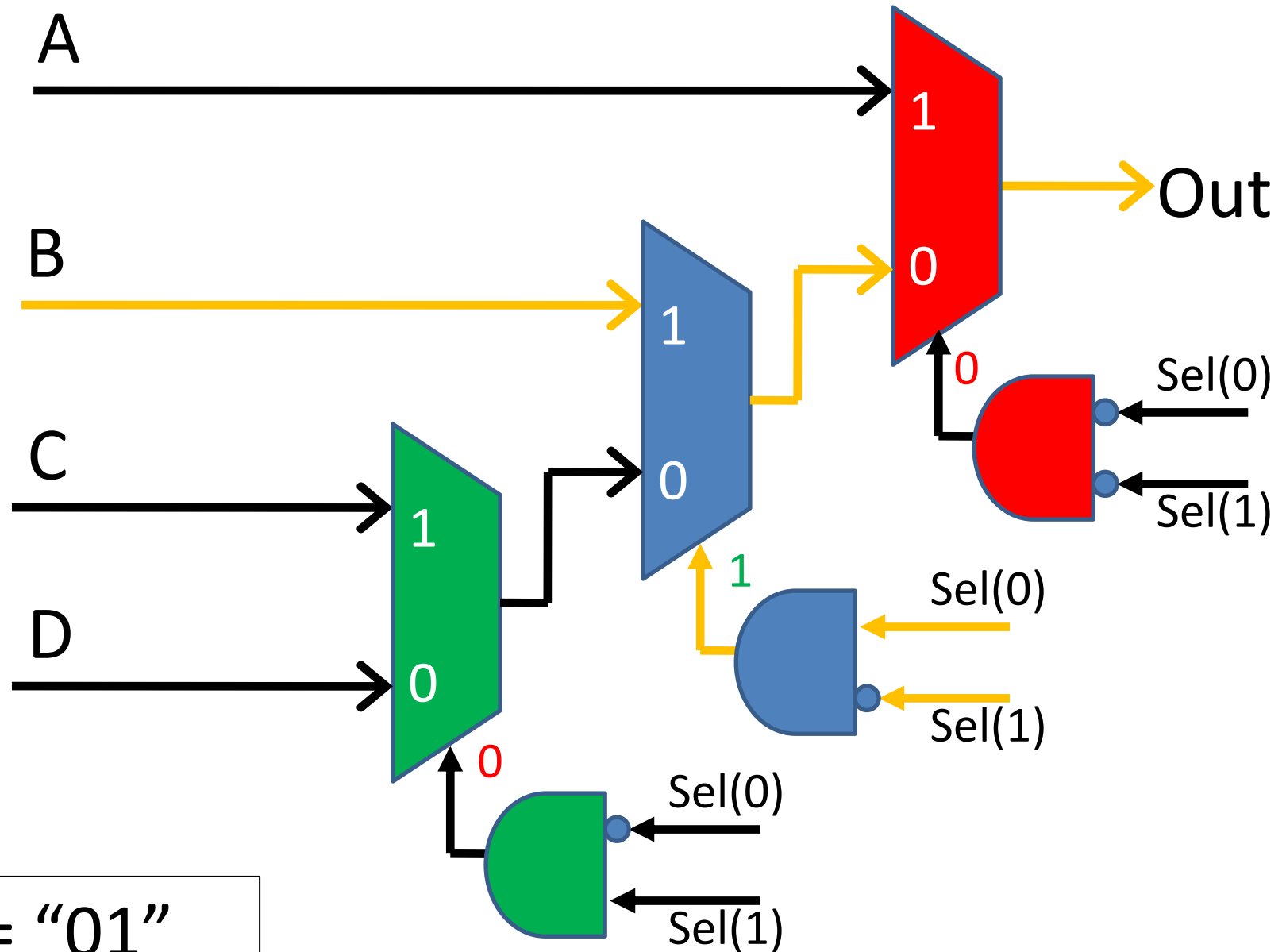


If Statement – 3rd Condition


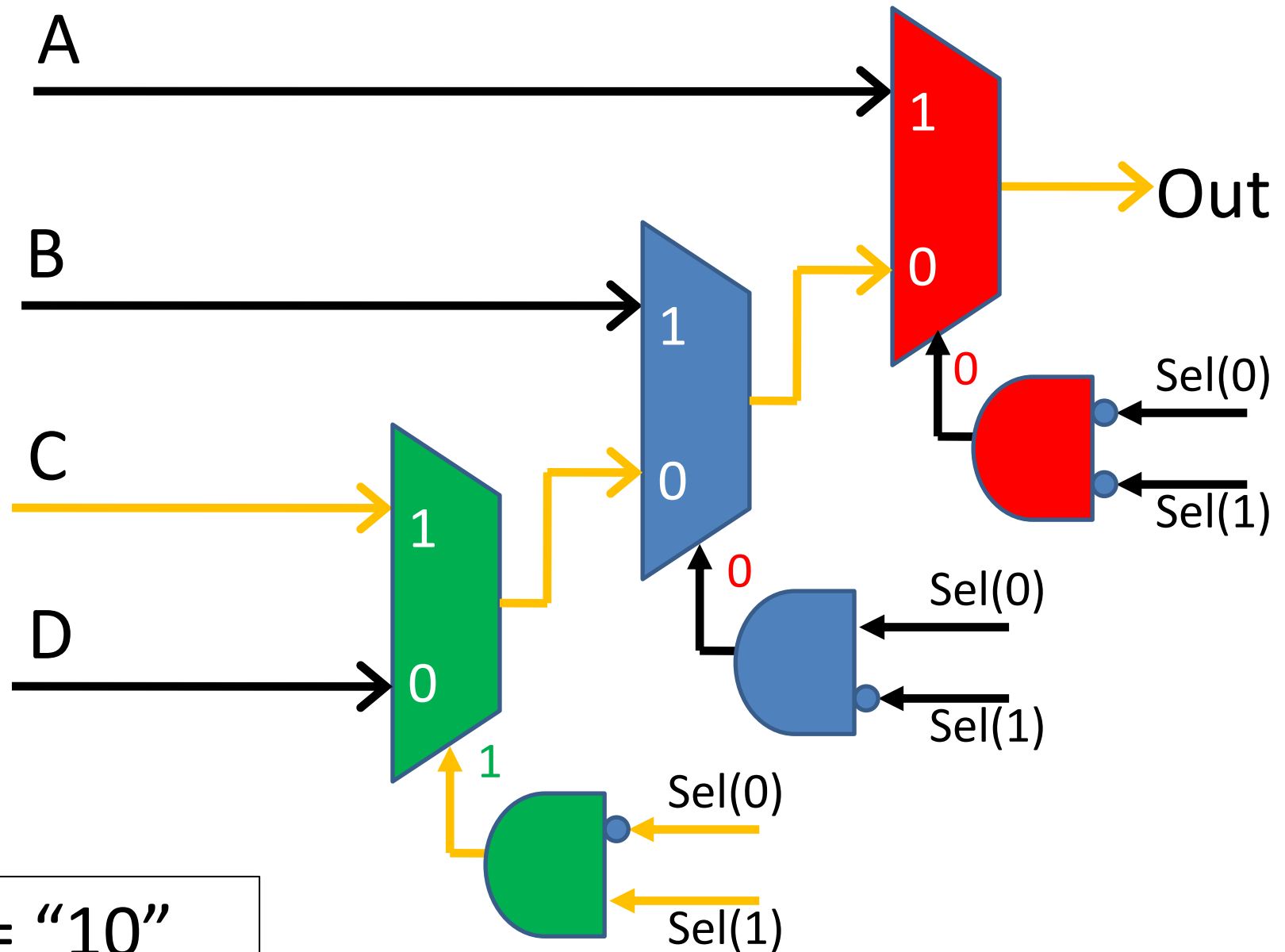


Sel = "10"

If Statement – Default

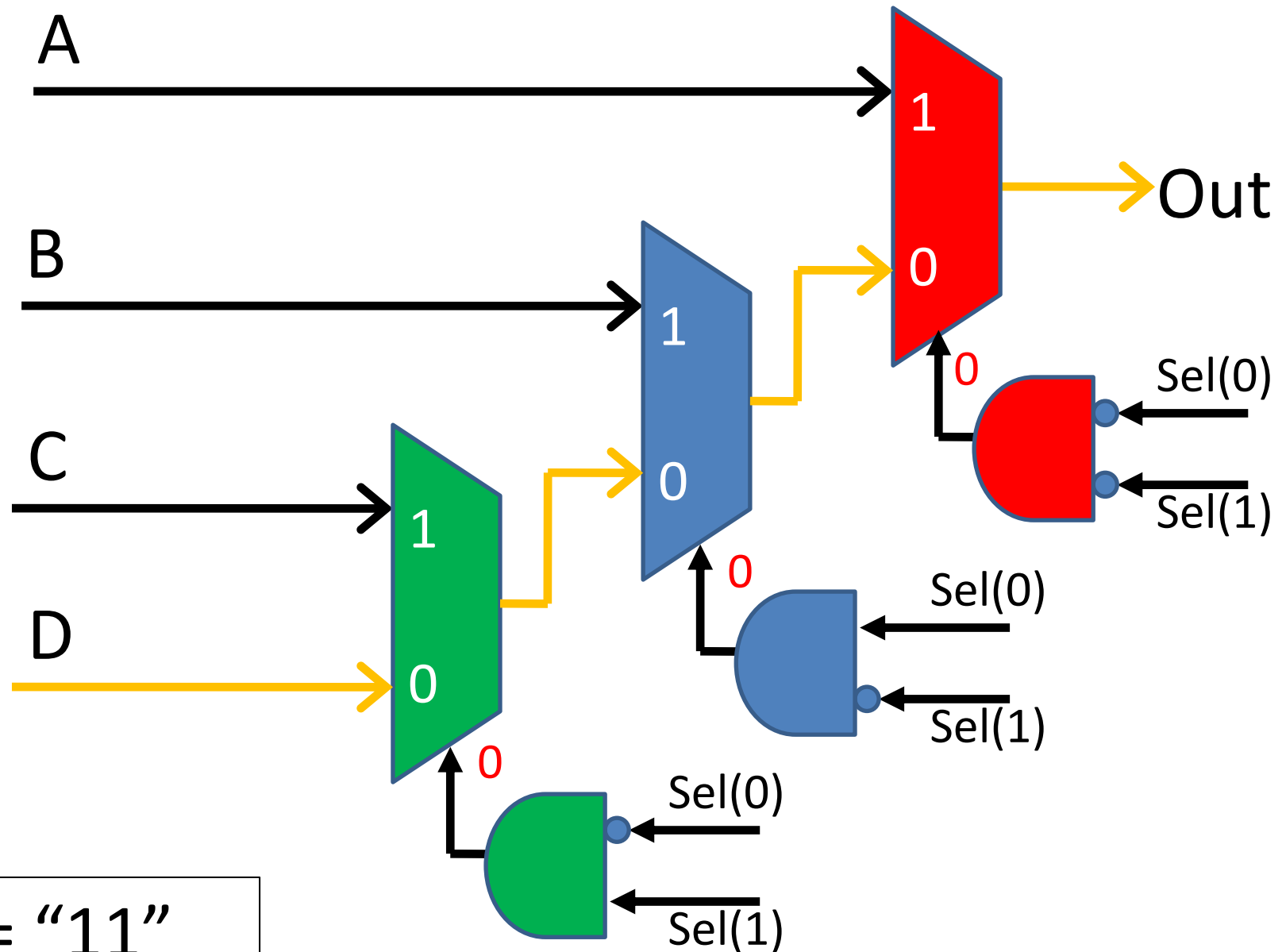

Propagation Delay

  

If Statement – Notes

- The conditions must return a Boolean (true or false) result.
- If statements having more than one condition will create cascaded multiplexers.
- Lowest priority path has to propagate through all multiplexers to get to output.
- This is bad for timing closure.

If Statement – Notes

- The conditions must return a Boolean (true or false) result.
- If statements having more than one condition will create cascaded multiplexers.
- Lowest priority path has to propagate through all multiplexers to get to output.
- This is bad for timing closure.

Case Statement - Template

```
case (Expression) is
  when Choice1 =>
    -- Code Section 1
  when Choice2 =>
    -- Code Section 2
  when others =>
    -- Code Section 3
end case;
```


Case Statement - Template

```
case (Expression) is
    when Choice1 =>
        -- Code Section 1
    when Choice2 =>
        -- Code Section 2
    when others =>
        -- Code Section 3
end case;
```

Case Statement - Template

```
case (Expression) is
  when Choice1 =>
    -- Code Section 1
  when Choice2 =>
    -- Code Section 2
  when others =>
    -- Code Section 3
end case;
```


Case Statement – Combinational Process

```
MyProcess : process(Sel, A, B, C, D)
begin
    case (Sel) is
        when "00" => Out <= A;
        when "01" => Out <= B;
        when "10" => Out <= C;
        when others => Out <= D;
    end case;
end process;
```

Case Statement – Combinational Process

```
MyProcess : process(Sel, A, B, C, D)
begin
    case (Sel) is
        when "00" => Out <= A;
        when "01" => Out <= B;
        when "10" => Out <= C;
        when others => Out <= D;
    end case;
end process;
```


Case Statement – Combinational Process

 

Case Statement – Registered Process

```
MyProcess : process(Reset, Clock)
Begin
    if Reset = '1' then
        Out <= '0';
    elsif rising_edge(Clock) then
        case (Sel) is
            when "00" => Out <= A;
            when "01" => Out <= B;
            when "10" => Out <= C;
            when others => Out <= D;
        end case;
    end if;
end process;
```

Case Statement – Registered Process

 

Case Statement Notes


```
when "00" => Out <= A;
```

```
when "01" => Out <= A;
```


Case Statement Notes

```
when "00" => Out <= A;
```

```
when "01" => Out <= A;
```

 

```
when "00" | "01" => Out <= A;
```

Case Statement Notes

```
when 0 => Out <= A;
```


```
when 1 => Out <= A;
```

```
when 2 => Out <= A;
```

```
when 3 => Out <= B;
```

Case Statement Notes
 
```
when 0 => Out <= A;  
when 1 => Out <= A;  
when 2 => Out <= A;  
when 3 => Out <= B;
```



```
when 0 to 2 => Out <= A;  
when 3 => Out <= B;
```

Case Statement Notes

```
when "00" | "01" => Out <= A;
```

```
when "01" | "10" => Out <= B;
```

Test conditions cannot overlap!!

```
when Sig1 => Out <= A;
```

Test conditions must be constants!

For Loop - Template

```
for LoopVariableName in Range loop  
    -- Code Section That Needs Repeating  
end loop;
```

For Loop - Template

```
for LoopVariableName in Range loop  
    -- Code Section That Needs Repeating  
end loop;
```

For Loop - Template

```
for LoopVariableName in Range loop  
    -- Code Section That Needs Repeating  
end loop;
```


Range = 0 **to** 7

For Loop – Combinational Process

```
MyProcess : process(A, B)
Begin
    for i in 0 to 2 loop
        Y(i) <= A(2-i) and B(i);
    end loop;
end process;
```


For Loop – Combinational Process

 
```
MyProcess : process(A, B)
Begin
    for i in 0 to 2 loop
        Y(i) <= A(2-i) and B(i);
    end loop;
end process;
```



```
MyProcess : process(A, B)
Begin
    Y(0) <= A(2) and B(0);
    Y(1) <= A(1) and B(1);
    Y(2) <= A(0) and B(2);
end process;
```

For Loop – Combinational Process

 
```
MyProcess : process(A, B)
Begin
    for i in 0 to 2 loop
        Y(i) <= A(2-i) and B(i);
    end loop;
end process;
```



```
MyProcess : process(A, B)
Begin
    Y(0) <= A(2) and B(0);
    Y(1) <= A(1) and B(1);
    Y(2) <= A(0) and B(2);
end process;
```




For Loop – Combinational Process
 
```
MyProcess : process(A, B)
Begin
    for i in 0 to 2 loop
        Y(i) <= A(2-i) and B(i);
    end loop;
end process;
```



```
MyProcess : process(A, B)
Begin
    Y(0) <= A(2) and B(0);
    Y(1) <= A(1) and B(1);
    Y(2) <= A(0) and B(2);
end process;
```

For Loop – Combinational Process

   

For Loop – Registered Process

```
MyProcess : process(Reset, Clock)
```

```
Begin
```

```
    if Reset = '1' then
```

```
        Y <= "000";
```

```
    elsif rising_edge(Clock) then
```

```
        for i in 0 to 2 loop
```




```
            Y(i) <= A(2-i) and B(i);
```

```
        end loop;
```

```
    end if;
```

```
end process;
```

For Loop – Registered Process

   

For Loop Notes

```
signal A : std_logic_vector(2 downto 0);  
signal B : std_logic_vector(2 downto 0);  
signal Y : std_logic_vector(2 downto 0);  
for i in 0 to 2 loop  
    Y(i) <= A(2-i) and B(i);  
end loop;
```

For Loop Notes

```
signal A : std_logic_vector(2 downto 0);  
signal B : std_logic_vector(2 downto 0);  
signal Y : std_logic_vector(2 downto 0);
```

```
for i in 0 to 2 loop
```

```
    Y(i) <= A(2-i) and B(i);
```

```
end loop;
```

↑
Y'left

↑
Y'right

```
for i in Y'right to Y'left loop
```

```
    Y(i) <= A(2-i) and B(i);
```

```
end loop;
```


For Loop Notes

```
signal A : std_logic_vector(2 downto 0);  
signal B : std_logic_vector(2 downto 0);  
signal Y : std_logic_vector(2 downto 0);  
for i in 0 to 2 loop  
    Y(i) <= A(2-i) and B(i);  
end loop;
```

```
for i in Y'right to Y'left loop  
    Y(i) <= A(2-i) and B(i);  
end loop;
```

```
for i in Y'range loop  
    Y(i) <= A(2-i) and B(i);  
end loop;
```

Y'range = 2 downto 0.

The loop variable, i, counts down from 2 to 0.

For Loop Notes

```
-- A is a std_logic_vector of length 8
```

```
for i in 0 to 7 loop
```

```
    A(i) <= '1';
```

```
    if i = 3 then
```

```
        exit;
```

```
    end if;
```

```
end loop;
```

Can use “exit” to immediately exit the loop.

For Loop Notes

-- A is a std_logic_vector of length 8

for i in 0 to 7 loop

A(i) <= '1';

if i = 3 then

exit;

end if;

end loop;

Can use “exit” to immediately exit the loop.

for i in 0 to 7 loop

A(i) <= '1';

exit when i = 3;

end loop;

For Loop Notes

-- A is a std_logic_vector of length 8

for i in 0 to 7 loop

A(i) <= '1';

i = 2;

end loop;

Cannot change loop variable.

Wait Statement

- NOT Synthesisable!
- Used only in Test-Benches (or Models)
- Used to pause a simulation or model.
- Process must not have a sensitivity list
- Allows us to pause the simulation :
 - for a fixed period of time
 - until some event occurs

Wait Statement

- NOT Synthesisable!
- Used only in Test-Benches (or Models)
- Used to pause a simulation or model.
- Process must not have a sensitivity list
- Allows us to pause the simulation :
 - for a fixed period of time
 - until some event occurs

Wait

```
Test : process  
begin  
    Y <= X;  
    wait;  
    Z <= Y;  
end process;
```

Wait for

Test : process

begin

Y <= X;

wait for 100ns;

Z <= Y;

end process;

Clock Signal Using Wait for

Clk_Generator: process

begin

 Clock <= '0';

 wait for 10 ns;

 Clock <= '1';

 wait for 10 ns;

end process;

Wait On

Test : process

begin

Y \leq X;

wait on A;

Z \leq Y;

end process;

Wait On

Test : process

begin

$Y \leq X;$

wait on A;

$Z \leq Y;$

end process;

Wait Until

Test : process

begin

Y <= X;

wait until A = '0';

Z <= Y;

end process;

Wait Until

Test : process

begin

Y <= X;

wait until rising_edge(A);

Z <= Y;

end process;

Summary

- Can only be used inside process block
- If statements
- Case statements
- For loops
- Wait statements
- Hardware realisation

Summary

- Can only be used inside process block
- If statements
- Case statements
- For loops
- Wait statements
- Hardware realisation


Signal Assignments Inside The Process Block

Part I

Signal Assignments Inside The Process Block

Part I

Combinational Process - Hardware

 

Code For Example 1

```
TestProcess1 : process ( $X_1$ ,  $X_2$ ,  $X_3$ )
```

```
Begin
```

```
end process;
```

Code For Example 1

```
TestProcess1 : process ( $X_1$ ,  $X_2$ ,  $X_3$ )
```

```
Begin
```

```
    if  $X_1 = '1'$  then
```

```
    else
```

```
    end if;
```

```
end process;
```

Code For Example 1

```
TestProcess1 : process (X1, X2, X3)
```

```
Begin
```

```
    if X1 = '1' then
```

```
        Y <= '0';
```

```
    else
```

```
        end if;
```

```
end process;
```

Code For Example 1

```
TestProcess1 : process (X1, X2, X3)
```

```
Begin
```

```
    if X1 = '1' then
```

```
        Y <= '0';
```


```
    else
```

```
        Y <= X2 and X3;
```


```
    end if;
```

```
end process;
```


Hardware For Example 1

 

Hardware For Example 1

 

Hardware For Example 1

 

Code For Example 2

TestProcess2A : process (X_1 , X_2 , X_3)

Begin

$A \leq X_1$ and X_2 ;

$B \leq A$ and X_3 ;

end process;

TestProcess2B : process (X_1 , X_2 , X_3)


Begin

$B \leq A$ and X_3 ;


$A \leq X_1$ and X_2 ;

end process;


Hardware For TestProcess2A

 


Hardware For TestProcess2A

 


Hardware For TestProcess2B

 

Hardware For TestProcess2B

 

Hardware For TestProcess2B

 

Code For Example 3

TestProcess3A : process (X_1 , X_2)

Begin

$Y \leq X_1$ or X_2 ;

$Y \leq X_1$ and X_2 ;

end process;

TestProcess3B : process (X_1 , X_2)

Begin

$Y \leq X_1$ and X_2 ;

$Y \leq X_1$ or X_2 ;

end process;

Code For Example 3

TestProcess3A : process (X_1 , X_2)

Begin

$Y \leq X_1$ or X_2 ;

$Y \leq X_1$ and X_2 ;

end process;

TestProcess3B : process (X_1 , X_2)

Begin

$Y \leq X_1$ and X_2 ;

$Y \leq X_1$ or X_2 ;

end process;

Code For Example 3

TestProcess3A : process (X_1 , X_2)

Begin

$Y \leq X_1$ or X_2 ; -- this is ignored !

$Y \leq X_1$ and X_2 ; -- this is implemented.

end process;

TestProcess3B : process (X_1 , X_2)

Begin

$Y \leq X_1$ and X_2 ;

$Y \leq X_1$ or X_2 ;

end process;

Code For Example 3

TestProcess3A : process (X_1 , X_2)

Begin

$Y \leq X_1$ or X_2 ; -- this is ignored !

$Y \leq X_1$ and X_2 ; -- this is implemented.

end process;

TestProcess3B : process (X_1 , X_2)

Begin

$Y \leq X_1$ and X_2 ; -- this is ignored !

$Y \leq X_1$ or X_2 ; -- this is implemented.

end process;

Code For Example 4

```
TestProcess4 : process (X1, X2, X3)
```

```
Begin
```

```
    if X1 = '1' then
```

```
        Y <= X2 and X3;
```

```
    end if;
```

```
end process;
```

Code For Example 4

```
TestProcess4 : process (X1, X2, X3)
```


```
Begin
```

```
    if X1 = '1' then
```


```
        Y <= X2 and X3;
```


```
    end if;
```

```
end process;
```

 


Latch

 

 

Latch

 

More On Latches

- Latches can be created in **Combinational** processes.
- Latches are created when the state of the output is **not** defined in all paths through the process.
- A process can have **multiple paths** due to **branch statements** (if statement, case statement).
- Make sure your outputs are assigned in **all** possible branches of the code (In combinational processes)

More On Latches

- Latches can be created in **Combinational** processes.
- Latches are created when the state of the output is **not** defined in all paths through the process.
- A process can have **multiple paths** due to **branch statements** (if statement, case statement).
- Make sure your outputs are assigned in **all** possible branches of the code (In combinational processes)

Avoiding Latches

TestProcess : process (X_1 , X_2 , X_3)

Begin

if $X_1 = '1'$ then

$Y \leq X_2$ and X_3 ;

else

$Y \leq '0'$;

end if;

end process;

Avoiding Latches

TestProcess : process (X_1 , X_2 , X_3)

Begin

if $X_1 = '1'$ then

$Y \leq X_2$ and X_3 ;

else

$Y \leq '0'$;

end if;

end process;

TestProcess : process (Reset, Clock)

Begin

if Reset = '1' then

Y <= '0';

elsif rising_edge(Clock) then


if X_1 = '1' then


Y <= X_2 and X_3 ;


end if;


end if;

end process;

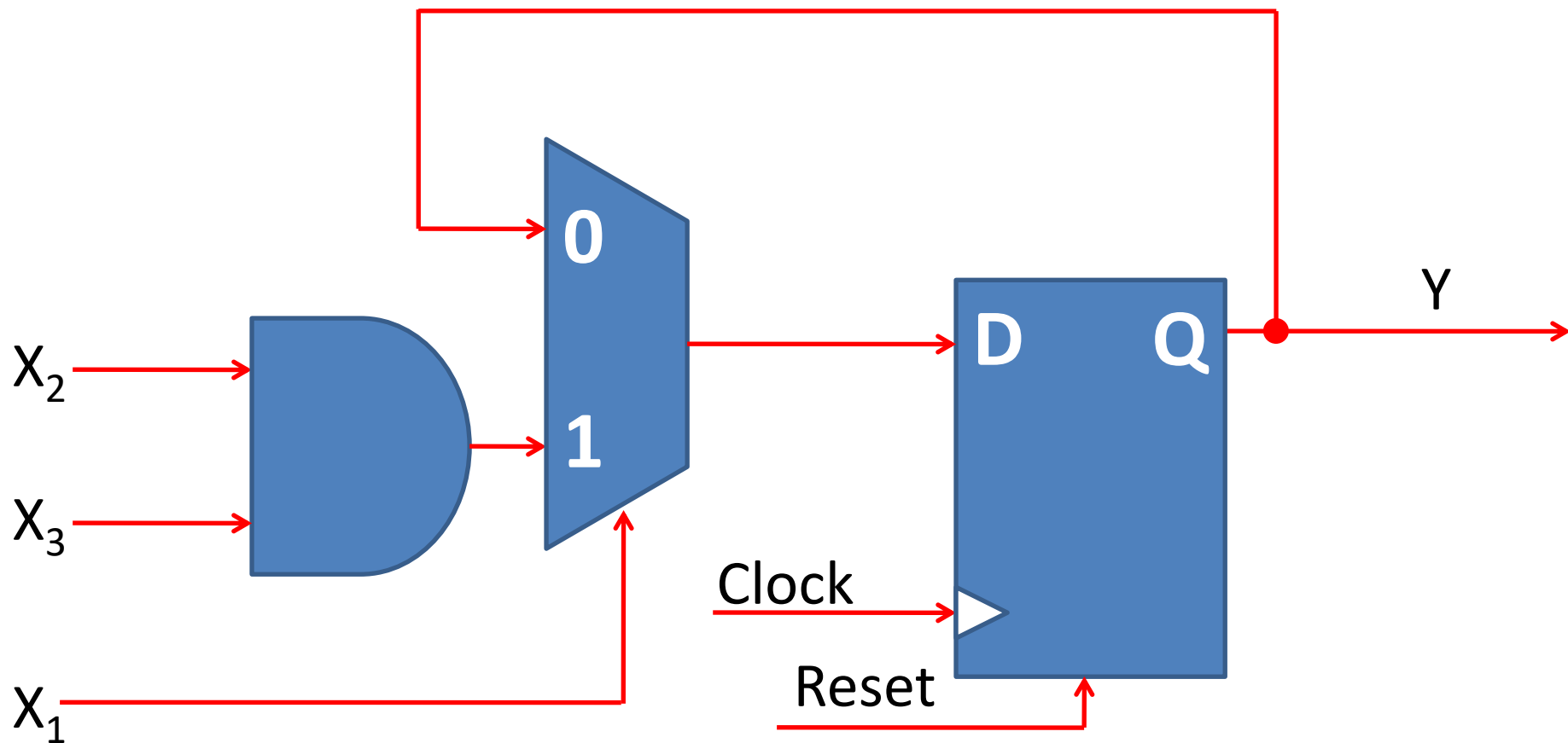

 

 

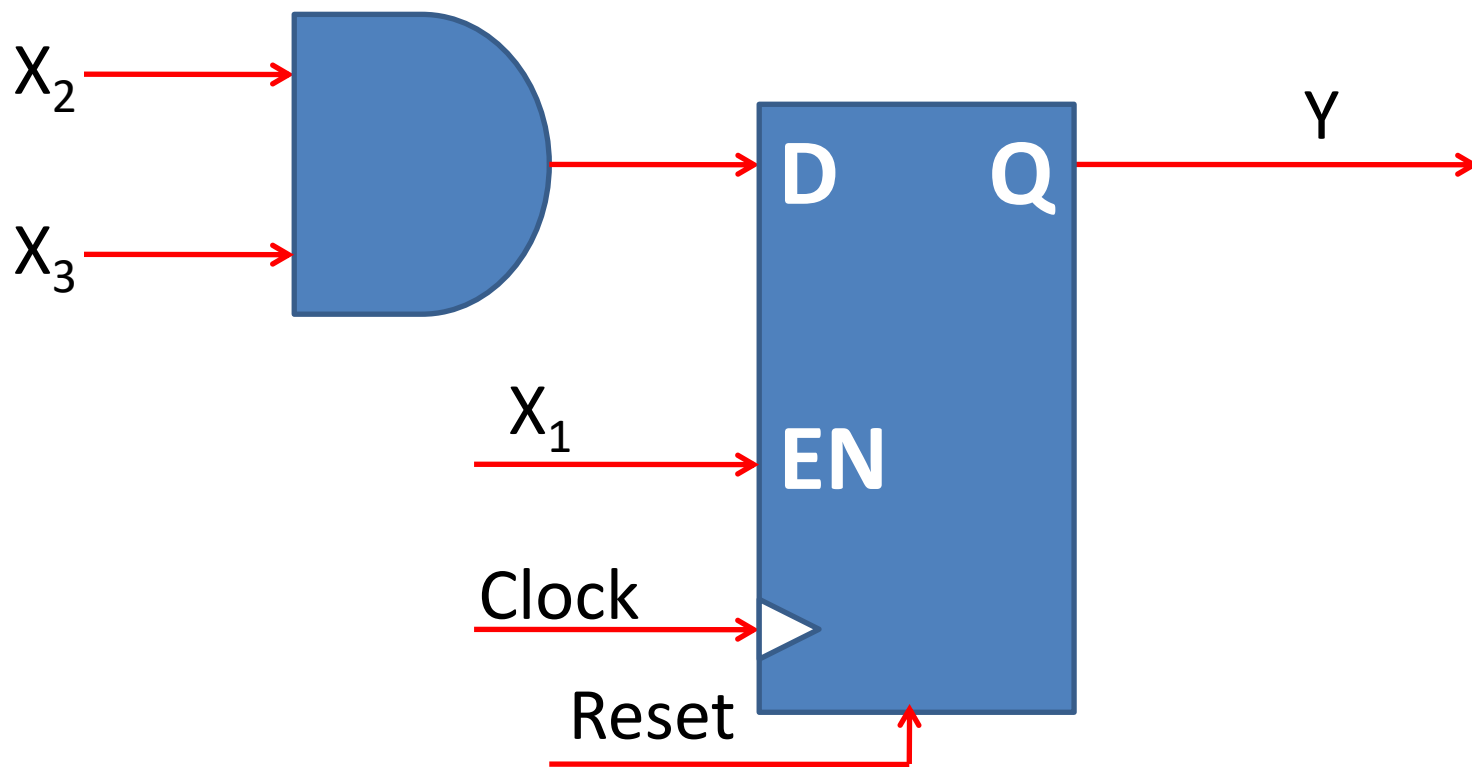

Signal Assignments Inside The Process Block

Part II

TestProcess : process(Reset, Clock)

begin

end process;

```
TestProcess : process(Reset, Clock)
```

```
begin
```

```
    if Reset = '1' then
```

```
        Y <= '0';
```

```
end process;
```

TestProcess : process(Reset, Clock)

begin

if Reset = '1' then

Y <= '0';

elsif rising_edge(Clock) then

Y <= Function(X_1 , X_2 , $X_3, \dots X_N$);

end if;

end process;

TestProcess : **process**(Reset, Clock)

begin

if Reset = '1' **then**


Y <= '0';

elsif rising_edge(Clock) **then**

Y <= Function(X_1 , X_2 , $X_3, \dots X_N$);

end if;

end process;

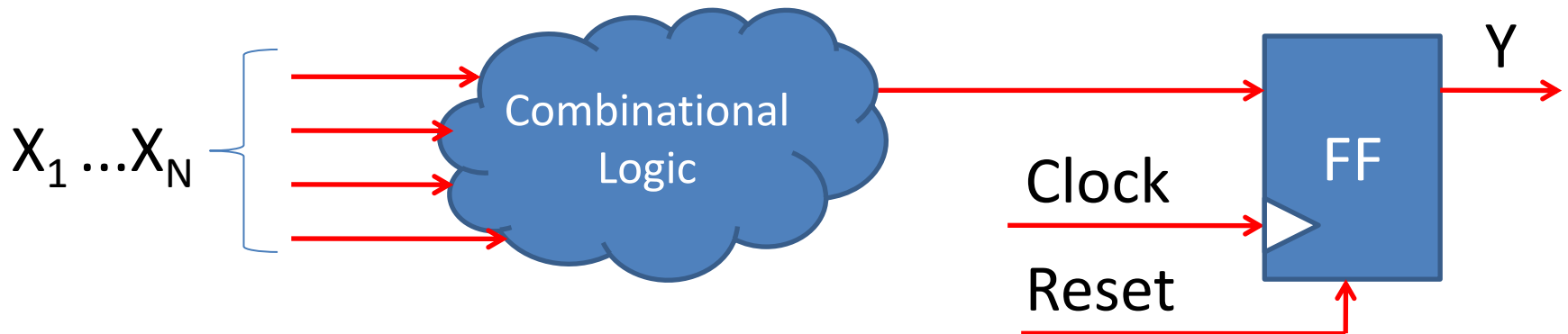

TestProcess : **process**(Reset, Clock)

begin

if Reset = '1' **then**


Y <= '0';

elsif rising_edge(Clock) **then**

Y <= Function(X_1 , X_2 , $X_3, \dots X_N$);

end if;

end process;

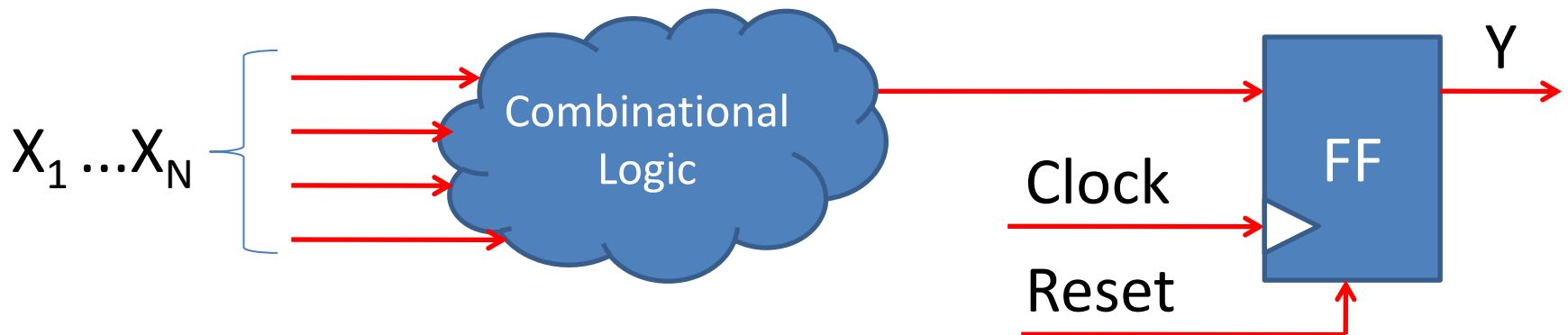

TestProcess : **process**(Reset, Clock)

begin

if Reset = '1' **then**


Y <= '0';

elsif rising_edge(Clock) **then**

Y <= X₁ or X₂;

end if;

end process;

 

TestProcess : **process**(Reset, Clock)

begin

if Reset = '1' **then**


Y <= '0';

elsif rising_edge(Clock) **then**


Y <= X₁ or X₂;

end if;



end process;

 


 

```
TestProcess : process(Reset, Clock)
begin
    if Reset = '1' then
        Y <= '0';
    elsif rising_edge(Clock) then
        Y <= X1 or X2;
    end if;
end process;
```





Timing Of Signal Y

    



Timing Of Signal Y



Timing Of Signal Y

  

Timing Of Signal Y

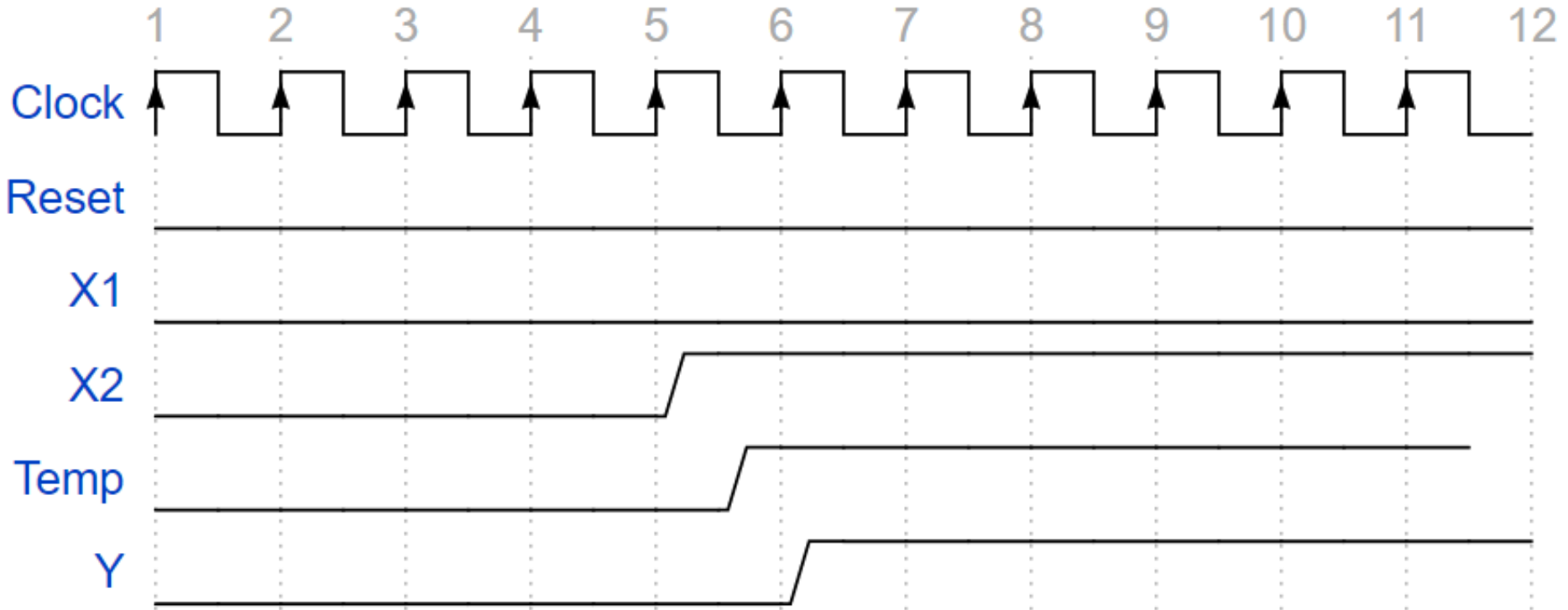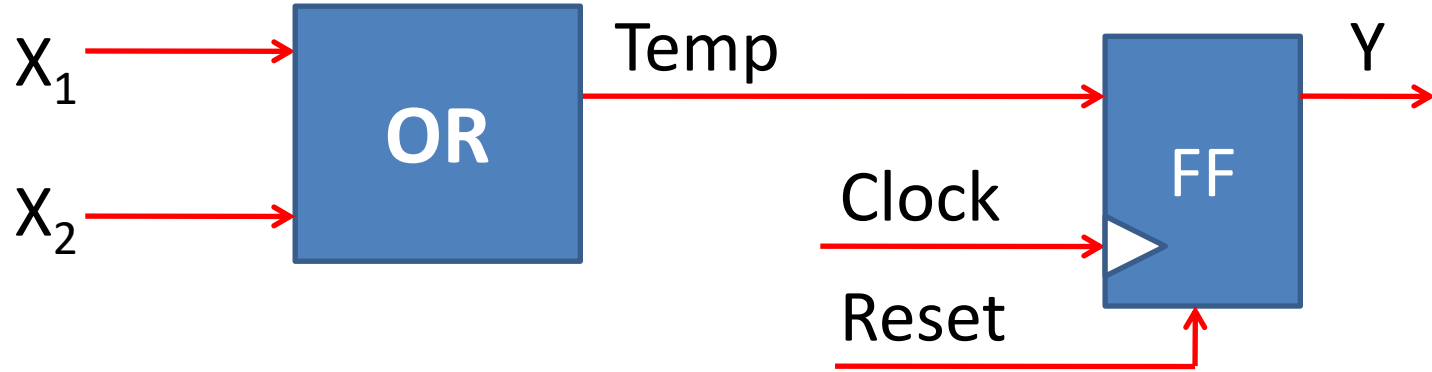


```
TestProcess : process(Reset, Clock)
begin
    if Reset = '1' then
        X1 <= '0';
        X2 <= '0';
        X3 <= '0';
    elsif rising_edge(Clock) then
        X1 <= '1';
        X2 <= X1;
        X3 <= X2;
    end if;
end process;
```


```
TestProcess : process(Reset, Clock)
begin
    if Reset = '1' then
         $X_1 \leq '0';$ 
         $X_2 \leq '0';$ 
         $X_3 \leq '0';$ 
    elsif rising_edge(Clock) then
         $X_1 \leq '1';$ 
         $X_2 \leq X_1;$ 
         $X_3 \leq X_2;$ 
    end if;
end process;
```



```
TestProcess : process(Reset, Clock)
begin
    if Reset = '1' then
        X1 <= '0';
        X2 <= '0';
        X3 <= '0';
    elsif rising_edge(Clock) then
        X1 <= '1';
        X2 <= X1;
        X3 <= X2;
    end if;
end process;
```






 
```
TestProcess : process(Reset, Clock)
begin
    if Reset = '1' then
        X1 <= '0';
        X2 <= '0';
        X3 <= '0';
    elsif rising_edge(Clock) then
        X1 <= '1';
        X2 <= X1;
        X3 <= X2;
    end if;
end process;
```






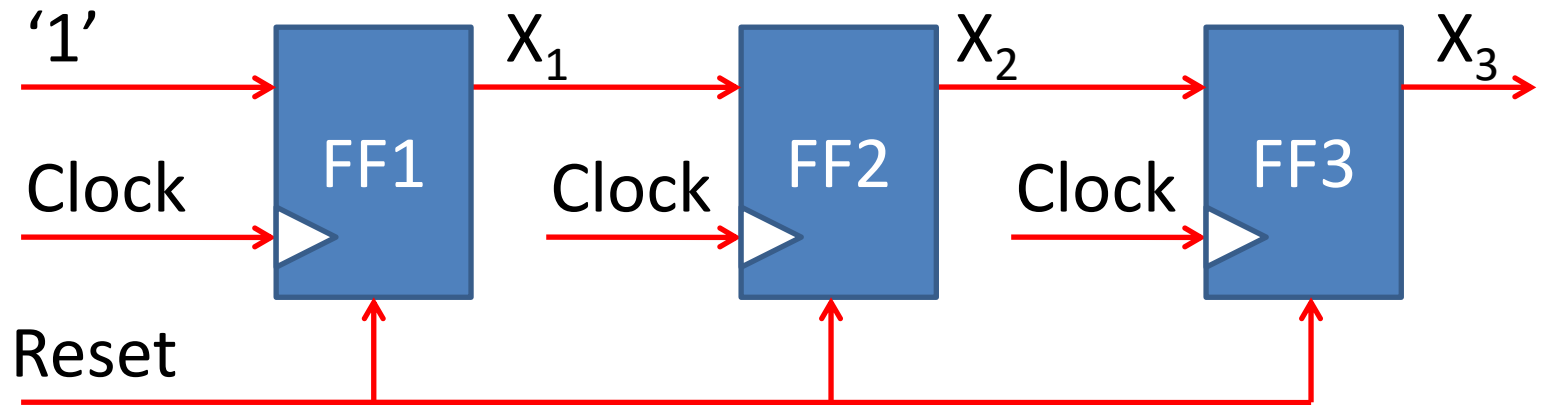


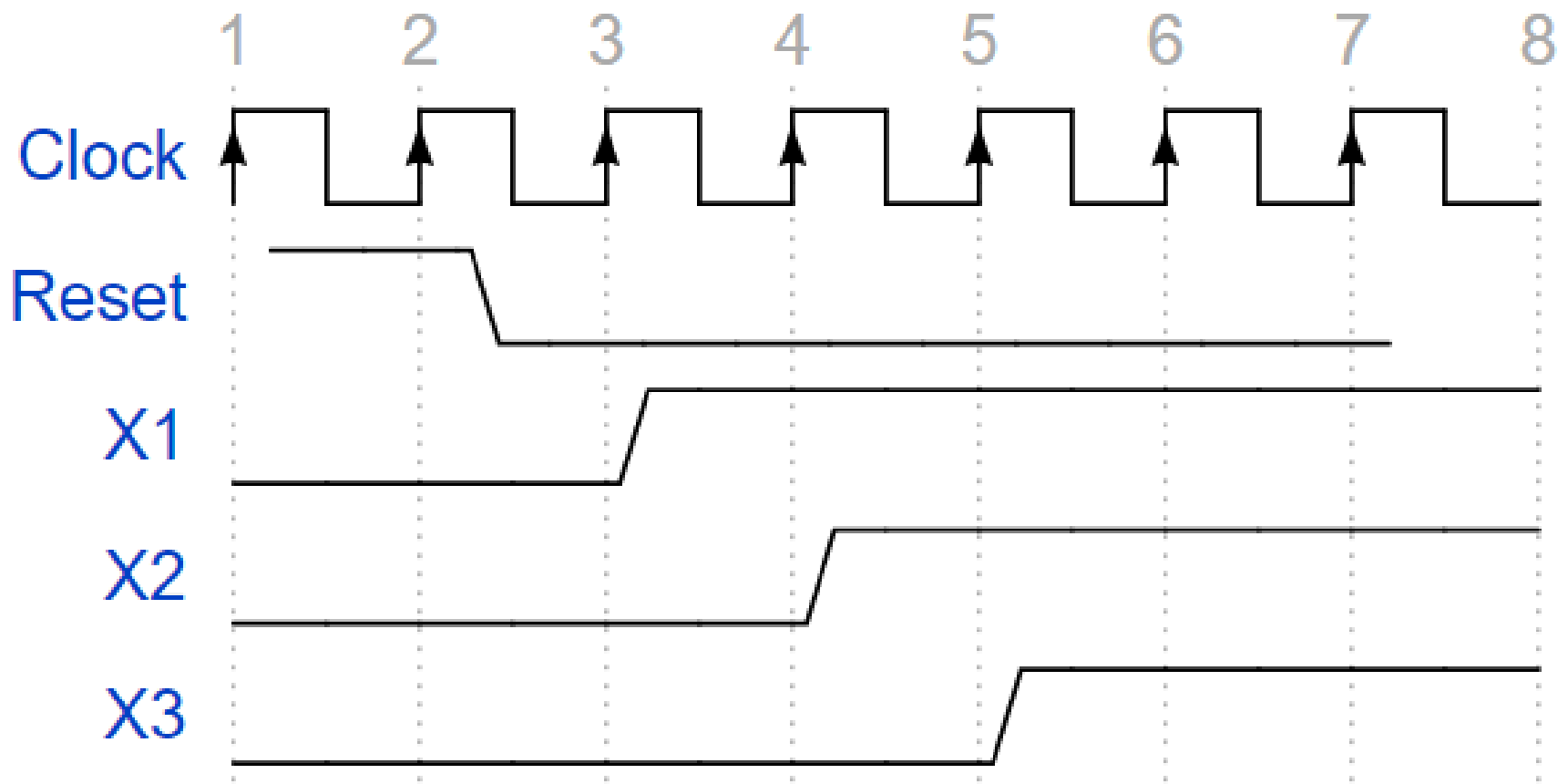 

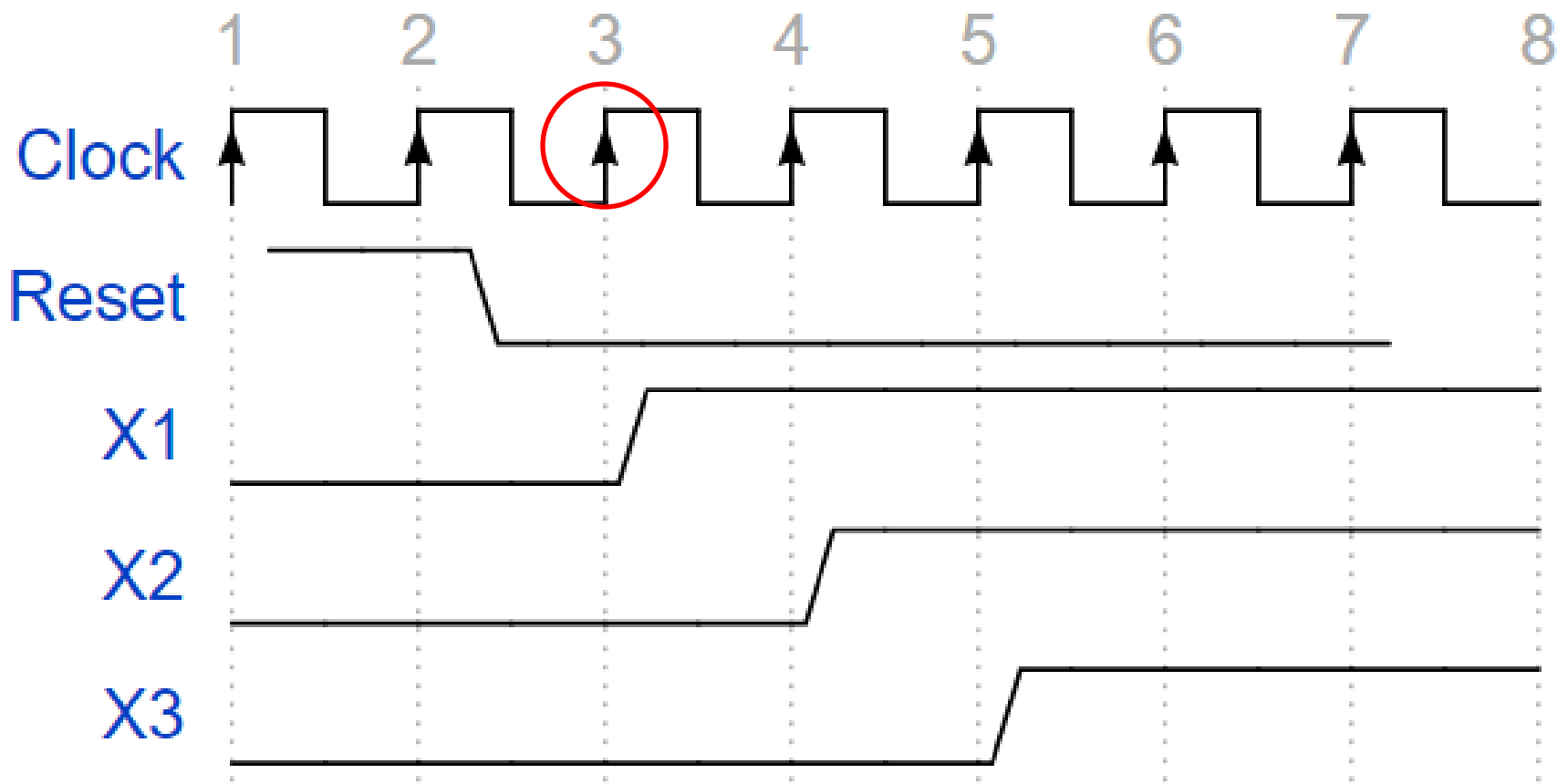 

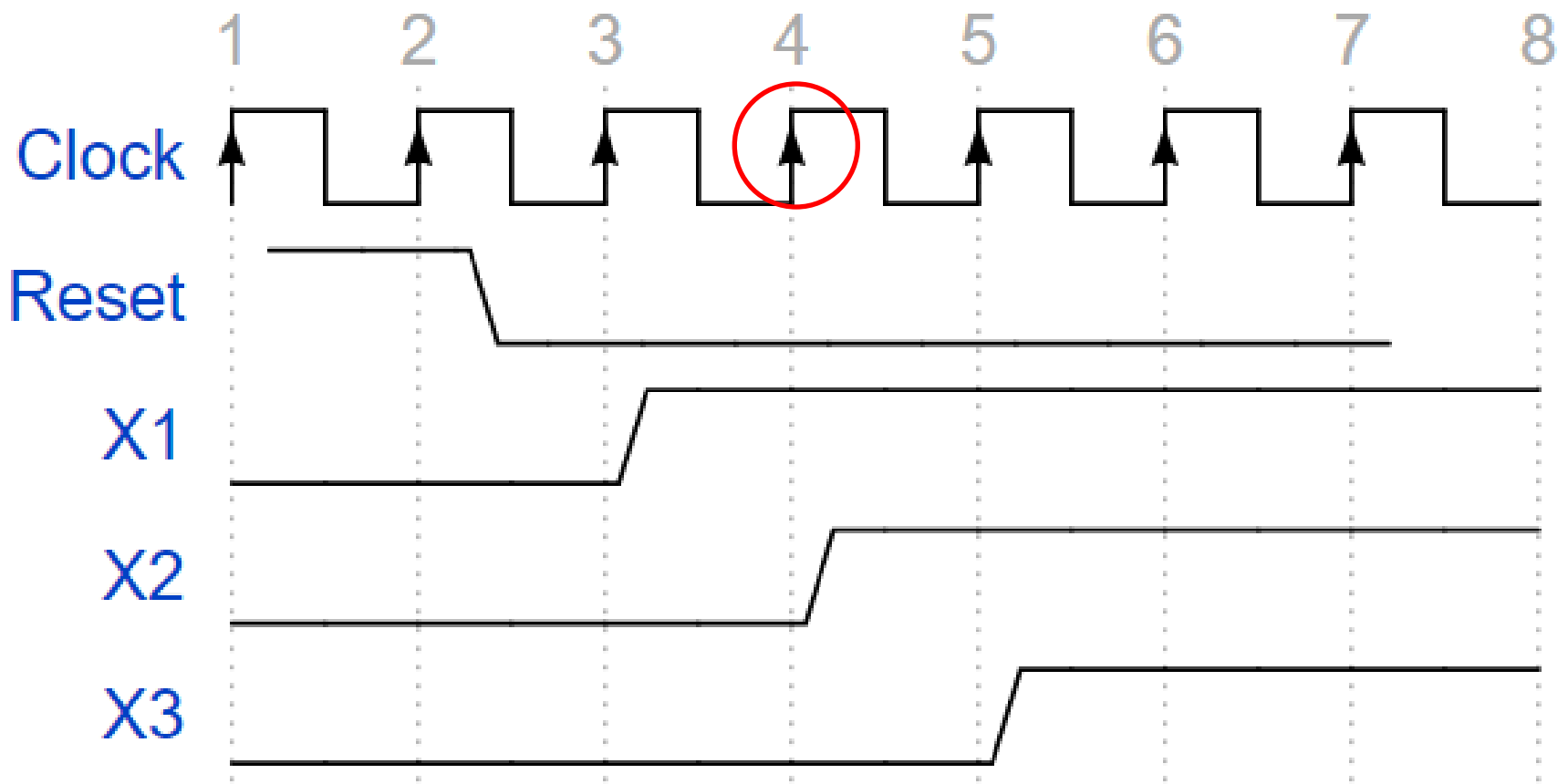 

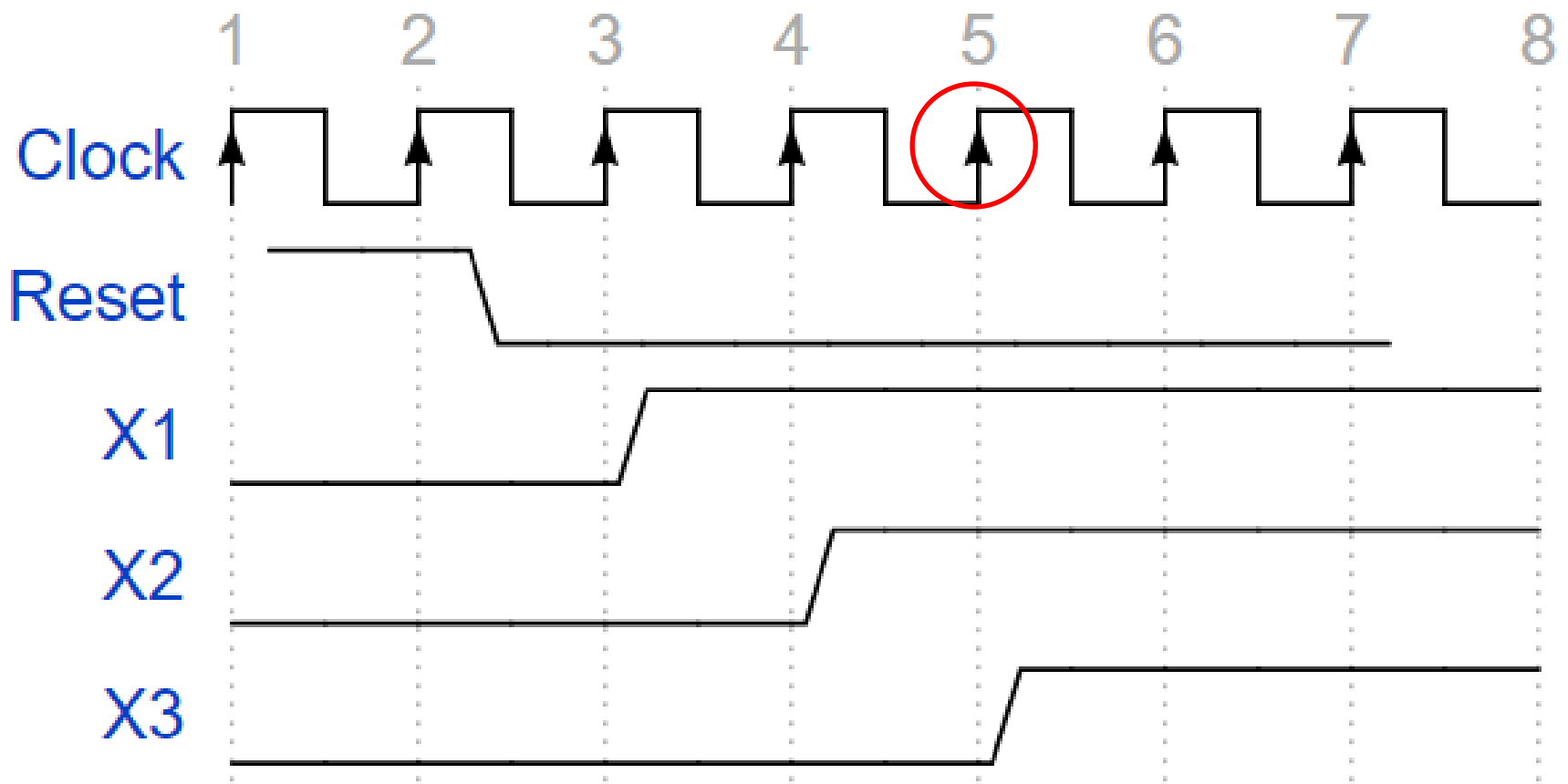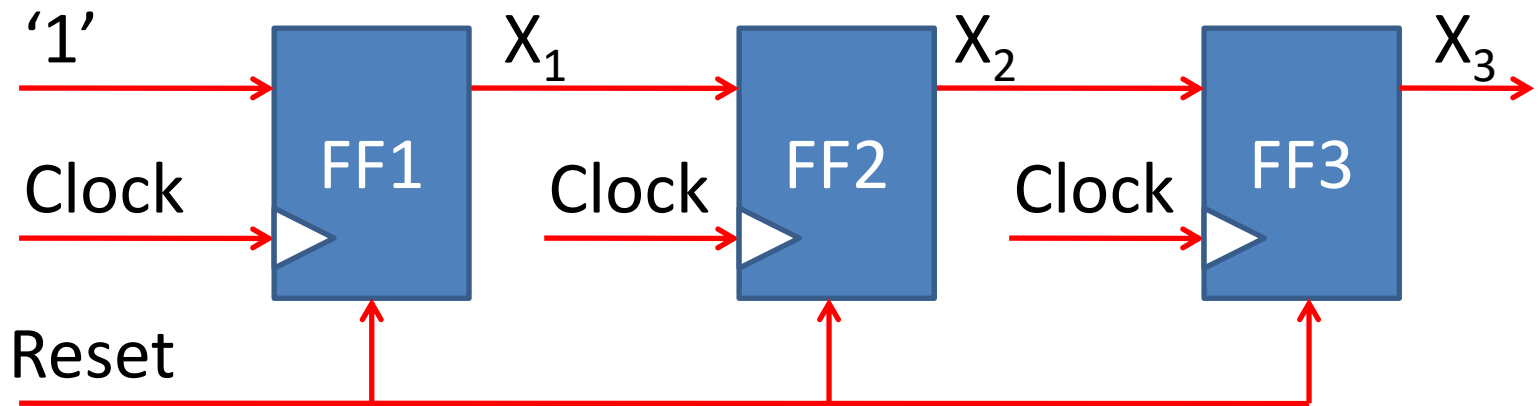

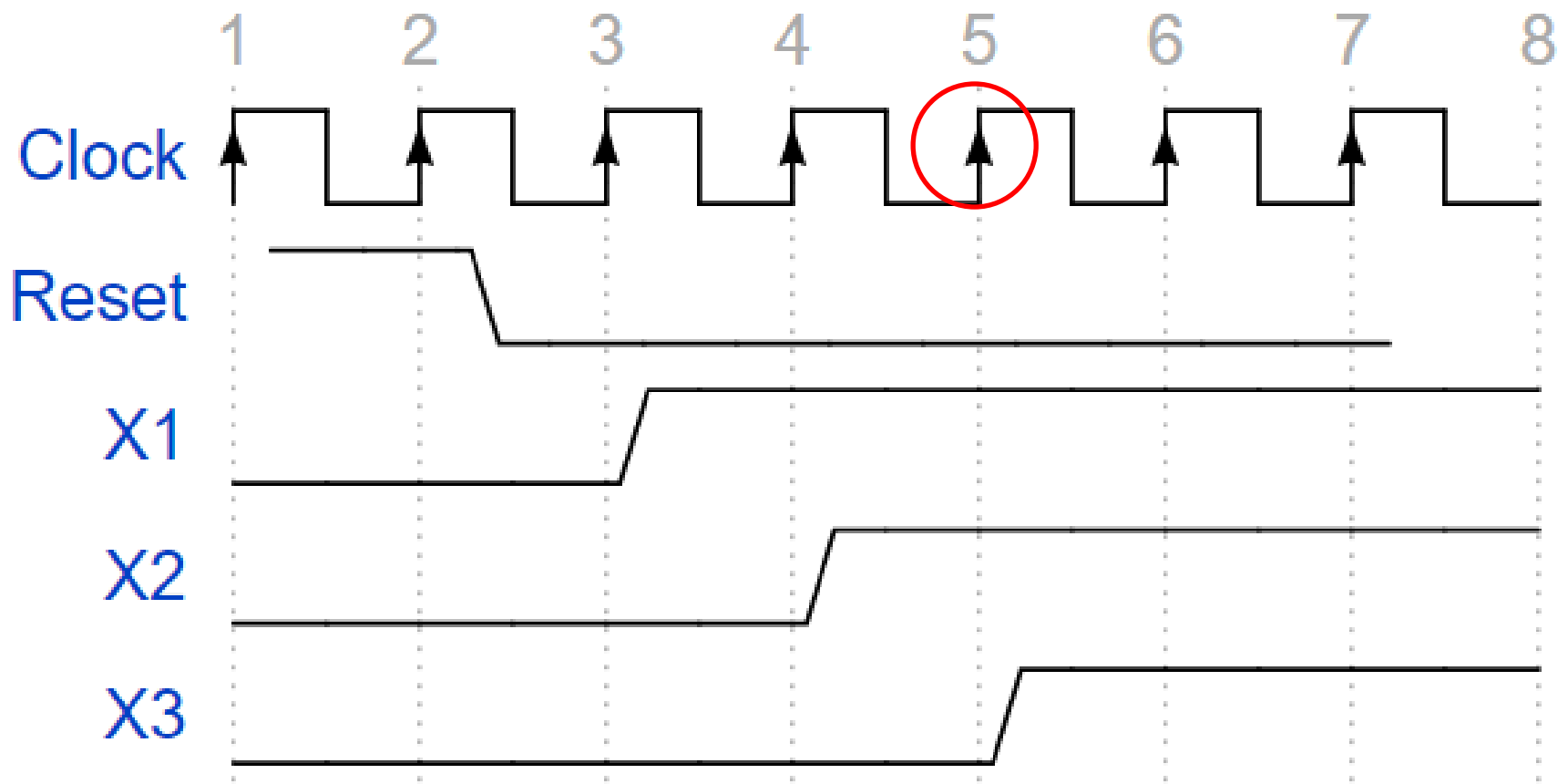 


```
TestProcess : process(Reset, Clock)
begin
    if Reset = '1' then
        X1 <= '0';
        X2 <= '0';
    elsif rising_edge(Clock) then
        X1 <= '1';
        X2 <= '1';
    end if;
end process;
```

```
TestProcess : process(Reset, Clock)
begin
    if Reset = '1' then
        X1 <= '0';
        X2 <= '0';
    elsif rising_edge(Clock) then
        X1 <= '1';
        X2 <= '1';
    end if;
end process;
```

```
TestProcess : process(Reset, Clock)
begin
    if Reset = '1' then
         $X_1 \leq '0'$ ;
    elsif rising_edge(Clock) then
         $X_1 \leq X_2$ ;
         $X_1 \leq X_3$ ;
    end if;
end process;
```

```
TestProcess : process(Reset, Clock)
begin
    if Reset = '1' then
        X1 <= '0';
    elsif rising_edge(Clock) then
        X1 <= X2; -- VHDL will ignore this line!
        X1 <= X3;
    end if;
end process;
```

End Of Video

Variables

What Are Variables?

- Stores intermediate values within a **process, function or procedure.**

What Are Variables?

- Stores intermediate values within a **process, function or procedure.**
- Cannot be used outside of process, function or procedure.

What Are Variables?

- Stores intermediate values within a **process, function or procedure**.
- Cannot be used outside of process, function or procedure.
- Variable declaration is similar to signal declaration.

What Are Variables?

- Stores intermediate values within a **process, function or procedure**.
- Cannot be used outside of process, function or procedure.
- Variable declaration is similar to signal declaration.
- Like signals, the initial value of a variable is ignored by synthesis!

```
TestProcess : process(Reset, Clock)
    variable X : integer; -- Declaration
begin

end process;
```

```
TestProcess : process(Reset, Clock)
    variable X : integer; -- Declaration
begin
    if Reset = '1' then
        X := 0; -- Variable assignment
        Y <= 0;
    elsif rising_edge(Clock) then

        end if;
end process;
```

```
TestProcess : process(Reset, Clock)
    variable X : integer; -- Declaration
begin
    if Reset = '1' then
        X := 0; -- Variable assignment
        Y <= 0;
    elsif rising_edge(Clock) then
        X := 7; -- X takes the value 7 immediately.

    end if;
end process;
```

```
TestProcess : process(Reset, Clock)
    variable X : integer; -- Declaration
begin
    if Reset = '1' then
        X := 0; -- Variable assignment
        Y <= 0;
    elsif rising_edge(Clock) then
        X := 7; -- X takes the value 7 immediately.
        X := X + 1; -- X becomes 8 here.

    end if;
end process;
```

```
TestProcess : process(Reset, Clock)
    variable X : integer; -- Declaration
begin
    if Reset = '1' then
        X := 0; -- Variable assignment
        Y <= 0;
    elsif rising_edge(Clock) then
        X := 7; -- X takes the value 7 immediately.
        X := X + 1; -- X becomes 8 here.

    end if;
end process;
```

A

15

7

3

57

49

8

6

27

A

15

7

3

57

49

8

6

27

TestProcess : `process`(Reset, Clock)

`variable` Temp : `integer`; -- Declaration

`begin`

`end process;`

A

15

7

3

57

49

8

6

27

TestProcess : process(Reset, Clock)

variable Temp : integer; -- Declaration

begin

if Reset = '1' then

Temp := 0;

Sum <= 0;

elsif rising_edge(Clock) then

end if;

end process;

A

15

7

3

57

49

8

6

27

TestProcess : **process**(Reset, Clock)

variable Temp: **integer**; -- Declaration

begin

if Reset = '1' **then**

 Temp := 0;

 Sum <= 0;

elsif rising_edge(Clock) **then**

for i **in** 0 **to** 7 **loop**

 Temp := Temp + A(i);

end loop;

end if;

end process;

A

15

7

3

57

49

8

6

27

TestProcess : **process**(Reset, Clock)

variable Temp: **integer**; -- Declaration

begin

if Reset = '1' **then**

 Temp := 0;

 Sum <= 0;

elsif rising_edge(Clock) **then**

 Temp := 0;

for i **in** 0 **to** 7 **loop**

 Temp := Temp + A(i);

end loop;

end if;

end process;

A

15

7

3

57

49

8

6

27

TestProcess : process(Reset, Clock)

variable Temp: integer; -- Declaration

begin

if Reset = '1' then

Temp := 0;

Sum <= 0;

elsif rising_edge(Clock) then

Temp := 0;

for i in 0 to 7 loop

Temp := Temp + A(i);

end loop;

Sum <= Temp;

end if;

end process;

```
elsif rising_edge(Clock) then
```

```
    Temp:= 0;
```

```
end if;
```

```
elsif rising_edge(Clock) then
```

```
    Temp:= 0;
```

```
    Temp := Temp + A(0);
```

```
end if;
```

```
elsif rising_edge(Clock) then
```

```
    Temp:= 0;
```

```
    Temp := Temp + A(0);
```

```
    Temp := Temp + A(1);
```

```
end if;
```


elsif rising_edge(Clock) **then**

Temp := 0;

Temp := Temp + A(0);

Temp := Temp + A(1);

Temp := Temp + A(2);

.

.

Temp := Temp + A(6);

Temp := Temp + A(7);

Comes from the FOR
loop

end if;

elsif rising_edge(Clock) **then**

Temp:= 0;

Temp := Temp + A(0);

Temp := Temp + A(1);

Temp := Temp + A(2);

.

.

Temp := Temp + A(6);

Temp := Temp + A(7);

Sum <= Temp;

end if;

Comes from the FOR
loop

```
TestProcess : process(Reset, Clock)
begin
    if Reset = '1' then
        Sum <= 0;
    elsif rising_edge(Clock) then
        Sum <= A(0) + A(1) + ..... A(7);
    end if;
end process;
```

```
TestProcess : process(Reset, Clock)
begin
    if Reset = '1' then
        Sum <= 0;
    elsif rising_edge(Clock) then
        Sum <= 0;
        for i in 0 to 15 loop
            Sum <= Y + A(i);
        end loop;
    end if;
end process;
```

This code will
not work!

```
elsif rising_edge(Clock) then
```

```
    Sum <= 0;
```

```
    Sum <= Sum + A(0);
```

```
    Sum <= Sum + A(1);
```

```
    .
```

```
    .
```

```
    Sum <= Sum + A(6);
```

```
    Sum <= Sum + A(7);
```

```
end if;
```

```
elsif rising_edge(Clock) then
```

```
    Sum <= 0;
```

```
    Sum <= Sum + A(0);
```

```
    Sum <= Sum + A(1);
```

```
    .
```

```
    .
```

```
    Sum <= Sum + A(6);
```

```
    Sum <= Sum + A(7); -- Only this line will be executed.
```

```
end if;
```

Summary

- Variables capture their assignments immediately.
- Can have multiple assignments.
- Used to accumulate results.
- Used to store intermediate values in a calculation.

Functions And Procedures

Functions & Procedures

- Similar to functions in software programming languages.

Functions & Procedures

- Similar to functions in software programming languages.
- Used to perform commonly repeated operations or tasks.

Functions & Procedures

- Similar to functions in software programming languages.
- Used to perform commonly repeated operations or tasks.
- Called from VHDL code to perform tasks.

Functions & Procedures

- Similar to functions in software programming languages.
- Used to perform commonly repeated operations or tasks.
- Called from VHDL code to perform tasks.
- Cannot use registers. Only logic gates.

Functions & Procedures

- Similar to functions in software programming languages.
- Used to perform commonly repeated operations or tasks.
- Called from VHDL code to perform tasks.
- Cannot use registers. Only logic gates.
- Can be declared in architecture, processes & packages.

Functions

- Similar to functions in software programming languages.
- Used to perform regularly used algorithms.
- Can take zero or more inputs.
 - Functions **cannot** change input values.
- Must return an output value.
 - **Cannot** return void or omit a return value.
- **Cannot** contain **wait** statements.

Basic Function Template

```
function FunctionName (input parameters)
return ReturnType is
    -- Constant or variable declarations
Begin
    -- Write the function code here.
    return Something;
end;
```

Basic Function Template

```
function FunctionName (input parameters)
return ReturnType is
    -- Constant or variable declarations
Begin
    -- Write the function code here.
    return Something;
end;
```


Function Example

```
function Increment (InputNum : integer)
```

Function Example

```
function Increment (InputNum : integer)  
return integer is
```

Function Example

```
function    Increment (InputNum    : integer)
return integer is
    variable temp    : integer;
```

Function Example

```
function    Increment (InputNum    : integer)
return integer is
    variable    temp    : integer;
begin
    temp := InputNum + 1;
    return temp;
end;
```

Function Example

```
function Increment (InputNum : integer)
return integer is
    variable temp : integer;
begin
    temp := InputNum + 1;
    return temp;
end;
```

```
C <= Increment(4);  -- Function Usage
```

Procedures

- Similar to Functions.
- Does NOT return a value.
- Parameters can be in, out or inout.
 - In – used to pass values into a procedure
 - Out – used to pass values out of a procedure.
Can have more than one.
 - Inout – used to pass a value into a procedure where it can be modified and passed back out again.

Procedures

- Similar to Functions.
- Does NOT return a value.
- Parameters can be in, out or inout.
 - In – used to pass values into a procedure
 - Out – used to pass values out of a procedure.
Can have more than one.
 - Inout – used to pass a value into a procedure where it can be modified and passed back out again.

Procedures

- Similar to Functions.
- Does NOT return a value.
- Parameters can be in, out or inout.
 - In – used to pass values into a procedure
 - Out – used to pass values out of a procedure.
Can have more than one.
 - Inout – used to pass a value into a procedure where it can be modified and passed back out again.


Basic Procedure Template

```
procedure ProcedureName (parameters) is
    -- Constant or variable declarations
Begin
    -- Write the procedure code here.
end;
```


Basic Procedure Template

```
procedure ProcedureName (parameters) is
    -- Constant or variable declarations
Begin
    -- Write the procedure code here.
end;
```

Full Adder Circuit

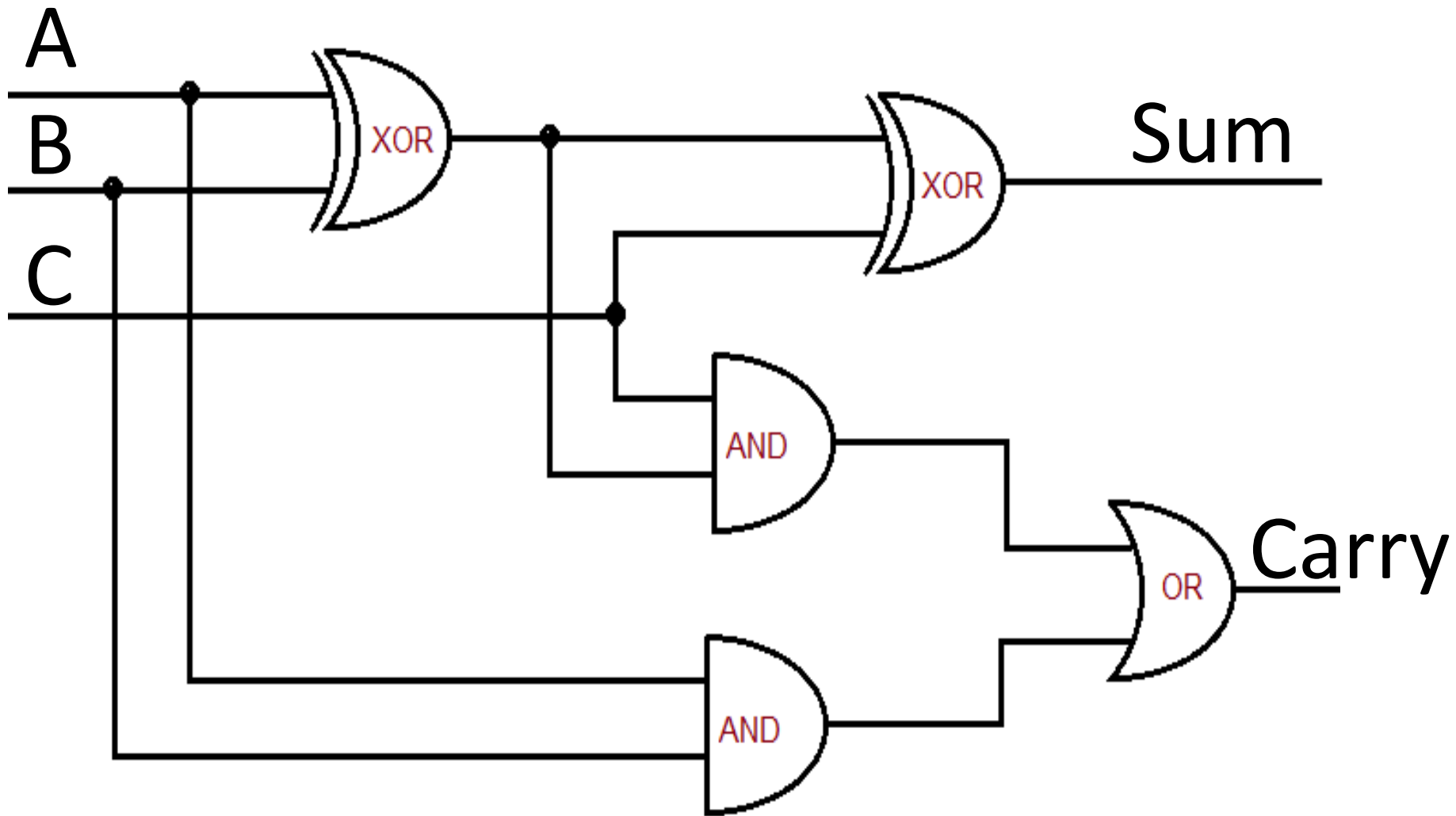

Full Adder Circuit

 

Procedure Example

```
procedure FullAdder
```

Procedure Example

```
procedure FullAdder  
( signal A, B, C      : in  std_logic;  
  signal Sum, Carry : out std_logic  
) is
```

Procedure Example

```
procedure FullAdder
( signal A, B, C      : in  std_logic;
  signal Sum, Carry : out std_logic
) is
begin
    Sum <= A xor B xor C;
    Carry <= (A and B) or (A and C) or (B and C);
end;
```

Procedure Example

```
procedure FullAdder
( signal A, B, C      : in std_logic;
  signal Sum, Carry : out std_logic
) is
begin
    Sum <= A xor B xor C;
    Carry <= (A and B) or (A and C) or (B and C);
end;
```

```
FullAdder (P, Q, R, SO, CO); -- Function Usage
```


End of Video

Packages And Libraries

Package

- Groups various declarations to be shared to be shared among several designs.
- A package can contain these items :
 - Signals & Constants
 - Data Types & Sub Types
 - Functions & Procedures
 - Components
 - Files
 - Attributes

Packages We Have Seen Before

- Need to declare `std_logic_1164` package to use :
 - `Std_logic` and `std_logic_vector` types
- Need to declare `numeric_std` package to use :
 - `Unsigned` and `signed` types

Without Using Packages

Architecture Arch1 of Entity1 is

.....

type TLightType is (RED, AMBER, GREEN);

Signal TrafficLight : TLightType;

.....

Begin

Without Using Packages

Architecture Arch1 of Entity1 is

.....

type TLightType is (RED, AMBER, GREEN);

Signal TrafficLight : TLightType;

.....

Begin

Without Using Packages

VHDL File 1

```
Architecture Arch1 of Module1 is  
    type TLightType is (RED, AMBER, GREEN);  
    Signal TrafficLight : TLightType;  
Begin
```

VHDL File 2

```
Architecture Arch1 of Module2 is  
    type TLightType is (RED, AMBER, GREEN);  
    Signal TrafficLight : TLightType;  
Begin
```

Without Using Packages

VHDL File 1

```
Architecture Arch1 of Module1 is  
    type TLightType is (RED, AMBER, GREEN);  
    Signal TrafficLight : TLightType;  
Begin
```

VHDL File 2

```
Architecture Arch1 of Module2 is  
    type TLightType is (RED, AMBER, GREEN);  
    Signal TrafficLight : TLightType;  
Begin
```


Writing A Basic Package

MyPkg.vhd

```
package MyPackage is
```

```
    type TLightType is (RED, AMBER, GREEN);
```

```
end MyPackage;
```

Writing A Basic Package

MyPkg.vhd

```
package MyPackage is
```

```
    type TLightType is (RED, AMBER, GREEN);
```

```
end MyPackage;
```

Example Using Packages

VHDL File 1

```
use work.MyPackage.all; ←  
Architecture Arch1 of Module1 is  
    Signal TrafficLight : TLightType;  
Begin
```

VHDL File 2

```
use work.MyPackage.all; ←  
Architecture Arch1 of Module2 is  
    Signal TrafficLight : TLightType;  
Begin
```

Example Using Packages

VHDL File 1

```
use work.MyPackage.all; ←  
Architecture Arch1 of Module1 is  
    Signal TrafficLight : TLightType;  
Begin
```

VHDL File 2

```
use work.MyPackage.all; ←  
Architecture Arch1 of Module2 is  
    Signal TrafficLight : TLightType;  
Begin
```

Example Using Packages

VHDL File 1

```
use work.MyPackage.all;
```

```
Architecture Arch1 of Module1 is
```

```
    Signal TrafficLight : TLightType; ←
```

```
Begin
```

VHDL File 2

```
use work.MyPackage.all;
```

```
Architecture Arch1 of Module2 is
```

```
    Signal TrafficLight : TLightType; ←
```

```
Begin
```

Libraries

- Is a **container** that contains **compiled design units**.

Libraries

- Is a **container** that contains **compiled design units**.
- The compiler compiles a design modules into an **intermediate form** and stores this in a library.

Libraries

- Is a **container** that contains **compiled design units**.
- The compiler compiles a design modules into an **intermediate form** and stores this in a library.
- By default, the intermediate forms are stored in the Library you are **currently working in**.

Libraries

- Is a **container** that contains **compiled design units**.
- The compiler compiles a design modules into an **intermediate form** and stores this in a library.
- By default, the intermediate forms are stored in the Library you are **currently working in**.
- Most simulators and synthesis tools **automatically create** this default Library for you.

Libraries

- Is a **container** that contains **compiled design units**.
- The compiler compiles a design modules into an **intermediate form** and stores this in a library.
- By default, the intermediate forms are stored in the Library you are **currently working in**.
- Most simulators and synthesis tools **automatically create** this default Library for you.
- The library you are working in will have a name of its own.

Libraries

- Is a **container** that contains **compiled design units**.
- The compiler compiles a design modules into an **intermediate form** and stores this in a library.
- By default, the intermediate forms are stored in the Library you are **currently working in**.
- Most simulators and synthesis tools **automatically create** this default Library for you.
- The library you are working in will have a name of its own.
- You can use the keyword **Work** to refer to (or point to) the library you are currently working in.

Libraries

- Every library has a name.
- To use a library, you must declare it at the top of your file.
- This makes all the design units in the library available for use in the current design.

Example:

```
Library ieee;  
  
use ieee.numeric_std.all;  
  
use ieee.std_logic_1164.all;
```

Summary

- Creating & using simple VHDL packages.
- Packages are used to share declarations.
- Libraries store compiled design units.
- Current active library is where compiler stores compiled code by default.
- **Work** is used to refer to current active library.

Parameterised Components

Generics

- Generics are a special type of constant.
- Constant is declared in:
 - The declarative part of the architecture (for module scope).
 - VHDL packages (for global scope)
 - Value of a constant is the same across whole design.
- Generic is declared in:
 - The entity declaration.
 - Value of generic unique to each module instance.

Generics

- Generics are a special type of constant.
- Constant is declared in:
 - The declarative part of the architecture (for module scope).
 - VHDL packages (for global scope)
 - Value of a constant is the same across whole design.
- Generic is declared in:
 - The entity declaration.
 - Value of generic unique to each module instance.

Generics

- Generics are a special type of constant.
- Constant is declared in:
 - The declarative part of the architecture (for module scope).
 - VHDL packages (for global scope)
 - Value of a constant is the same across whole design.
- Generic is declared in:
 - The entity declaration.
 - Value of generic unique to each module instance.

entity Adder is

port

(

A : in unsigned(7 downto 0);

B : in unsigned(7 downto 0);

C : out unsigned(7 downto 0)

);

end entity;

architecture rtl of Adder is

begin

C <= A + B;

end architecture;

entity Adder is

port

(

A : in unsigned(7 downto 0);

B : in unsigned(7 downto 0);

C : out unsigned(7 downto 0)

);

end entity;

architecture rtl of Adder is

begin

C <= A + B;

end architecture;

entity Adder is



We are going to declare our generic here

port

(

A : in unsigned(7 downto 0);

B : in unsigned(7 downto 0);

C : out unsigned(7 downto 0)

);

end entity;

architecture rtl of Adder is

begin

C <= A + B;

end architecture;

```
entity Adder is
  generic (
    N : integer := 8
  );
  port
  (
    A  : in  unsigned(7 downto 0);
    B  : in  unsigned(7 downto 0);
    C  : out unsigned(7 downto 0)
  );
end entity;
```

```
architecture rtl of Adder is
begin
    C <= A + B;
end architecture;
```

```
entity Adder is
  generic (
    N : integer := 8
  );
  port
  (
    A  : in  unsigned(N-1 downto 0);
    B  : in  unsigned(N-1 downto 0);
    C  : out unsigned(N-1 downto 0)
  );
end entity;
```

```
architecture rtl of Adder is
begin
    C <= A + B;
end architecture;
```

Top level VHDL Module

Top level VHDL Module

Adder



```
graph TD; subgraph "Top level VHDL Module"; direction TB; A1[Adder]; A2[Adder]; end;
```

The diagram illustrates a hierarchical VHDL module structure. A large blue rectangle represents the 'Top level VHDL Module'. Inside this module, two identical gray rectangles are stacked vertically. Each gray rectangle is labeled 'Adder' in white text, indicating that the top-level module contains two instances of an adder component.


Adder

Top level VHDL Module

Adder
N = 12

Adder
N = 16


```
Adder12Bit : Adder  
generic map (  
    N => 12  
)  
port  
(  
    ...  
);
```



We write this code in
our Top Level VHDL
module to instantiate
the two Adder
components

```
Adder12Bit : Adder  
generic map (  
    N => 12  
)  
port  
(  
    ...  
);
```

```
Adder16Bit : Adder  
generic map (  
    N => 16  
)  
port  
(  
    ...  
);
```



We write this code in
our Top Level VHDL
module to instantiate
the two Adder
components

Summary

- Generics are a special type of constant.
- Generics allow VHDL modules to be parameterised.
- Parameterised modules :
 - Allow their instances to be configurable.
 - Makes it easier to reuse in other projects.
 - Reduces code redundancy.

Type Conversions

Need For Type Conversion

- VHDL is very strict about data types.
 - VHDL is a strongly typed language.
- Cannot use different types in the same expression.
- When performing a signal assignment, the data type of LHS must match the RHS exactly.
- Type conversion functions & Type Casting.

U
Unsigned

V
Std_logic_vector

I
Integer

S
Signed

U
Unsigned

V
Std_logic_vector

I
Integer

S
Signed

Std_logic_vector(U)


U
Unsigned


V
Std_logic_vector


I
Integer


S
Signed




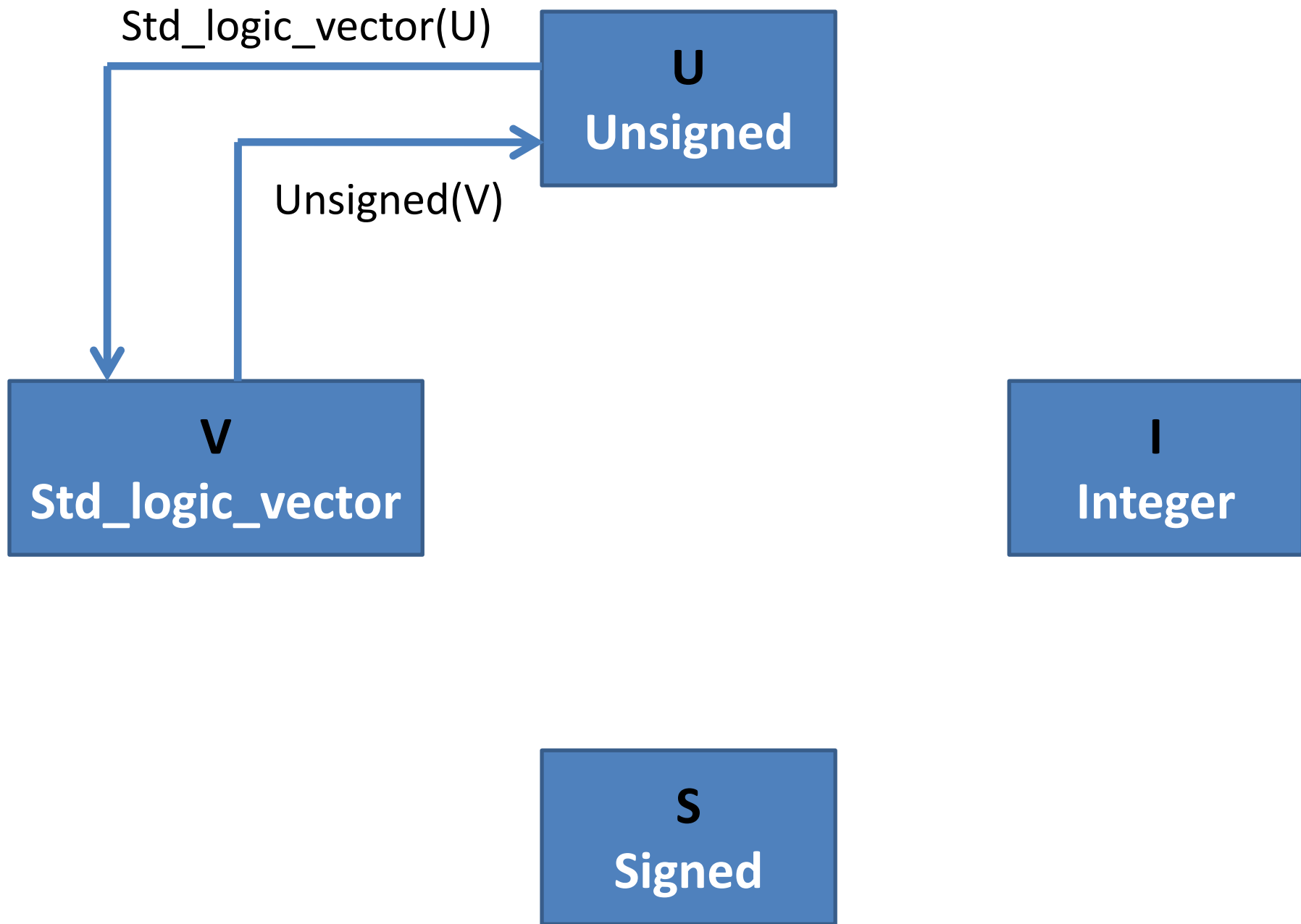


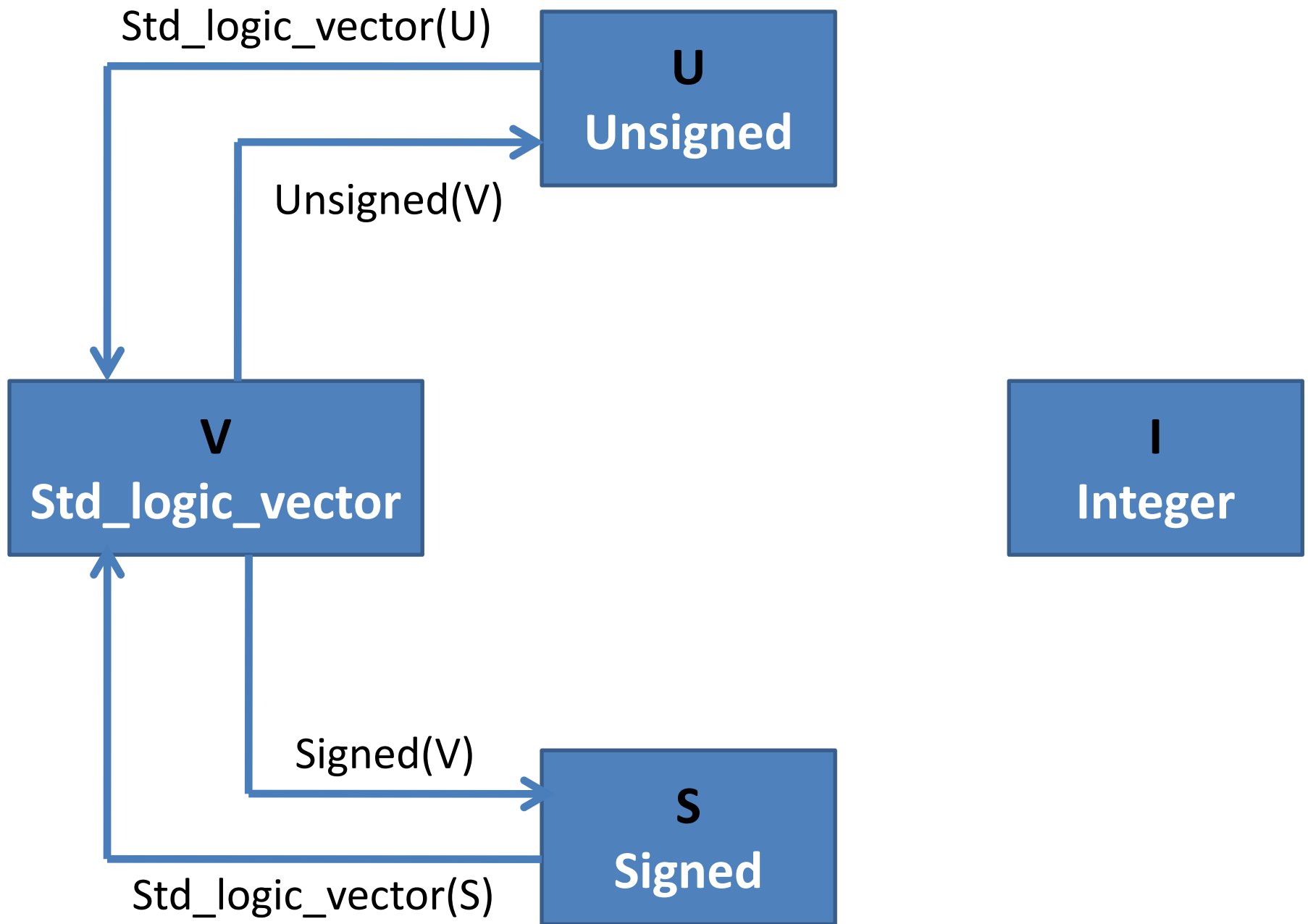

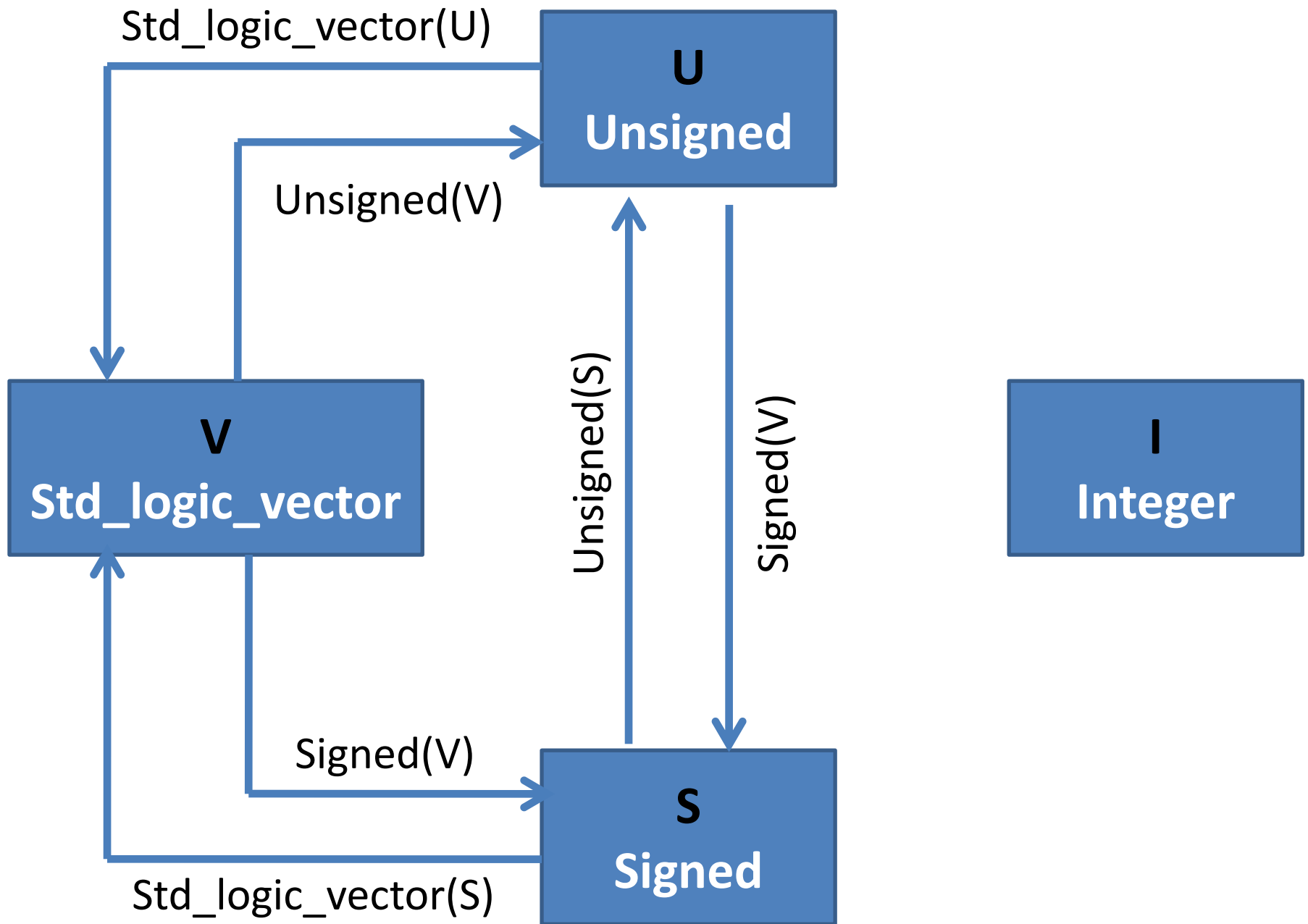

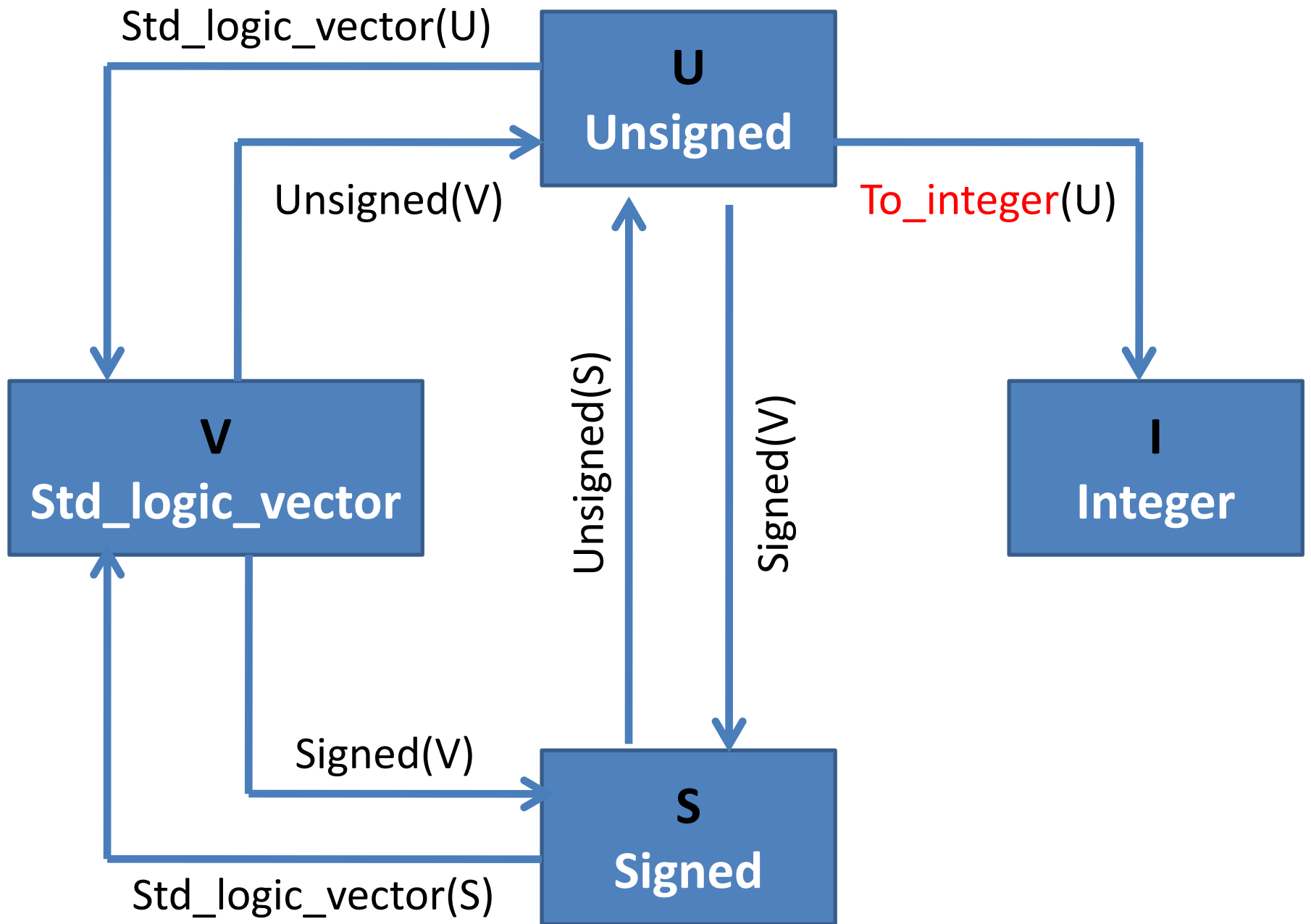

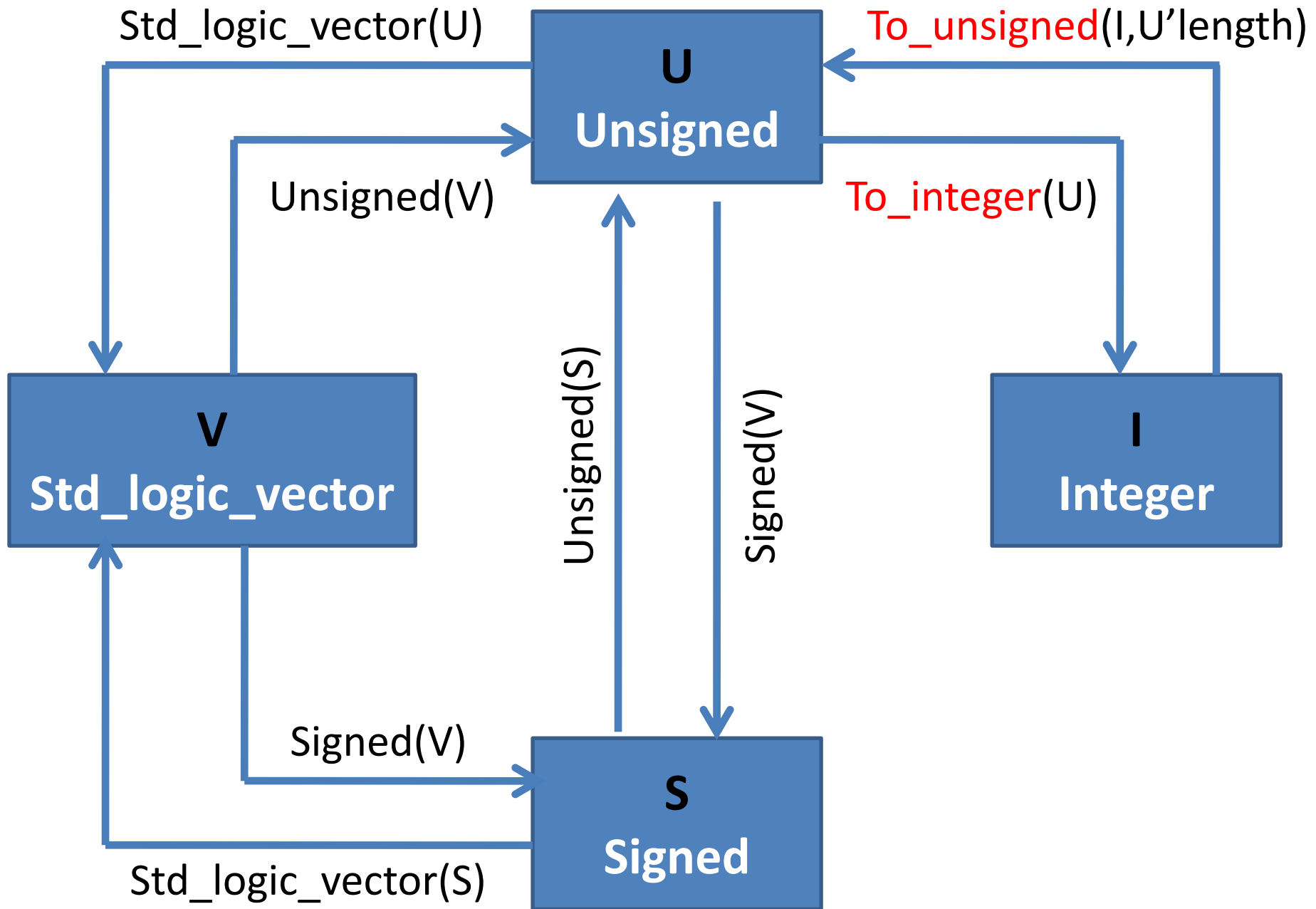

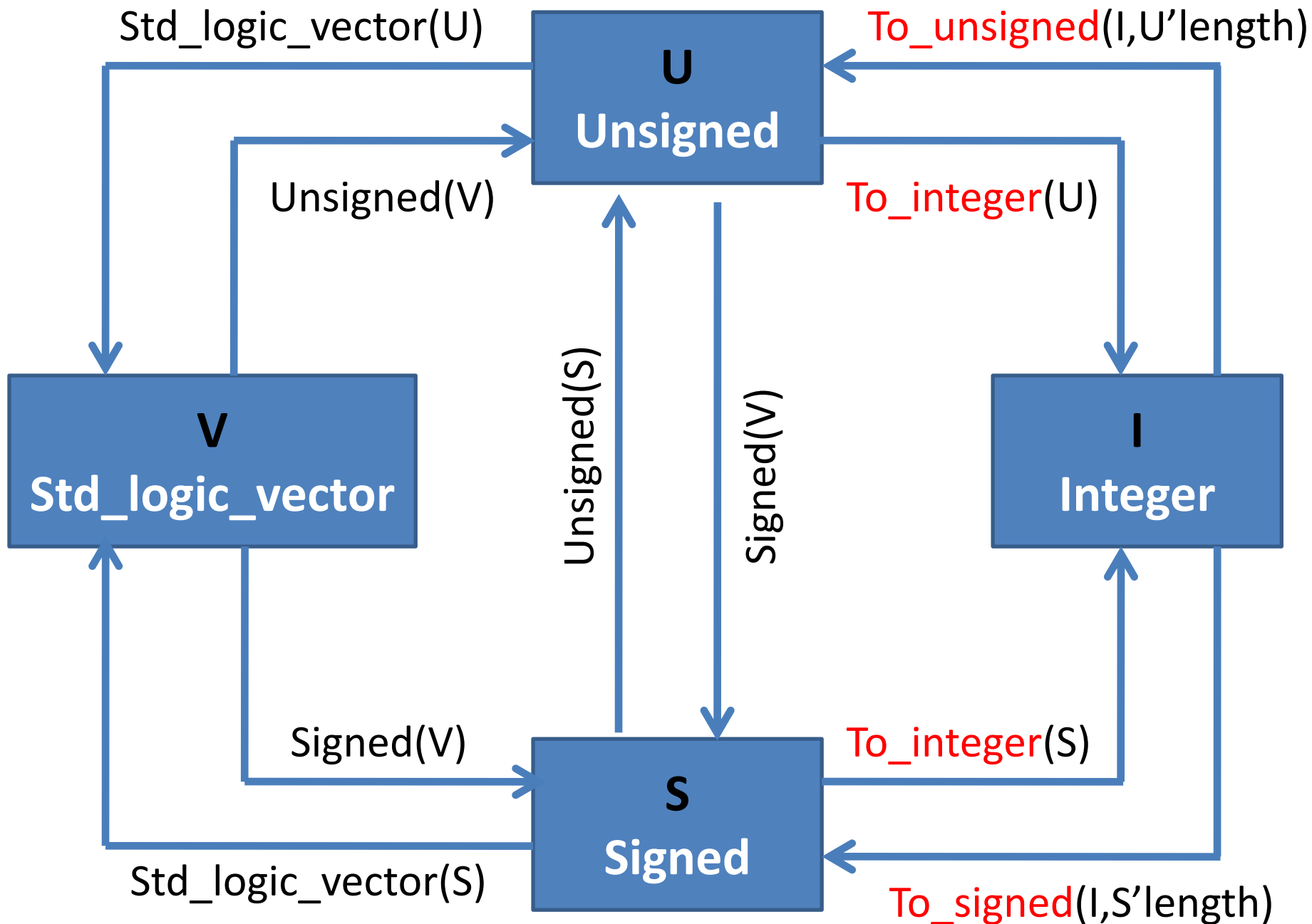

Writing Type Conversion Functions

```
function to_std_logic( A : in boolean)
return std_logic is
begin
    if A then
        return '1';
    else
        return '0';
    end if;
end;
```


Summary

- The need for type conversion in VHDL.
- Type conversions provided by numeric standard package.
- We can write our own type conversion functions.
- Type conversion does not cost extra FPGA resources.

Others Keyword

Others Keyword

- To cover all choices that have not been explicitly covered in a CASE statement

Others Keyword

- To cover all choices that have not been explicitly covered in a CASE statement
- Assign all elements of an array.

Others Keyword

```
signal A : std_logic_vector (7 downto 0);
```

```
A <= "00000000";
```

Others Keyword

```
signal A : std_logic_vector (7 downto 0);
```

```
A <= "00000000";
```

```
A <= x"00";
```

Others

```
signal A : std_logic_vector (7 downto 0);
```

```
A <= "00000000";
```

```
A <= x"00";
```

```
A <= (others => '0');
```

Tri-State Drivers


Tri-State Drivers

- Are only available on IO pins of FPGA.

Tri-State Drivers

- Are only available on IO pins of FPGA.
- Cannot have Tri-state signals internal to the FPGA.

Tri-State Drivers

 


Tri-State Drivers

```
TriState_Example : process (D , Enable)
```


```
begin
```

```
end process;
```

 


Tri-State Drivers
 
```
TriState_Example : process (D , Enable)
begin
    if Enable = '1' then
        Q <= D;
    end process;
```



Tri-State Drivers
 
```
TriState_Example : process (D , Enable)
begin
    if Enable = '1' then
        Q <= D;
    else
        Q <= 'Z';
    end if;
end process;
```



Comparators

Comparators

VHDL for Comparator

```
architecture rtl of SomeRandomVHDLModule is
    signal A      : integer;
    signal B      : integer;
    signal Out    : std_logic;
begin
```

VHDL for Comparator

```
architecture rtl of SomeRandomVHDLModule is
    signal A      : integer;
    signal B      : integer;
    signal Out    : std_logic;
begin
```

VHDL for Comparator

```
architecture rtl of SomeRandomVHDLModule is
    signal A      : integer;
    signal B      : integer;
    signal Out    : std_logic;
begin
    MyComparatorProcess : process (A, B)
    begin
```

VHDL for Comparator

```
architecture rtl of SomeRandomVHDLModule is
    signal A      : integer;
    signal B      : integer;
    signal Out     : std_logic;
begin
    MyComparatorProcess : process (A, B)
    begin
        if A > B then
            Out <= '1';
```

VHDL for Comparator

```
architecture rtl of SomeRandomVHDLModule is
```

```
    signal A      : integer;
```

```
    signal B      : integer;
```

```
    signal Out     : std_logic;
```

```
begin
```

```
    MyComparatorProcess : process (A, B)
```

```
    begin
```

```
        if A > B then
```

```
            Out <= '1';
```

```
        else
```

```
            Out <= '0';
```

```
        end if;
```

VHDL for Comparator

```
architecture rtl of SomeRandomVHDLModule is
```

```
    signal A      : integer;
```

```
    signal B      : integer;
```

```
    signal Out    : std_logic;
```

```
begin
```

```
    MyComparatorProcess : process (A, B)
```

```
    begin
```

```
        if A > B then
```

```
            Out <= '1';
```

```
        else
```

```
            Out <= '0';
```

```
        end if;
```

```
    end process;
```

```
...
```

```
...
```

```
...
```

```
...
```

```
end rtl;
```

VHDL for Comparator

```
architecture rtl of SomeRandomVHDLModule is
```

```
    signal A      : integer;
```

```
    signal B      : integer;
```

```
    signal Out     : std_logic;
```

```
begin
```

```
    MyComparatorProcess : process (A, B)
```

```
    begin
```

```
        if A > B then
```

```
            Out <= '1';
```

```
        else
```

```
            Out <= '0';
```

```
        end if;
```

```
    end process;
```

```
...
```


```
...
```

```
...
```

```
...
```

```
end rtl;
```

Multiplexers

 

VHDL for Multiplexer

```
architecture rtl of SomeRandomVHDLModule is
```

```
    signal A      : integer;
```

```
    signal B      : integer;
```

```
    signal C      : integer;
```

```
    signal D      : integer;
```

```
    signal Out    : integer;
```

```
    signal Sel     : integer range 0 to 3;
```

```
begin
```

VHDL for Multiplexer

```
architecture rtl of SomeRandomVHDLModule is
```

```
    signal A      : integer;
```

```
    signal B      : integer;
```

```
    signal C      : integer;
```

```
    signal D      : integer;
```

```
    signal Out    : integer;
```

```
    signal Sel    : integer range 0 to 3;
```

```
begin
```

```
    MyMuxProcess : process (A, B, C, D, Sel)
```

```
    begin
```

VHDL for Multiplexer

```
architecture rtl of SomeRandomVHDLModule is
```

```
    signal A      : integer;  
    signal B      : integer;  
    signal C      : integer;  
    signal D      : integer;  
    signal Out     : integer;  
    signal Sel     : integer range 0 to 3;
```

```
begin
```

```
    MyMuxProcess : process (A, B, C, D, Sel)
```

```
    begin
```

```
        case Sel is
```

VHDL for Multiplexer

```
architecture rtl of SomeRandomVHDLModule is
```

```
    signal A      : integer;  
    signal B      : integer;  
    signal C      : integer;  
    signal D      : integer;  
    signal Out    : integer;  
    signal Sel    : integer range 0 to 3;
```

```
begin
```

```
    MyMuxProcess : process (A, B, C, D, Sel)
```

```
    begin
```

```
        case Sel is
```

```
            when 0 => Out <= A;
```

VHDL for Multiplexer

```
architecture rtl of SomeRandomVHDLModule is
```

```
    signal A      : integer;  
    signal B      : integer;  
    signal C      : integer;  
    signal D      : integer;  
    signal Out     : integer;  
    signal Sel     : integer range 0 to 3;
```

```
begin
```

```
    MyMuxProcess : process (A, B, C, D, Sel)
```

```
    begin
```

```
        case Sel is
```

```
            when 0 => Out <= A;
```

```
            when 1 => Out <= B;
```

VHDL for Multiplexer

```
architecture rtl of SomeRandomVHDLModule is
```

```
    signal A      : integer;  
    signal B      : integer;  
    signal C      : integer;  
    signal D      : integer;  
    signal Out    : integer;  
    signal Sel     : integer range 0 to 3;
```

```
begin
```

```
    MyMuxProcess : process (A, B, C, D, Sel)
```

```
    begin
```

```
        case Sel is
```

```
            when 0 => Out <= A;
```

```
            when 1 => Out <= B;
```

```
            when 2 => Out <= C;
```

VHDL for Multiplexer

```
architecture rtl of SomeRandomVHDLModule is
```

```
    signal A      : integer;  
    signal B      : integer;  
    signal C      : integer;  
    signal D      : integer;  
    signal Out    : integer;  
    signal Sel     : integer range 0 to 3;
```

```
begin
```

```
    MyMuxProcess : process (A, B, C, D, Sel)
```

```
    begin
```

```
        case Sel is
```

```
            when 0 => Out <= A;
```

```
            when 1 => Out <= B;
```

```
            when 2 => Out <= C;
```

```
            when 3 => Out <= D;
```


VHDL for Multiplexer

```
architecture rtl of SomeRandomVHDLModule is
```

```
    signal A      : integer;  
    signal B      : integer;  
    signal C      : integer;  
    signal D      : integer;  
    signal Out    : integer;  
    signal Sel     : integer range 0 to 3;
```

```
begin
```

```
    MyMuxProcess : process (A, B, C, D, Sel)
```

```
    begin
```

```
        case Sel is
```

```
            when 0 => Out <= A;
```

```
            when 1 => Out <= B;
```

```
            when 2 => Out <= C;
```

```
            when 3 => Out <= D;
```

```
            when others =>
```

VHDL for Multiplexer

```
architecture rtl of SomeRandomVHDLModule is
```

```
    signal A      : integer;  
    signal B      : integer;  
    signal C      : integer;  
    signal D      : integer;  
    signal Out    : integer;  
    signal Sel     : integer range 0 to 3;
```

```
begin
```

```
    MyMuxProcess : process (A, B, C, D, Sel)
```

```
    begin
```

```
        case Sel is
```

```
            when 0 => Out <= A;
```

```
            when 1 => Out <= B;
```

```
            when 2 => Out <= C;
```

```
            when 3 => Out <= D;
```

```
            when others =>
```

```
        end case;
```

VHDL for Multiplexer

architecture rtl of SomeRandomVHDLModule is

```
signal A      : integer;
signal B      : integer;
signal C      : integer;
signal D      : integer;
signal Out    : integer;
signal Sel    : integer range 0 to 3;
```

begin

```
MyMuxProcess : process (A, B, C, D, Sel)
```

```
begin
```

```
    case Sel is
```

```
        when 0 => Out <= A;
```

```
        when 1 => Out <= B;
```

```
        when 2 => Out <= C;
```


```
        when 3 => Out <= D;
```

```
        when others =>
```

```
    end case;
```

```
end process;
```

```
end rtl;
```

 

VHDL for Multiplexer

MyMuxProcess : `process` (reset, clk)

`begin`

VHDL for Multiplexer

```
MyMuxProcess : process (reset, clk)
```

```
begin
```

```
    if reset = '1' then
```

```
        Out <= 0;
```

VHDL for Multiplexer

```
MyMuxProcess : process (reset, clk)
```

```
begin
```

```
    if reset = '1' then
```

```
        Out <= 0;
```

```
    elsif rising_edge(clk) then
```

VHDL for Multiplexer

```
MyMuxProcess : process (reset, clk)
```

```
begin
```

```
    if reset = '1' then
```

```
        Out <= 0;
```

```
    elsif rising_edge(clk) then
```

```
        case Sel is
```

```
            when 0 => Out <= A;
```

```
            when 1 => Out <= B;
```

```
            when 2 => Out <= C;
```

```
            when 3 => Out <= D;
```

```
            when others =>
```

```
        end case;
```


VHDL for Multiplexer

```
MyMuxProcess : process (reset, clk)
```

```
begin
```

```
    if reset = '1' then
```

```
        Out <= 0;
```

```
    elsif rising_edge(clk) then
```

```
        case Sel is
```

```
            when 0 => Out <= A;
```

```
            when 1 => Out <= B;
```

```
            when 2 => Out <= C;
```

```
            when 3 => Out <= D;
```


```
            when others =>
```


```
        end case;
```

```
    end if;
```

```
end process;
```

Shift Registers

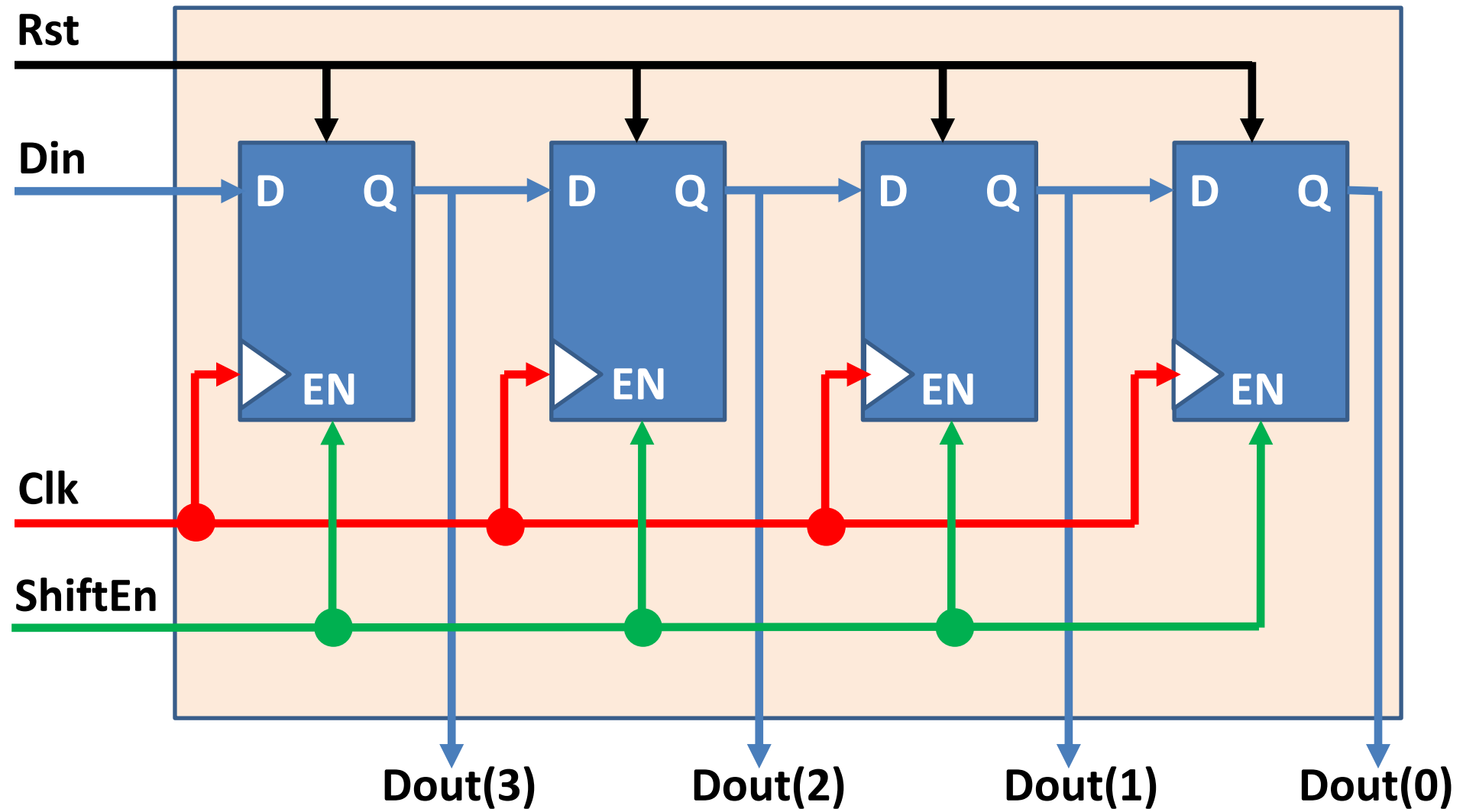

 

VHDL for Shift Register

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.all;
```

VHDL for Shift Register

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.all;
```

```
entity ShiftRegisterChain is
```

VHDL for Shift Register

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.all;
```

```
entity ShiftRegisterChain is
```

```
    generic (
```

```
        CHAIN_LENGTH : integer
```

```
    );
```

VHDL for Shift Register

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.all;
```

```
entity ShiftRegisterChain is
```

```
    generic (
```

```
        CHAIN_LENGTH : integer
```

```
    );
```

```
    port(
```

```
        Clk      : in std_logic;
```

```
        Rst      : in std_logic;
```

```
        ShiftEn  : in std_logic;
```

```
        Din      : in std_logic;
```

```
        Dout     : out std_logic_vector(CHAIN_LENGTH-1 downto 0)
```

```
    );
```


VHDL for Shift Register

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.all;
```

```
entity ShiftRegisterChain is
```

```
    generic (
```

```
        CHAIN_LENGTH : integer
```

```
    );
```

```
    port(
```

```
        Clk      : in std_logic;
```

```
        Rst      : in std_logic;
```

```
        ShiftEn  : in std_logic;
```

```
        Din      : in std_logic;
```

```
        Dout     : out std_logic_vector(CHAIN_LENGTH-1 downto 0)
```

```
    );
```

```
end entity;
```

VHDL for Shift Register

```
architecture rtl of ShiftRegisterChain is  
begin
```

VHDL for Shift Register

```
architecture rtl of ShiftRegisterChain is  
begin
```

```
    ShiftRegisterProcess : process(rst, clk)
```

VHDL for Shift Register

```
architecture rtl of ShiftRegisterChain is  
begin
```

```
    ShiftRegisterProcess : process(rst, clk)  
    begin
```

VHDL for Shift Register

```
architecture rtl of ShiftRegisterChain is  
begin
```

```
    ShiftRegisterProcess : process(rst, clk)
```

```
    begin
```

```
        if rst = '1' then
```

```
            Dout <= (others => '0');
```

VHDL for Shift Register

```
architecture rtl of ShiftRegisterChain is  
begin
```

```
    ShiftRegisterProcess : process(rst, clk)
```

```
    begin
```

```
        if rst = '1' then
```

```
            Dout <= (others => '0');
```

```
        elsif rising_edge(clk) then
```

VHDL for Shift Register

```
architecture rtl of ShiftRegisterChain is  
begin
```

```
ShiftRegisterProcess : process(rst, clk)  
begin
```

```
    if rst = '1' then
```

```
        Dout <= (others => '0');
```

```
    elsif rising_edge(clk) then
```

```
        Dout <= Din & Dout (Dout'left downto 1) ;
```


VHDL for Shift Register

```
Dout : out std_logic_vector(CHAIN_LENGTH-1 downto 0);
```

```
Dout <= Din & Dout (Dout 'left downto 1);
```


VHDL for Shift Register

```
Dout : out std_logic_vector(CHAIN_LENGTH-1 downto 0);
```



```
Dout <= Din & Dout (Dout 'left downto 1);
```

VHDL for Shift Register


```
Dout : out std_logic_vector(3 downto 0);
```

```
Dout <= Din & Dout (Dout 'left downto 1);
```

VHDL for Shift Register

```
Dout : out std_logic_vector(3 downto 0);
```

```
Dout <= Din & Dout (Dout 'left downto 1);
```



VHDL for Shift Register


```
Dout : out std_logic_vector(3 downto 0);
```

```
Dout <= Din & Dout (3 downto 1);
```

VHDL for Shift Register

```
Dout : out std_logic_vector(3 downto 0);
```

```
Dout <= Din & Dout (3 downto 1);
```

 


Index	3	2	1	0
Value	Dout(3)	Dout(2)	Dout(1)	Dout(0)



VHDL for Shift Register

```
Dout : out std_logic_vector(3 downto 0);
```

```
Dout <= Din & Dout (3 downto 1);
```

 


Index	3	2	1	0
Value	Dout(3)	Dout(2)	Dout(1)	Dout(0)



VHDL for Shift Register

```
Dout : out std_logic_vector(3 downto 0);
```

```
Dout <= Din & Dout (3 downto 1);
```

 


Index	3	2	1	0
Value	Dout(3)	Dout(2)	Dout(1)	Dout(0)



VHDL for Shift Register

```
Dout : out std_logic_vector(3 downto 0);
```

```
Dout <= Din & Dout (3 downto 1);
```

 


Index	3	2	1	0
Value	Dout(3)	Dout(2)	Dout(1)	Dout(0)



VHDL for Shift Register

```
Dout : out std_logic_vector(3 downto 0);
```

```
Dout <= Din & Dout (3 downto 1);
```

 

Index	3	2	1	0
Value	Dout(3)	Dout(2)	Dout(1)	Dout(0)

<=


Index	3	2	1	0
Value	Din	Dout(3)	Dout(2)	Dout(1)

A red arrow points upwards from below the 'Din' cell in the right-hand table, highlighting the input source for the new value at index 3.

VHDL for Shift Register

```
Dout : out std_logic_vector(3 downto 0);
```

```
Dout <= Din & Dout (3 downto 1);
```

 

Index	3	2	1	0
Value	Dout(3)	Dout(2)	Dout(1)	Dout(0)

<=


Index	3	2	1	0
Value	Din	Dout(3)	Dout(2)	Dout(1)



VHDL for Shift Register

```
Dout : out std_logic_vector(3 downto 0);
```

```
Dout <= Din & Dout (3 downto 1);
```

 


Index	3	2	1	0		Index	3	2	1	0
Value	Dout(3)	Dout(2)	Dout(1)	Dout(0)	<=	Value	Din	Dout(3)	Dout(2)	Dout(1)

A red arrow points upwards from below the table to the cell containing `Dout(2)` in the next state, indicating that the value currently at index 1 is being shifted into index 2.

VHDL for Shift Register

```
Dout : out std_logic_vector(3 downto 0);
```

```
Dout <= Din & Dout (3 downto 1);
```

 


Index	3	2	1	0		Index	3	2	1	0
Value	Dout(3)	Dout(2)	Dout(1)	Dout(0)	<=	Value	Din	Dout(3)	Dout(2)	Dout(1)

A red arrow points upwards from below the table to the cell containing `Dout(1)` in the right-hand table, indicating that the value currently at index 1 is being shifted to index 0.

VHDL for Shift Register

```
Dout : out std_logic_vector(3 downto 0);
```

```
Dout <= Din & Dout (3 downto 1);
```

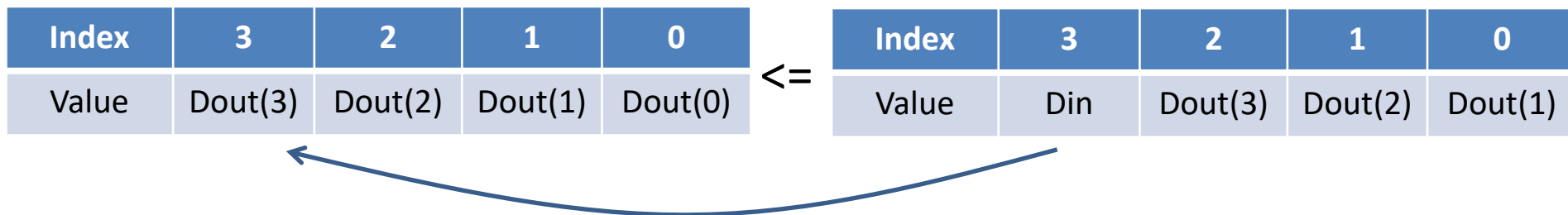


```
Dout(3) <= Din;
```

VHDL for Shift Register

```
Dout : out std_logic_vector(3 downto 0);
```

```
Dout <= Din & Dout (3 downto 1);
```

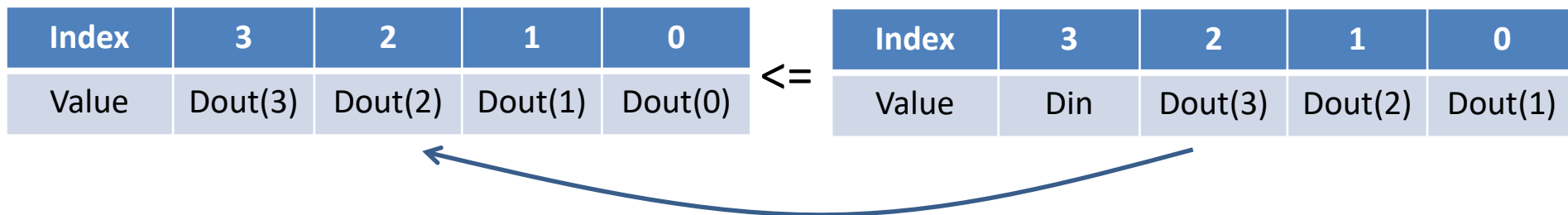


```
Dout(3) <= Din;
```

```
Dout(2) <= Dout(3);
```

VHDL for Shift Register

```
Dout : out std_logic_vector(3 downto 0);
```

```
Dout <= Din & Dout (3 downto 1);
```

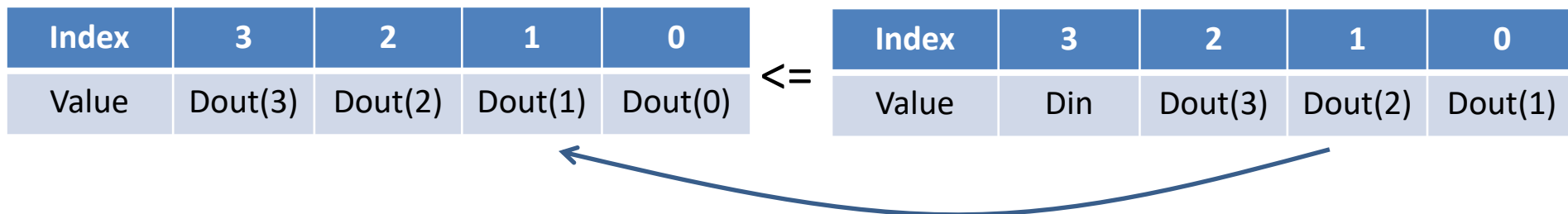

```
Dout(3) <= Din;
```


```
Dout(2) <= Dout(3);
```

```
Dout(1) <= Dout(2);
```

VHDL for Shift Register

```
Dout : out std_logic_vector(3 downto 0);
```

```
Dout <= Din & Dout (3 downto 1);
```

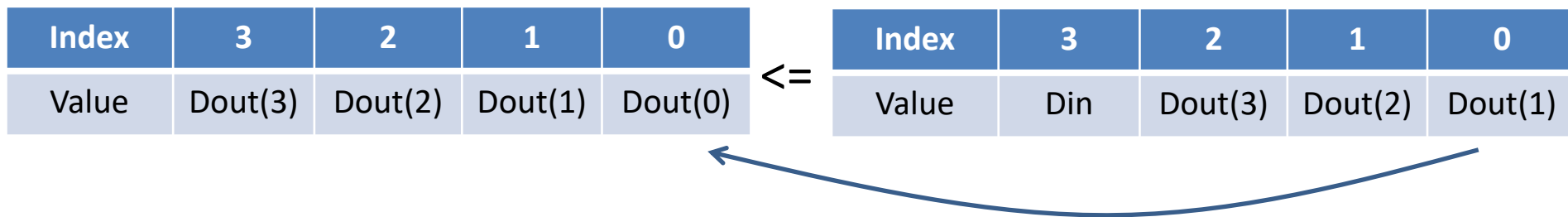

```
Dout(3) <= Din;
```


```
Dout(2) <= Dout(3);
```

```
Dout(1) <= Dout(2);
```

```
Dout(0) <= Dout(1);
```


VHDL for Shift Register
 
```
Dout(3) <= Din;  
Dout(2) <= Dout(3);  
Dout(1) <= Dout(2);  
Dout(0) <= Dout(1);
```



VHDL for Shift Register


```
Dout(3) <= Din;
```



```
Dout(2) <= Dout(3);
```

```
Dout(1) <= Dout(2);
```

```
Dout(0) <= Dout(1);
```

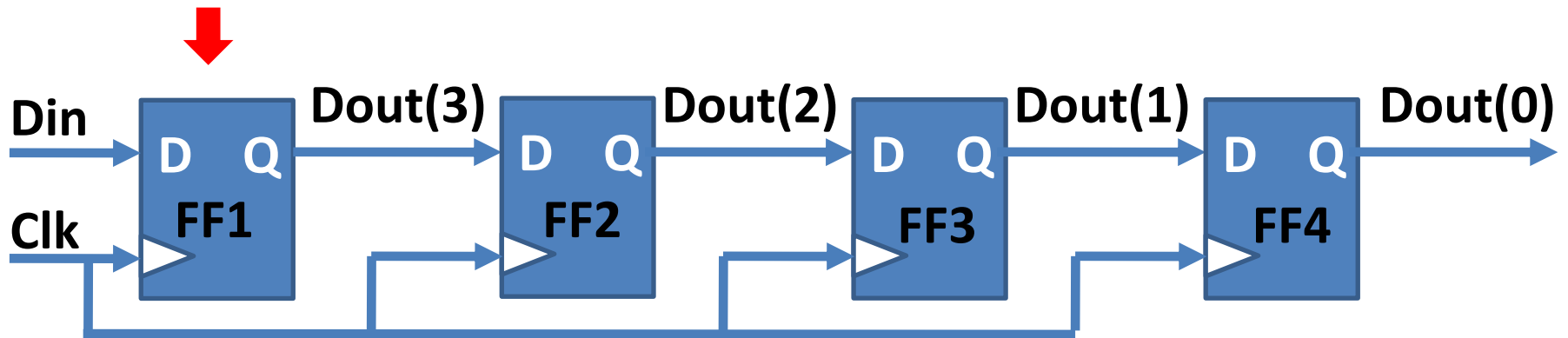


VHDL for Shift Register

```
Dout(3) <= Din;
```

```
Dout(2) <= Dout(3);
```

```
Dout(1) <= Dout(2);
```

```
Dout(0) <= Dout(1);
```

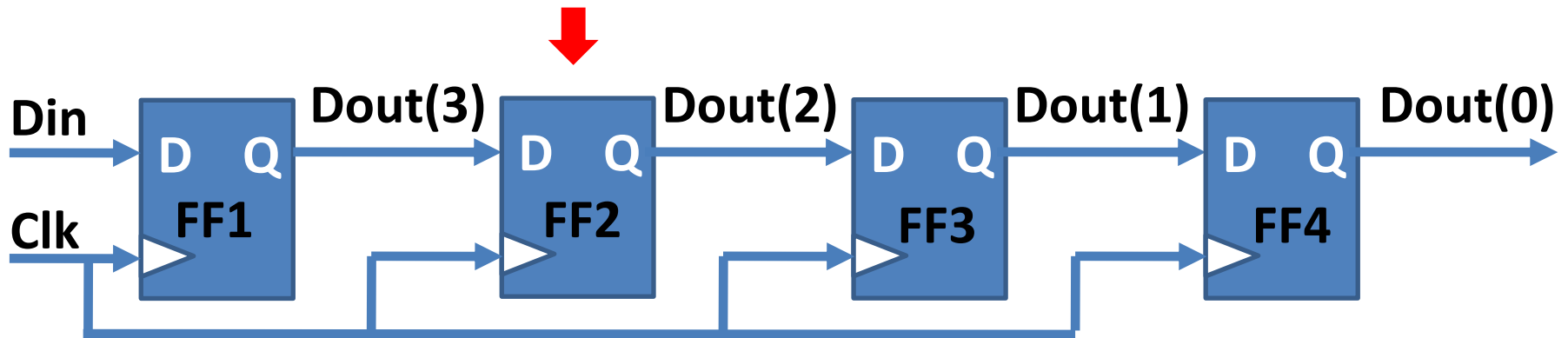


VHDL for Shift Register

```
Dout(3) <= Din;
```

```
Dout(2) <= Dout(3);
```

```
Dout(1) <= Dout(2);
```

```
Dout(0) <= Dout(1);
```

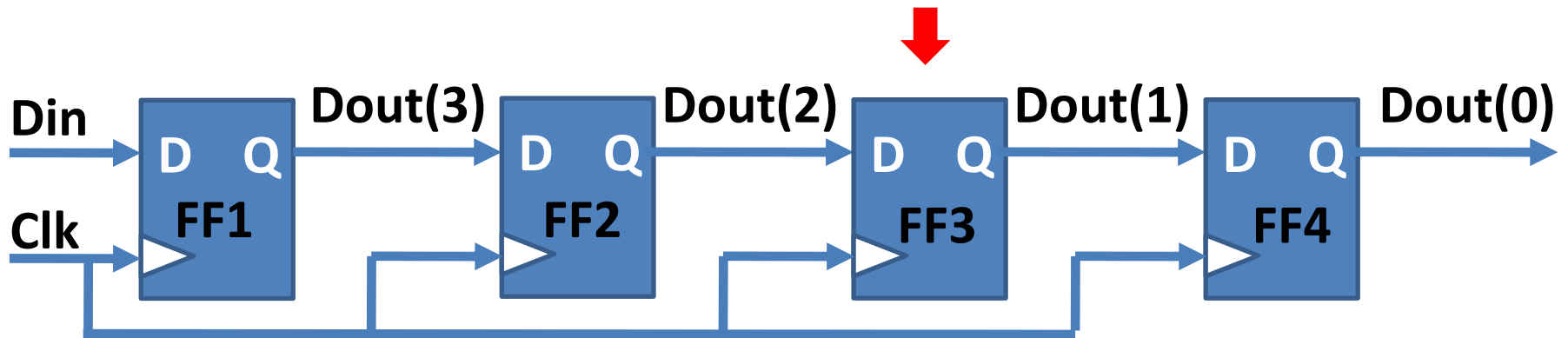


VHDL for Shift Register

```
Dout(3) <= Din;
```

```
Dout(2) <= Dout(3);
```

```
Dout(1) <= Dout(2);
```

```
Dout(0) <= Dout(1);
```

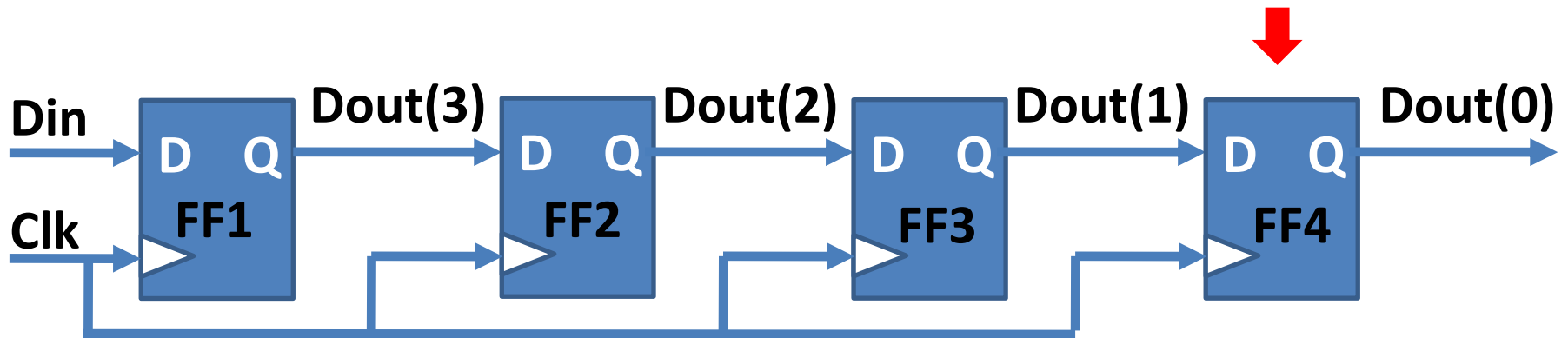

VHDL for Shift Register

```
architecture rtl of ShiftRegisterChain is  
begin
```

```
    ShiftRegisterProcess : process(rst, clk)  
    begin  
        if rst = '1' then  
            Dout <= (others => '0');  
        elsif rising_edge(clk) then  
            Dout <= Din & Dout (Dout'left downto 1) ;  
        end if;  
    end process;
```

VHDL for Shift Register

```
architecture rtl of ShiftRegisterChain is  
begin
```

```
ShiftRegisterProcess : process(rst, clk)  
begin
```

```
    if rst = '1' then
```

```
        Dout <= (others => '0');
```

```
    elsif rising_edge(clk) then
```

```
        if ShiftEn = '1' then
```

```
            Dout <= Din & Dout (Dout'left downto 1) ;
```

```
        end if;
```

```
    end if;
```

```
end process;
```

VHDL for Shift Register

```
architecture rtl of ShiftRegisterChain is  
begin
```

```
    ShiftRegisterProcess : process(rst, clk)  
    begin
```

```
        if rst = '1' then
```

```
            Dout <= (others => '0');
```

```
        elsif rising_edge(clk) then
```

```
            if ShiftEn = '1' then
```

```
                Dout <= Din & Dout (Dout'left downto 1) ;
```

```
            end if;
```


```
        end if;
```


```
    end process;
```

```
end rtl;
```


Serialiser

Serialiser

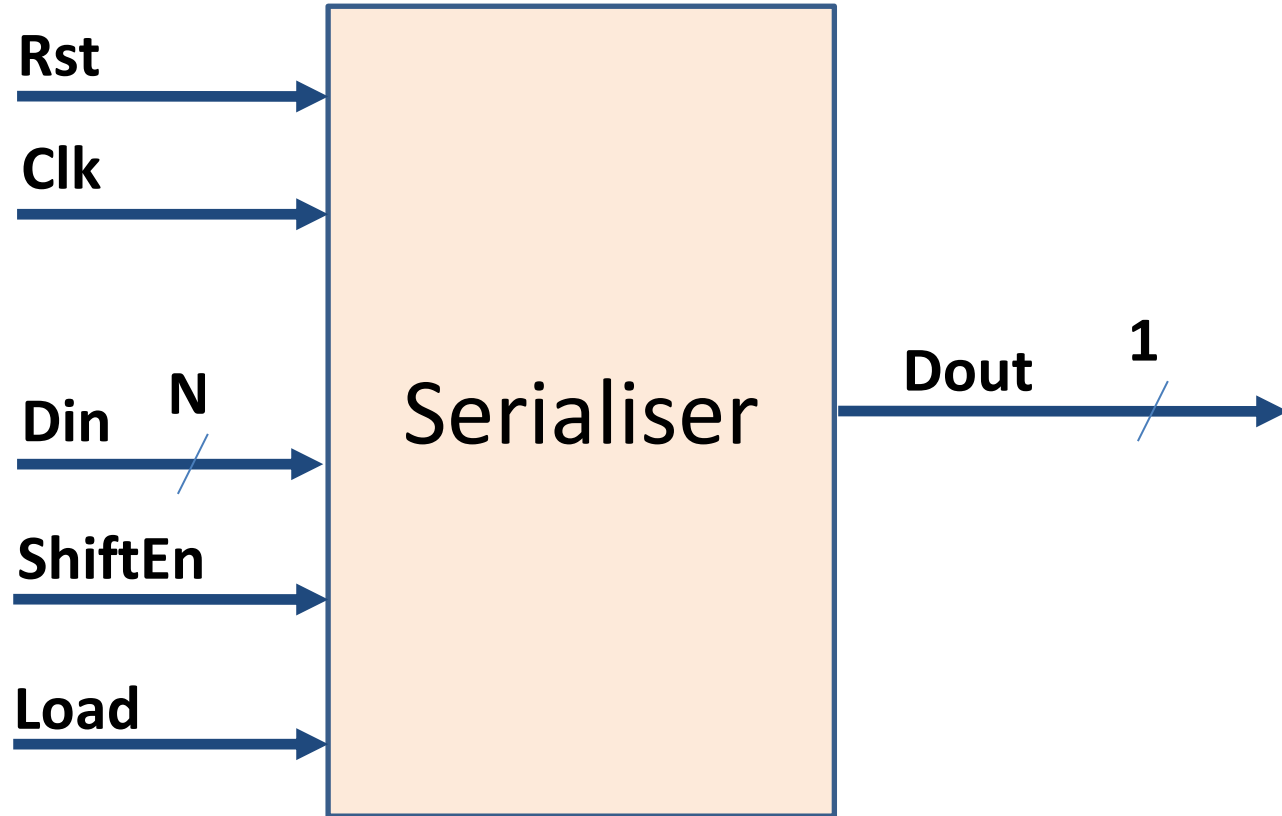

 

```
library IEEE;  
use IEEE.STD_LOGIC_1164.all;
```

```
library IEEE;  
use IEEE.STD_LOGIC_1164.all;
```

```
entity Serialiser is
```

```
library IEEE;  
use IEEE.STD_LOGIC_1164.all;  
  
entity Serialiser is  
    generic (  
        DataWidth : integer  
    );
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity Serialiser is
    generic (
        DataWidth : integer
    );
    port(
        Clk      : in std_logic;
        Rst      : in std_logic;
        ShiftEn   : in std_logic;
        Load     : in std_logic;
        Din      : in std_logic_vector(DataWidth -1 downto 0);
        Dout     : out std_logic
    );
end entity;
```


architecture rtl of Serialiser is

architecture rtl of Serialiser is

 Signal DataRegister : std_logic_vector(DataWidth-1 downto 0);

Begin

architecture rtl of Serialiser is

Signal DataRegister : std_logic_vector(DataWidth-1 downto 0);

Begin

SerialiserProcess : process(Rst,Clk)

begin

architecture rtl of Serialiser is

Signal DataRegister : std_logic_vector(DataWidth-1 downto 0);

Begin

SerialiserProcess : process(Rst,Clk)

begin

if Rst = '1' then

DataRegister <= (others => '0');

architecture rtl of Serialiser is

Signal DataRegister : std_logic_vector(DataWidth-1 downto 0);

Begin

SerialiserProcess : process(Rst,Clk)

begin

if Rst = '1' then

DataRegister <= (others => '0');

elsif rising_edge(Clk) then

architecture rtl of Serialiser is

Signal DataRegister : std_logic_vector(DataWidth-1 downto 0);

Begin

SerialiserProcess : process(Rst,Clk)

begin

if Rst = '1' then

DataRegister <= (others => '0');

elsif rising_edge(Clk) then

if Load = '1' then

DataRegister <= DIN;

architecture rtl of Serialiser is

Signal DataRegister : std_logic_vector(DataWidth-1 downto 0);

Begin

SerialiserProcess : process(Rst,Clk)

begin

if Rst = '1' then

DataRegister <= (others => '0');

elsif rising_edge(Clk) then

if Load = '1' then

DataRegister <= DIN;

elsif ShiftEn = '1' then

architecture rtl of Serialiser is

Signal DataRegister : std_logic_vector(DataWidth-1 downto 0);

Begin

SerialiserProcess : process(Rst,Clk)

begin

if Rst = '1' then

DataRegister <= (others => '0');

elsif rising_edge(Clk) then

if Load = '1' then

DataRegister <= DIN;

elsif ShiftEn = '1' then

DataRegister <= '0' & DataRegister(DataWidth-1 downto 1);

architecture rtl of Serialiser is

Signal DataRegister : std_logic_vector(DataWidth-1 downto 0);

Begin

SerialiserProcess : process(rst,clk)

begin

if rst = '1' then

DataRegister <= (others => '0');

elsif rising_edge(clk) then

if Load = '1' then

DataRegister <= DIN;

elsif ShiftEn = '1' then

DataRegister <= '0' & DataRegister(DataWidth-1 downto 1);

end if;

end if;

end process;

architecture rtl of Serialiser is

Signal DataRegister : std_logic_vector(DataWidth-1 downto 0);

Begin

SerialiserProcess : process(rst,clk)

begin

if rst = '1' then

DataRegister <= (others => '0');

elsif rising_edge(clk) then

if Load = '1' then

DataRegister <= DIN;

elsif ShiftEn = '1' then

DataRegister <= '0' & DataRegister(DataWidth-1 downto 1);

end if;

end if;

end process;

Dout <= DataRegister(0);

architecture rtl of Serialiser is

Signal DataRegister : std_logic_vector(DataWidth-1 downto 0);

Begin

SerialiserProcess : process(rst,clk)

begin

if rst = '1' then

DataRegister <= (others => '0');

elsif rising_edge(clk) then

if Load = '1' then

DataRegister <= DIN;

elsif ShiftEn = '1' then

DataRegister <= '0' & DataRegister(DataWidth-1 downto 1);

end if;

end if;

end process;

Dout <= DataRegister(0);

end rtl;

RAMs


RAM Implementation

- FPGAs implement RAM using :
 1. Register Banks (for smaller memories)
 2. Block RAM (for larger memories)
- Synthesiser infers how to implement RAM by looking at your VHDL code.
- Synthesiser by default goes for Register bank implementation.
- VHDL code must follow a particular template to get the synthesiser to use Block RAM.


RAM Implementation

- FPGAs implement RAM using :
 1. Register Banks (for smaller memories)
 2. Block RAM (for larger memories)
- Synthesiser infers how to implement RAM by looking at your VHDL code.
- Synthesiser by default goes for Register bank implementation.
- VHDL code must follow a particular template to get the synthesiser to use Block RAM.


Single Port RAM

 

Single Port RAM

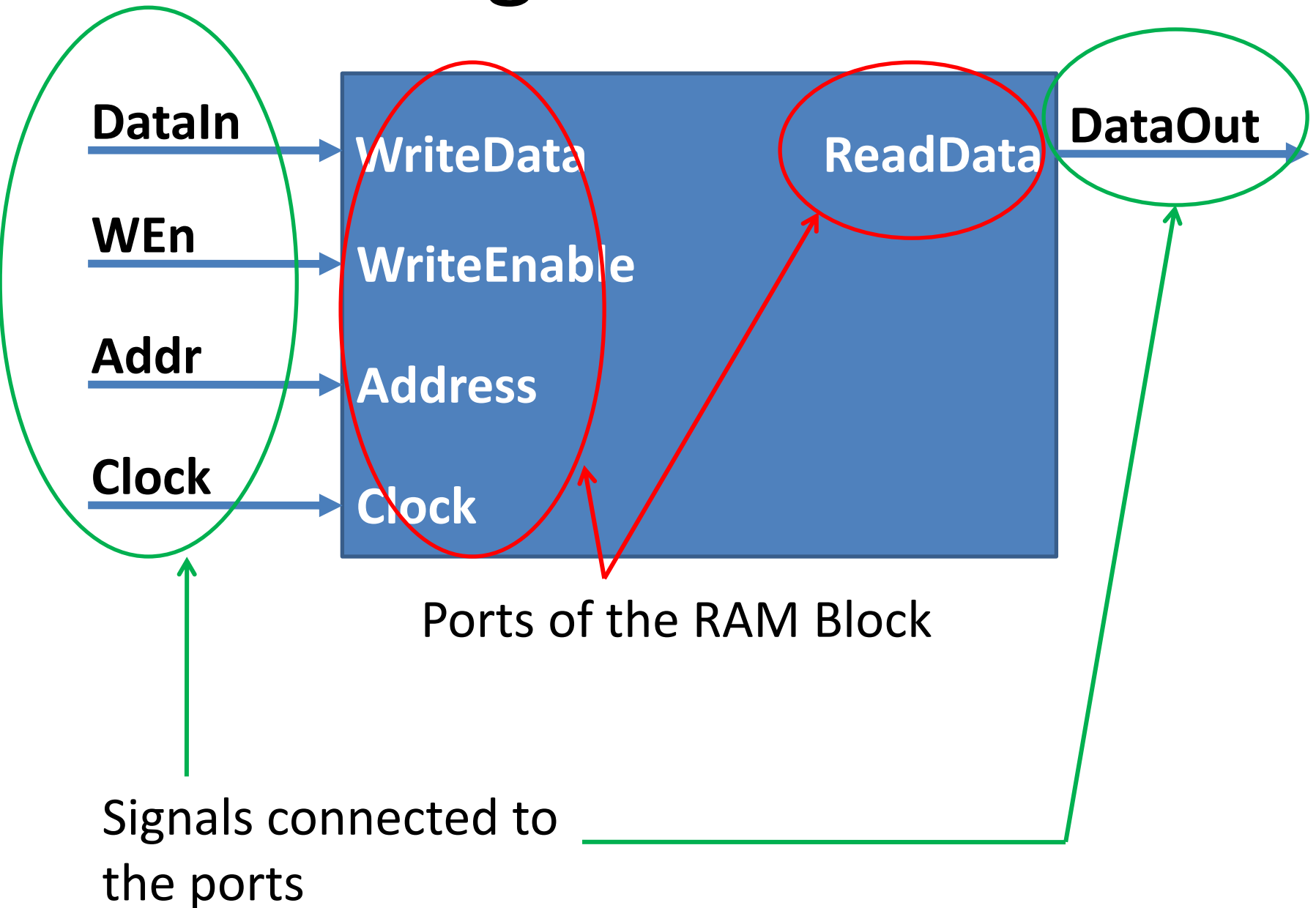


Single Port RAM

 


Write Single Word

Single Port RAM

 


Write Two Words

Single Port RAM

 


Write Two Words

Single Port RAM

 

Read Single Word

Single Port RAM

 

Read Two Words

VHDL for Single Port RAM

```
library IEEE;  
use IEEE.STD_LOGIC_1164.all;  
use ieee.numeric_std.all;
```

VHDL for Single Port RAM

```
entity SinglePortRAM is
    generic(
        Dwidth : integer;
        Awidth : integer
    );
    port(
        Clock      : in  std_logic;
        WriteData   : in  std_logic_vector(Dwidth - 1 downto 0);
        ReadData    : out std_logic_vector(Dwidth - 1 downto 0);
        Address     : in  std_logic_vector(Awidth - 1 downto 0);
        WriteEnable : in  std_logic
    );
end SinglePortRAM ;
```

VHDL for Single Port RAM

```
entity SinglePortRAM is
    generic(
        Dwidth : integer;
        Awidth : integer
    );
    port(
        Clock      : in  std_logic;
        WriteData   : in  std_logic_vector(Dwidth - 1 downto 0);
        ReadData    : out std_logic_vector(Dwidth - 1 downto 0);
        Address     : in  std_logic_vector(Awidth - 1 downto 0);
        WriteEnable : in  std_logic
    );
end SinglePortRAM ;
```


VHDL for Single Port RAM

```
entity SinglePortRAM is
    generic(
        Dwidth : integer;
        Awidth : integer
    );
    port(
        Clock      : in  std_logic;
        WriteData   : in  std_logic_vector(Dwidth - 1 downto 0);
        ReadData    : out std_logic_vector(Dwidth - 1 downto 0);
        Address     : in  std_logic_vector(Awidth - 1 downto 0);
        WriteEnable : in  std_logic
    );
end SinglePortRAM ;
```

VHDL for Single Port RAM

architecture rtl of SinglePortRAM is

VHDL for Single Port RAM

architecture rtl of SinglePortRAM is

-- Build a 2D array type for the RAM

type **memory_t** is array(0 to 2**Awidth -1) of
std_logic_vector((Dwidth-1) downto 0);

VHDL for Single Port RAM

```
architecture rtl of SinglePortRAM is
    -- Build a 2D array type for the RAM
    type memory_t is array(0 to 2**Awidth -1 ) of
        std_logic_vector((Dwidth-1) downto 0);
    -- Declare the RAM signal
    signal MyRam : memory_t ;
begin
```

VHDL for Single Port RAM

```
architecture rtl of SinglePortRAM is
    -- Build a 2D array type for the RAM
    type memory_t is array(0 to 2**Awidth -1 ) of
        std_logic_vector((Dwidth-1) downto 0);
    -- Declare the RAM signal
    signal MyRam : memory_t ;
begin
    RAMProcess : process (Clock) begin
```

VHDL for Single Port RAM

```
architecture rtl of SinglePortRAM is
    -- Build a 2D array type for the RAM
    type memory_t is array(0 to 2**Awidth -1 ) of
        std_logic_vector((Dwidth-1) downto 0);
    -- Declare the RAM signal
    signal MyRam : memory_t ;
begin
    RAMProcess : process (Clock) begin
        if rising_edge(Clock) then
```

VHDL for Single Port RAM

architecture rtl of SinglePortRAM is

-- Build a 2D array type for the RAM

type **memory_t** is array(0 to 2**Awidth -1) of
std_logic_vector((Dwidth-1) downto 0);

-- Declare the RAM signal

signal MyRam : **memory_t** ;

begin

RAMProcess : **process** (Clock) **begin**

if rising_edge(Clock) **then**

if WriteEnable = '1' **then**

MyRam (to_integer(unsigned(Address))) <= WriteData;

end if;

VHDL for Single Port RAM

architecture rtl of SinglePortRAM is

-- Build a 2D array type for the RAM

type **memory_t** is array(0 to 2**Awidth -1) of
std_logic_vector((Dwidth-1) downto 0);

-- Declare the RAM signal

signal MyRam : **memory_t** ;

begin

RAMProcess : **process** (Clock) **begin**

if rising_edge(Clock) **then**

if WriteEnable = '1' **then**

MyRam (to_integer(unsigned(Address))) <= WriteData;


end if;

ReadData <= MyRam(to_integer(unsigned(Address)));


VHDL for Single Port RAM

```
architecture rtl of SinglePortRAM is
    -- Build a 2D array type for the RAM
    type memory_t is array(0 to 2**Awidth -1 ) of
        std_logic_vector((Dwidth-1) downto 0);
    -- Declare the RAM signal
    signal MyRam : memory_t ;
begin
    RAMProcess : process (Clock) begin
        if rising_edge(Clock) then
            if WriteEnable = '1' then
                MyRam (to_integer(unsigned(Address))) <= WriteData;
            end if;
            ReadData <= MyRam(to_integer(unsigned(Address)));
        end if;
    end process;
end rtl;
```


Dual Port RAM

 

Dual Port RAM

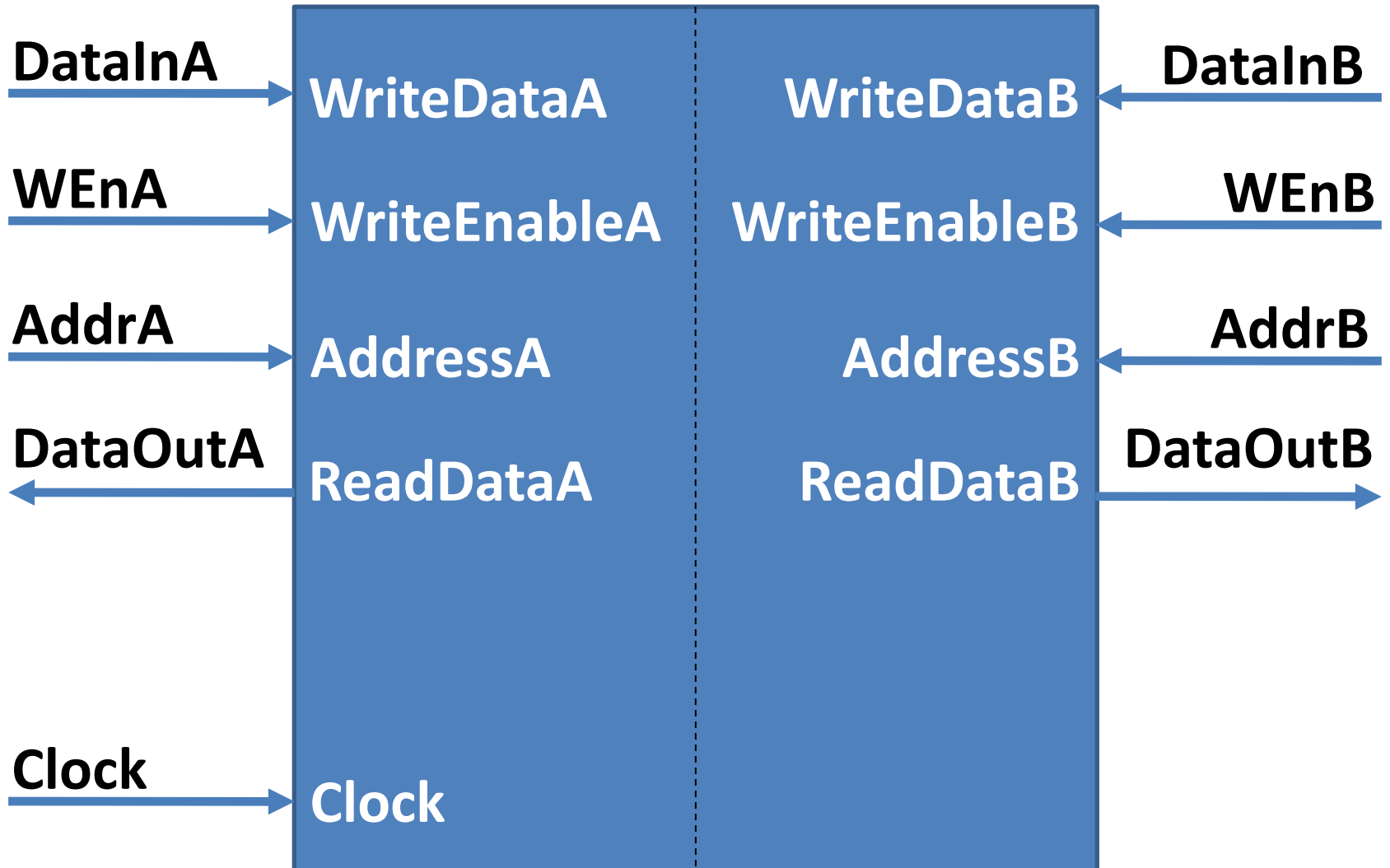

Dual Port RAM

 

VHDL for Dual Port RAM

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.all;
```

```
use ieee.numeric_std.all;
```

VHDL for Dual Port RAM

```
entity DualPortRAM is
```

```
  generic(
```

```
    Dwidth : integer;
```

```
    Awidth : integer
```

```
  );
```

```
  port(
```

```
    Clock           : in  std_logic;
```

```
    WriteDataA      : in  std_logic_vector(Dwidth - 1 downto 0);
```

```
    ReadDataA       : out std_logic_vector(Dwidth - 1 downto 0);
```

```
    AddressA        : in  std_logic_vector(Awidth - 1 downto 0);
```

```
    WriteEnableA    : in  std_logic;
```

```
    WriteDataB      : in  std_logic_vector(Dwidth - 1 downto 0);
```

```
    ReadDataB       : out std_logic_vector(Dwidth - 1 downto 0);
```

```
    AddressB        : in  std_logic_vector(Awidth - 1 downto 0);
```

```
    WriteEnableB    : in  std_logic
```

```
  );
```

```
end DualPortRAM ;
```

These ports
implement
the 1st “port”
which I have
called A.

These ports
implement the
2nd “port”
which I have
called B.

VHDL for Single Port RAM

```
architecture rtl of DualPortRAM is
    -- Build a 2D array type for the RAM
    type memory_t is array(0 to 2**Awidth -1 ) of std_logic_vector((Dwidth-1) downto 0);
    -- Declare the RAM signal
    signal MyRam : memory_t ;
begin
```

VHDL for Single Port RAM

```
architecture rtl of DualPortRAM is
    -- Build a 2D array type for the RAM
    type memory_t is array(0 to 2**Awidth -1 ) of std_logic_vector((Dwidth-1) downto 0);
    -- Declare the RAM signal
    signal MyRam : memory_t ;
begin
    RAMProcess : process (Clock) begin
        if rising_edge(Clock) then
```


VHDL for Single Port RAM

architecture rtl of DualPortRAM is

-- Build a 2D array type for the RAM

type **memory_t** is array(0 to 2**Awidth -1) of std_logic_vector((Dwidth-1) downto 0);

-- Declare the RAM signal

signal MyRam : **memory_t**;

begin

RAMProcess : process (Clock) begin

if rising_edge(Clock) then

if WriteEnableA = '1' then

MyRam (to_integer(unsigned(AddressA))) <= WriteDataA;

end if;

ReadDataA <= MyRam(to_integer(unsigned(AddressA)));

VHDL for Single Port RAM

architecture rtl of DualPortRAM is

-- Build a 2D array type for the RAM

type **memory_t** is array(0 to 2**Awidth -1) of std_logic_vector((Dwidth-1) downto 0);

-- Declare the RAM signal

signal MyRam : **memory_t**;

begin

RAMProcess : **process** (Clock) **begin**

if rising_edge(Clock) **then**

if WriteEnableA = '1' **then**

MyRam (to_integer(unsigned(AddressA))) <= WriteDataA;

end if;

ReadDataA <= MyRam(to_integer(unsigned(AddressA)));

if WriteEnableB = '1' **then**

MyRam (to_integer(unsigned(AddressB))) <= WriteDataB;

end if;

ReadDataB <= MyRam(to_integer(unsigned(AddressB)));

VHDL for Single Port RAM

architecture rtl of DualPortRAM is

-- Build a 2D array type for the RAM

type **memory_t** is array(0 to 2**Awidth -1) of std_logic_vector((Dwidth-1) downto 0);

-- Declare the RAM signal

signal MyRam : **memory_t**;

begin

RAMProcess : process (Clock) begin

if rising_edge(Clock) then

if WriteEnableA = '1' then

MyRam (to_integer(unsigned(AddressA))) <= WriteDataA;

end if;

ReadDataA <= MyRam(to_integer(unsigned(AddressA)));

if WriteEnableB = '1' then

MyRam (to_integer(unsigned(AddressB))) <= WriteDataB;

end if;

ReadDataB <= MyRam(to_integer(unsigned(AddressB)));

end if;


end process;


end rtl;


Finite State Machines


IDLE

Heater OFF
ALL LEDs OFF

 

 

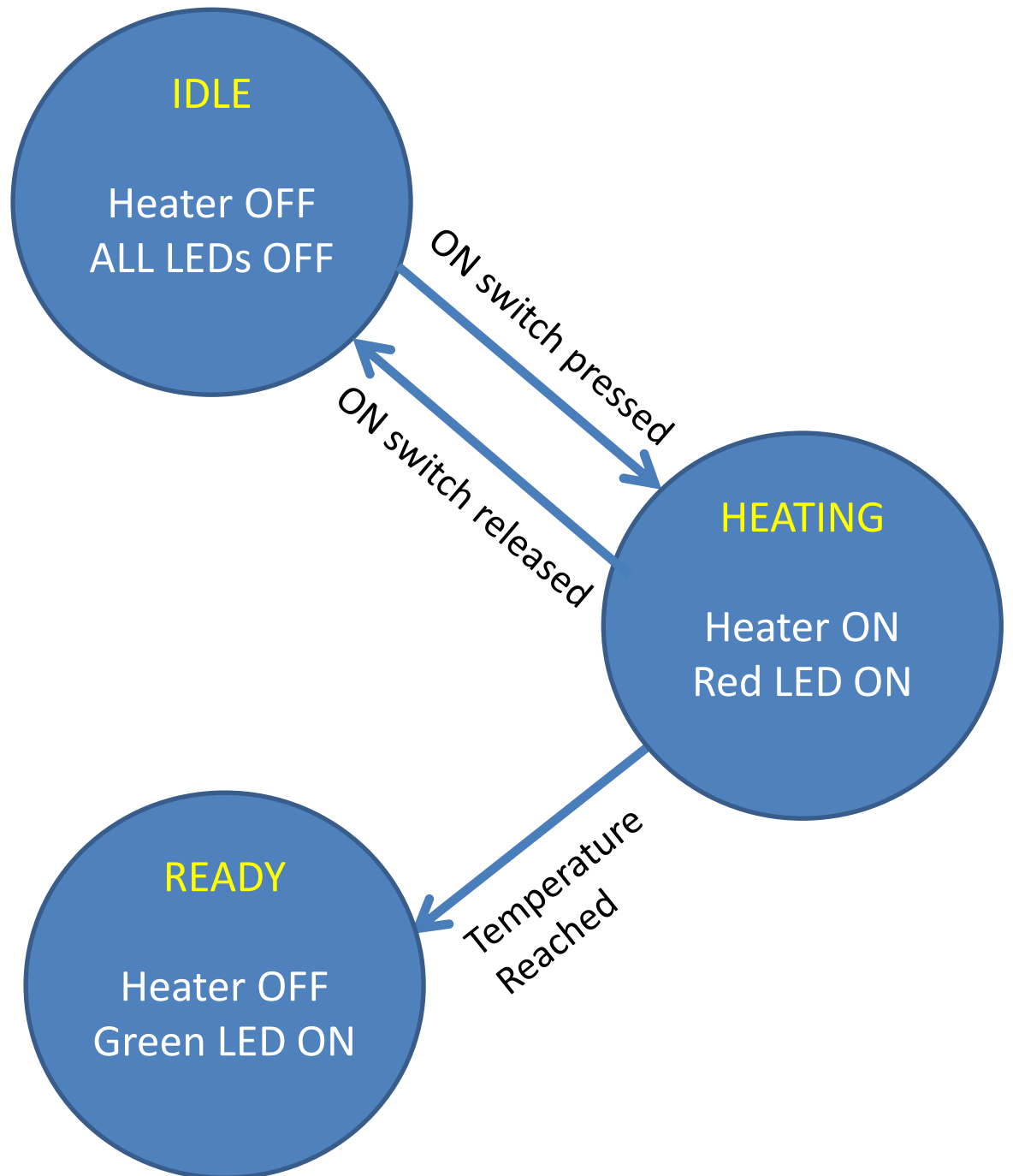

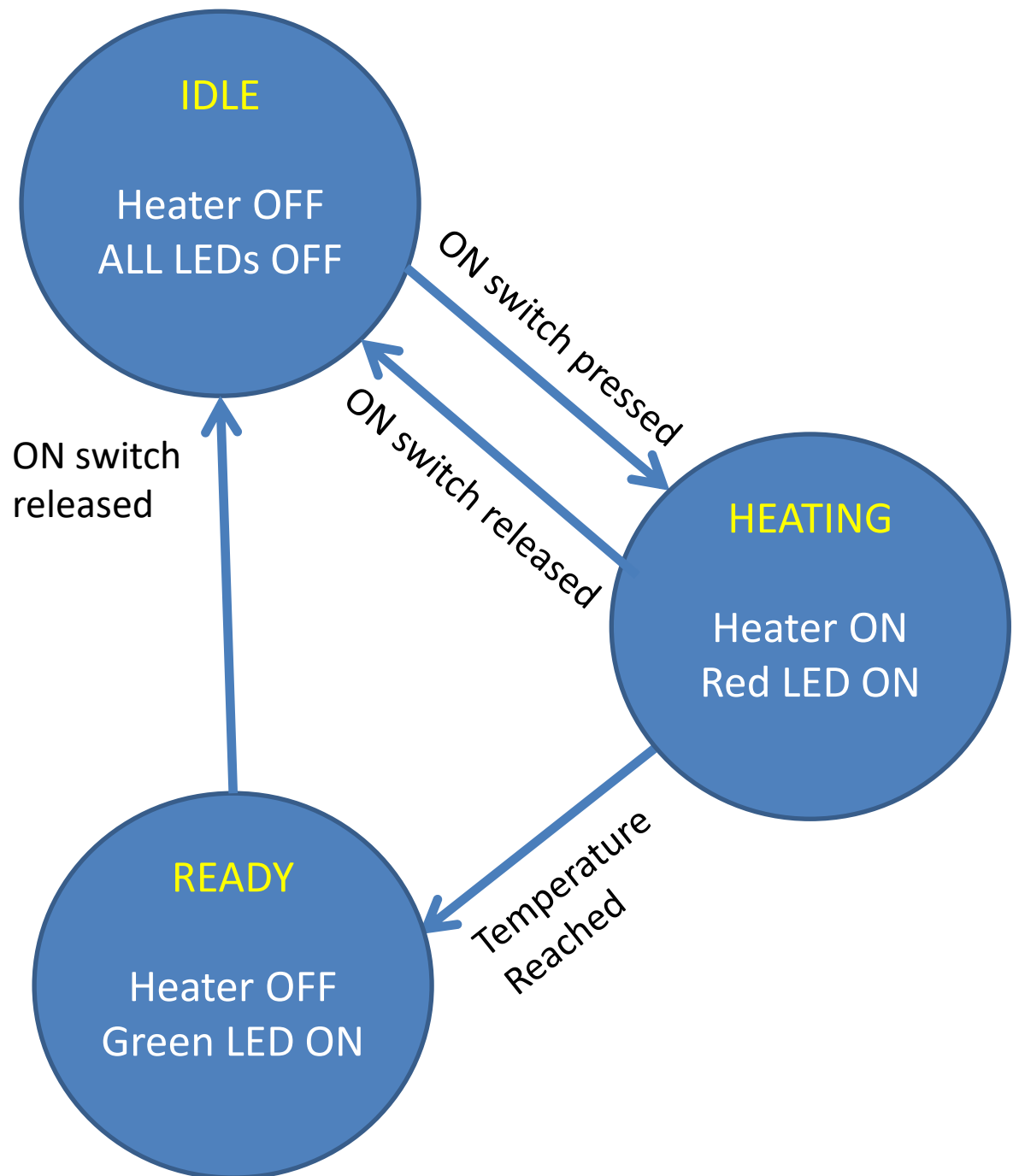

```
library IEEE;  
use IEEE.STD_LOGIC_1164.all;
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity HeaterFSM is
    port(
        Clk          : in std_logic;
        Rst          : in std_logic;
        Sw           : in std_logic;
        Temp         : in std_logic;
        Heater       : out std_logic;
        RedLED       : out std_logic;
        GreenLED     : out std_logic
    );
end entity;
```

architecture rtl of HeaterFSM is

```
architecture rtl of HeaterFSM is
```

```
    type FSMStateType is (IDLE, HEATING, READY);
```

```
architecture rtl of HeaterFSM is
```

```
    type FSMStateType is (IDLE, HEATING, READY);
```

```
    signal State : FSMStateType;
```

```
begin
```

```
architecture rtl of HeaterFSM is
```

```
    type FSMStateType is (IDLE, HEATING, READY);
```

```
    signal State : FSMStateType;
```

```
begin
```

```
FSMProcess: process(rst , clk)
begin
    if rst = '1' then
        GreenLED <= '0';
        RedLED <= '0';
        Heater <= '0';
        State <= IDLE;
    elsif rising_edge(clk) then
```



```
FSMProcess: process(rst , clk)
begin
    if rst = '1' then
        GreenLED <= '0';
        RedLED <= '0';
        Heater <= '0';
        State <= IDLE;
    elsif rising_edge(clk) then
        case State is
```

```
FSMProcess: process(rst , clk)
```

```
begin
```

```
    if rst = '1' then
```

```
        GreenLED <= '0';
```

```
        RedLED <= '0';
```

```
        Heater <= '0';
```

```
        State <= IDLE;
```

```
    elsif rising_edge(clk) then
```

```
        case State is
```

```
            when IDLE =>
```

```
                GreenLED <= '0';
```

```
                RedLED <= '0';
```

```
                Heater <= '0';
```

```
                if Sw = '1' then
```

```
                    State <= HEATING;
```

```
                end if;
```

```
FSMProcess: process(rst , clk)
```

```
begin
```

```
    if rst = '1' then
```

```
        GreenLED <= '0';
```

```
        RedLED <= '0';
```

```
        Heater <= '0';
```

```
        State <= IDLE;
```

```
    elsif rising_edge(clk) then
```

```
        case State is
```

```
            when IDLE =>
```

```
                GreenLED <= '0';
```

```
                RedLED <= '0';
```

```
                Heater <= '0';
```

```
                if Sw = '1' then
```

```
                    State <= HEATING;
```

```
                end if;
```

```
            when HEATING =>
```

```
                RedLED <= '1';
```

```
                Heater <= '1';
```

```
            if Sw = '0' then
```

```
                State <= IDLE ;
```

```
            elsif Temp = '1' then
```

```
                State <= READY ;
```

```
            end if;
```

```
FSMProcess: process(rst , clk)
```

```
begin
```

```
    if rst = '1' then
```

```
        GreenLED <= '0';
```

```
        RedLED <= '0';
```

```
        Heater <= '0';
```

```
        State <= IDLE;
```

```
    elsif rising_edge(clk) then
```

```
        case State is
```

```
            when IDLE =>
```

```
                GreenLED <= '0';
```

```
                RedLED <= '0';
```

```
                Heater <= '0';
```

```
                if Sw = '1' then
```

```
                    State <= HEATING;
```

```
                end if;
```

```
            when HEATING =>
```

```
                RedLED <= '1';
```

```
                Heater <= '1';
```

```
                if Sw = '0' then
```

```
                    State <= IDLE ;
```

```
                elsif Temp = '1' then
```

```
                    State <= READY ;
```

```
                end if;
```

```
            when READY =>
```

```
                RedLED <= '0';
```

```
                GreenLED <= '1';
```

```
                Heater <= '0';
```

```
                if Sw = '0' then
```

```
                    State <= IDLE ;
```

```
                end if;
```

```
FSMProcess: process(rst , clk)
```

```
begin
```

```
    if rst = '1' then
```

```
        GreenLED <= '0';
```

```
        RedLED <= '0';
```

```
        Heater <= '0';
```

```
        State <= IDLE;
```

```
    elsif rising_edge(clk) then
```

```
        case State is
```

```
            when IDLE =>
```

```
                GreenLED <= '0';
```

```
                RedLED <= '0';
```

```
                Heater <= '0';
```

```
                if Sw = '1' then
```

```
                    State <= HEATING;
```

```
                end if;
```

```
            when HEATING =>
```

```
                RedLED <= '1';
```

```
                Heater <= '1';
```

```
                if Sw = '0' then
```

```
                    State <= IDLE ;
```

```
                elsif Temp = '1' then
```

```
                    State <= READY ;
```

```
                end if;
```

```
            when READY =>
```

```
                RedLED <= '0';
```

```
                GreenLED <= '1';
```

```
                Heater <= '0';
```

```
                if Sw = '0' then
```

```
                    State <= IDLE ;
```

```
                end if;
```

```
            when others => State <= IDLE ;
```

```
        end case;
```

```
FSMProcess: process(rst , clk)
```

```
begin
```

```
    if rst = '1' then
```

```
        GreenLED <= '0';
```

```
        RedLED <= '0';
```

```
        Heater <= '0';
```

```
        State <= IDLE;
```

```
    elsif rising_edge(clk) then
```

```
        case State is
```

```
            when IDLE =>
```

```
                GreenLED <= '0';
```

```
                RedLED <= '0';
```

```
                Heater <= '0';
```

```
                if Sw = '1' then
```

```
                    State <= HEATING;
```

```
                end if;
```

```
            when HEATING =>
```

```
                RedLED <= '1';
```

```
                Heater <= '1';
```

```
                if Sw = '0' then
```

```
                    State <= IDLE ;
```

```
                elsif Temp = '1' then
```

```
                    State <= READY ;
```

```
                end if;
```

```
            when READY =>
```

```
                RedLED <= '0';
```

```
                GreenLED <= '1';
```

```
                Heater <= '0';
```

```
                if Sw = '0' then
```

```
                    State <= IDLE ;
```

```
                end if;
```

```
            when others => State <= IDLE ;
```

```
        end case;
```

```
    end if;
```

```
End process;
```

```
End rtl;
```

Recommendations :

Recommendations :

- Use a Registered Process with a Reset.

Recommendations :

- Use a Synchronous Process with a Reset.
- Create an enumerated data type to define states.

Recommendations :

- Use a Synchronous Process with a Reset.
- Create an enumerated data type to define states.
 - Use meaningful names for the states.

Recommendations :

- Use a Synchronous Process with a Reset.
- Create an enumerated data type to define states.
 - Use meaningful names for the states.
- Use a CASE statement to :
 - Implement the next state encoder.
 - Implement the output decoder encoder.

Recommendations :

- Use a Synchronous Process with a Reset.
- Create an enumerated data type to define states.
 - Use meaningful names for the states.
- Use a CASE statement to :
 - Implement the next state encoder.
 - Implement the output decoder encoder.
- Best to have registered outputs.

Recommendations :

- Use a Synchronous Process with a Reset.
- Create an enumerated data type to define states.
 - Use meaningful names for the states.
- Use a CASE statement to :
 - Implement the next state encoder.
 - Implement the output decoder encoder.
- Best to have registered outputs.
- Use “When Others” to return to a default state (in the event of entering an illegal state)

Good Design Practice 1

Code Readability

- Use meaningful names for signals, processes, generics, constants and entities.
- Make use of indentation to improve readability.
- Indent you code using :
 - Using the tab characters.
 - Or using spaces characters (typically 4 spaces)
- Text editors (such as notepad++ and Intel Quartus) can be configured to use either tabs or spaces.
- Disadvantage with using tabs :
 - Indentation may look wrong when files are opened with other editors.

No Indentation

```
TestProcess : process (Reset, Clk)
begin
  if Reset = '1' then
    Output <= 0;
  elsif rising_edge(Clk) then
    if A = '1' then
      Output <= 1;
    elsif B = '1' then
      Output <= 2;
    else
      Output <= 3;
    end if;
  end if;
end process;
```


With Indentation

```
TestProcess : process(Reset, Clk)
begin
    if Reset = '1' then
        Output <= 0;
    elsif rising_edge(Clk) then
        if A = '1' then
            Output <= 1;
        elsif B = '1' then
            Output <= 2;
        else
            Output <= 3;
        end if;
    end if;
end process;
```

Avoid Creating Latches

- Watch out for accidental latch creation inside combinational processes.
- Only a problem when there are conditional statements (if then / case).
- Make sure the outputs are defined in all possible cases.


Do Not Generate Clocks Using Logic

Do Not Generate Clocks Using Logic

- Suppose our FPGA has a 50MHz clock input and we want to generate a 25MHz internal clock.


Do Not Generate Clocks Using Logic

 - Suppose our FPGA has a 50MHz clock input and we want to generate a 25MHz internal clock.




Do Not Generate Clocks Using Logic

 - Suppose our FPGA has a 50MHz clock input and we want to generate a 25MHz internal clock.



Do Not Generate Clocks Using Logic

 - Suppose our FPGA has a 50MHz clock input and we want to generate a 25MHz internal clock.




Do Not Generate Clocks Using Logic

- Using a clocks generated by FPGA logic results in slower designs.
- Because FPGA will be forced to use non-global routing resources to some degree.
- These paths have much higher skew resulting in sub-optimal timing performance.


Better Way To Generate Clocks

 - Suppose our FPGA has a 50MHz clock input and we want to generate a 25MHz internal clock.





Do Not Use Clock Gating

 - For the same reasons, do not use clock gating.





Do Not Use Clock Gating

  - For the same reasons, do not use clock gating.





Use Data Gating Instead

  - For the same reasons, do not use clock gating.






Use Data Gating Instead

  - For the same reasons, do not use clock gating.






Use Data Gating Instead
   
```
DataGatingExample : process(Reset, Clk_50MHz)
begin
    if Reset = '1' then
        Output <= '0';
    elsif rising_edge(Clk_50MHz) then
        if Enable = '1' then
            Output <= A;
        end if;
    end if;
end process;
```



Use Data Gating Instead
   
```
DataGatingExample : process(Reset, Clk_50MHz)
begin
    if Reset = '1' then
        Output <= '0';
    elsif rising_edge(Clk_50MHz) then
        if Enable = '1' then
            Output <= A;
        end if;
    end if;
end process;
```




Make Generous Use Of Registers

- FPGAs have plenty of registers.
- Using registers generously improves circuit timing performance.
- Register all inputs and outputs from ports.

Make Generous Use Of Registers

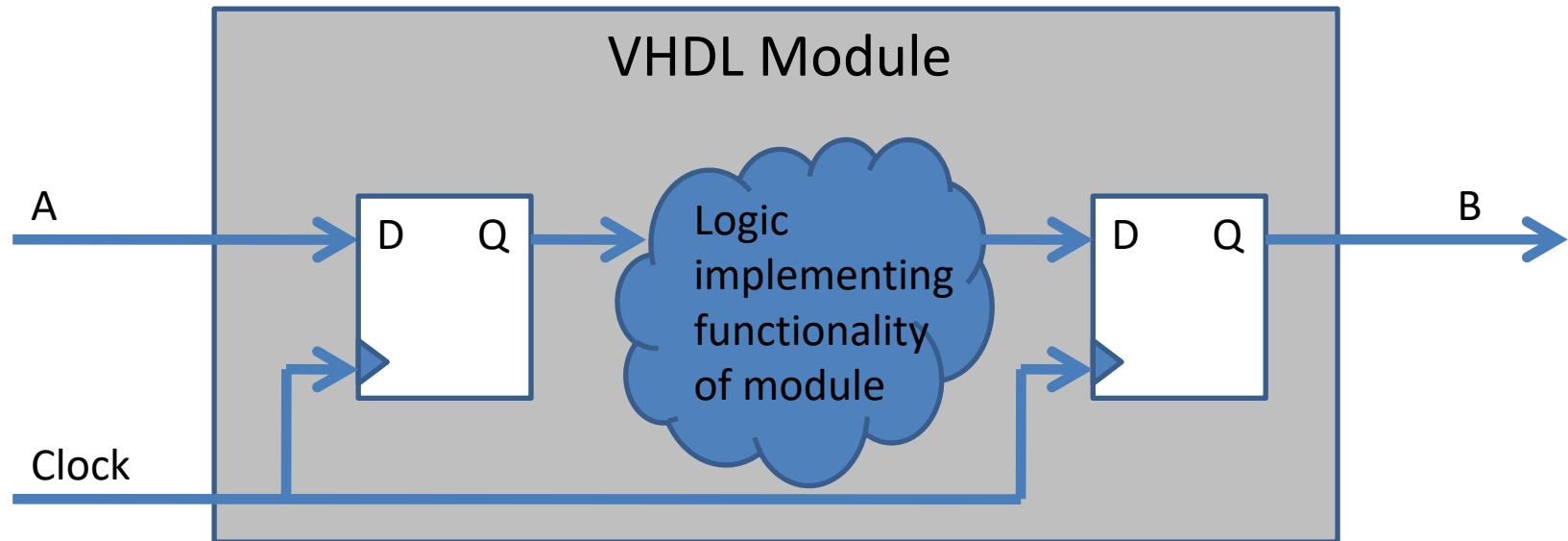
- Register all inputs and outputs ports of a VHDL module.



Pipelining

- Large combinational functions have big delays leading to a timing bottleneck.
- This leads to a slower FPGA design.
- Pipelining can be very effective in mitigating these delays and boost timing performance.
- Pipelining uses extra registers to break up a large combinational function.


Pipelining - Application

 

Logic delay = 10 ns


Pipelining - Application

Clock = 50 MHz

 


Pipelining - Application

Clock = 100 MHz

 


Pipelining - Application

Clock = 120 MHz

 

Pipelining - Application

 

Synchronous Systems

- Always design synchronous systems:
 - Having **registered** inputs and outputs.

Synchronous Systems

- Always design synchronous systems:
 - Having **registered** inputs and outputs.
- Why?
 - To avoid all sorts of timing glitches that are possible on a purely combinational system.

Topics


- Use meaningful names.
- Importance of indentation.
- Avoid creating latches.
- Avoid generate clocks using logic.
- Clock Gating vs Data Gating.
- Benefits of a register rich design.
- Benefits of a synchronous design.

Good Design Practice 2


Asynchronous Inputs

- Asynchronous inputs can change state at any point in time:
 - Push button input
 - RS232 Data
- These signals are not driven from a clock.
- We must make sure to synchronise **all** asynchronous inputs before using them.

2 Stage Synchronisation

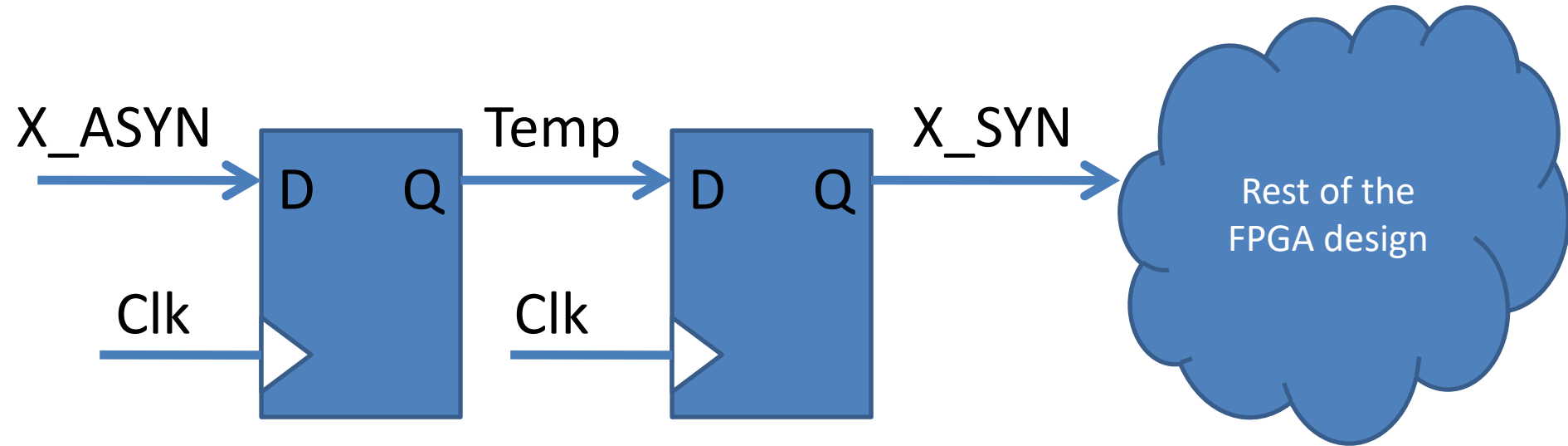

2 Stage Synchronisation

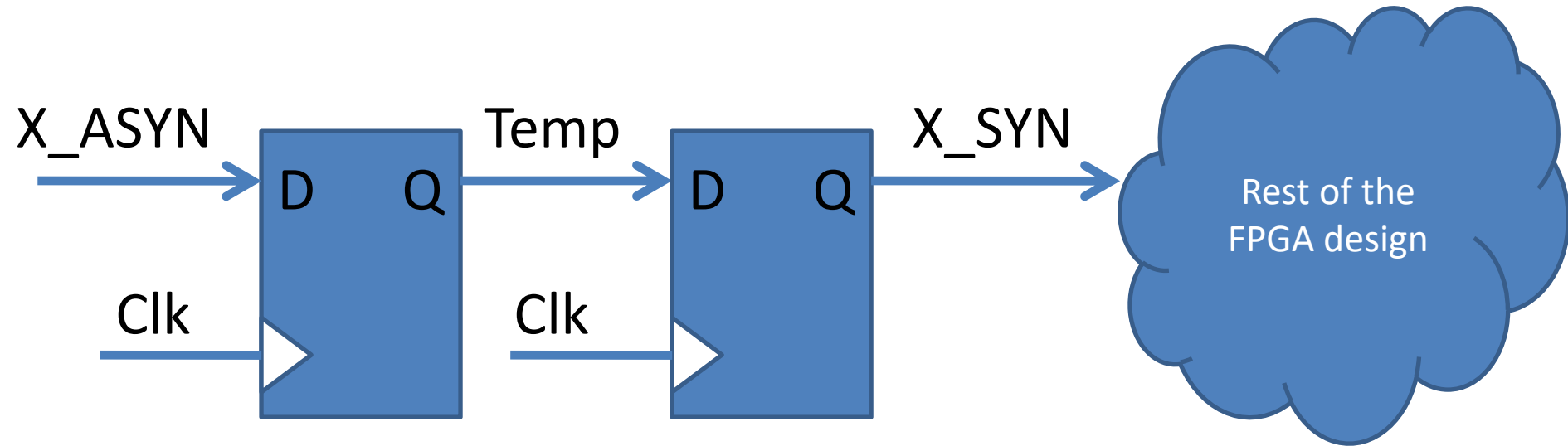

```
Synchronisation : process (Reset, Clk)
begin
    if Reset = '1' then
        Temp <= '0';
        X_SYN <= '0';
    elsif rising_edge(Clk) then
        Temp <= X_ASYN;
        X_SYN <= Temp;
    end if;
end process;
```

Crossing Clock Domains

- Similar to asynchronous inputs (danger of metastability)
- Usually, a signal or a bus going from one clock domain to another.
- The clock domain generating the signal can be running faster or slower than the receiving clock domain.

Crossing Clock Domains

- Ways of dealing with clock domain crossing:
 - 2 – stage synchronisation (identical to the asynchronous input case)
 - Using additional signals for hand-shaking.
 - Using FIFOs

Use Generics

- Makes modules reconfigurable.
- Allows for re-usable VHDL modules.
- Reduces code redundancy.
- Saves time in writing and testing code.

Initial Values


- Reset **all** outputs of a synchronous process using a reset :

```
TestProcess : process(Reset, Clk)
begin
    if Reset = '1' then
        Output <= 0; ←
    elsif rising_edge(Clk) then
        if A = '1' then
            Output <= 1;
        elsif B = '1' then
            Output <= 2;
        else
            Output <= 3;
        end if;
    end if;
end process;
```


Synchronised Reset De-Assertion

- Using a purely asynchronous reset can lead to problems.
- Reset signal takes different times to reach different parts within the FPGA (due to propagation delay).
- Therefore some registers of the FPGA will come out of reset slightly earlier than other parts.
- This has the potential to cause a glitch / bug.
- We must synchronise the de-assertion of the reset signal to avoid this type of fault.

Synchronised Reset De-Assertion

 

Synchronised Reset De-Assertion

 

```
ResetSync : process(Reset_In, Clk)
begin
    if Reset_In = '1' then
        Temp <= '1';
        Reset_Out <= '1';
    elsif rising_edge(Clk) then
        Temp <= '0';
        Reset_Out <= Temp;
    end if;
end process;
```

More On Clocks And Resets

- Route clocks and resets on global routing.
- Global routing has very low skew.
- Global routing allows signals to reach all registers in the FPGA almost at the same time.
- Use PLL to clean up the input clock.
- PLLs can reduce the effect of noise, ringing and reflections that can appear on the input clock signal.

Topics

- Dealing with Asynchronous inputs.
- Crossing clock domains.
- Reusable VHDL modules.
- Initialising signals.
- Synchronising the de-assertion of system reset.
- Route clocks and resets on global routing.
- Using PLL to clean clock

Test Benches


What is a Test Bench?

- VHDL modules are tested using Test benches.
- A Test Bench is also a VHDL module that we must develop.
- In a basic test bench we :
 - Generate input vectors.
 - Define checks on output vectors.
 - What kinds of tests we want to run.
 - How long we run the tests for.


Test Bench Model




Test Bench Model

 


Test Bench Model

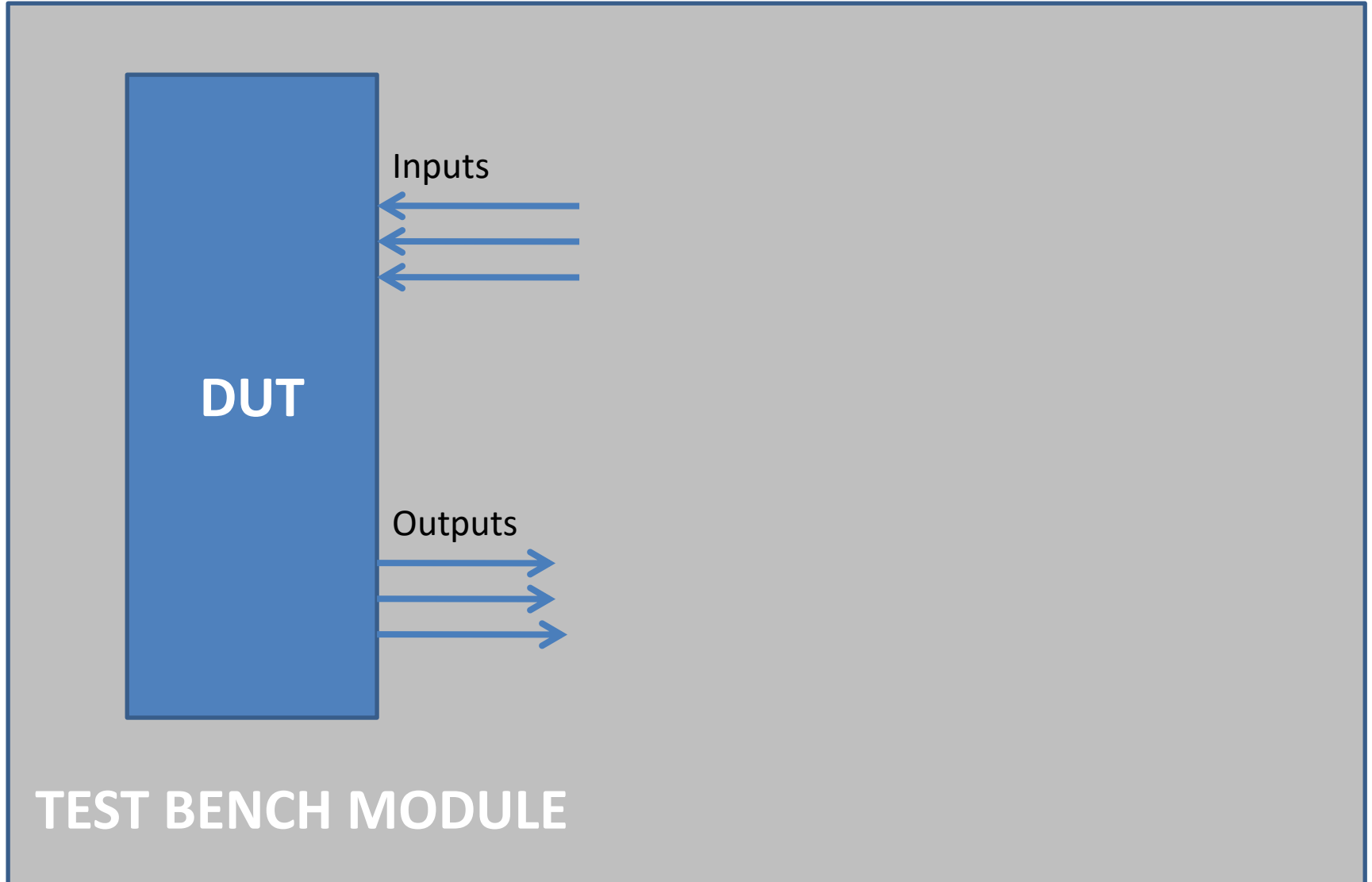

Test Bench Model

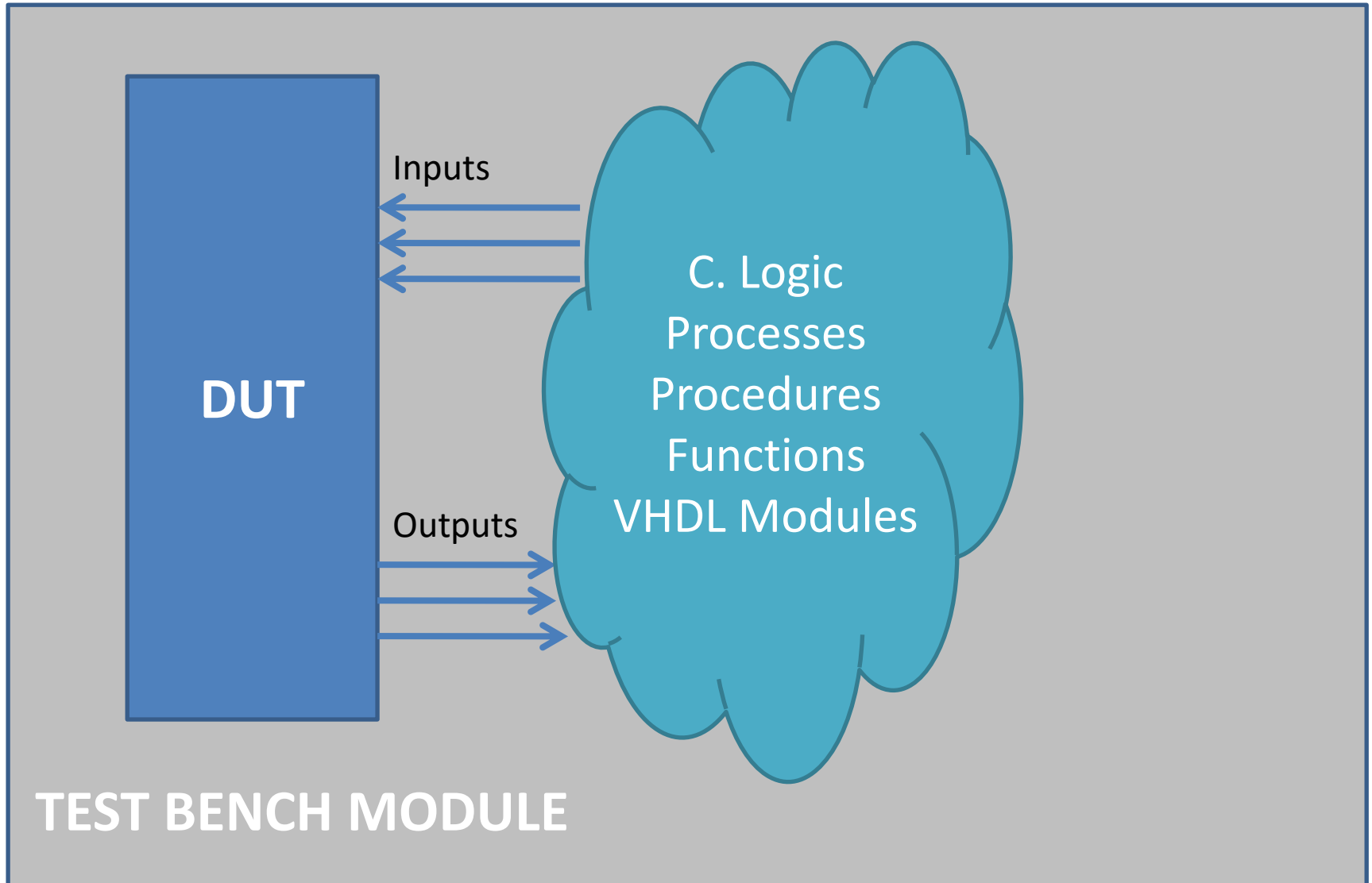

Test Bench Model

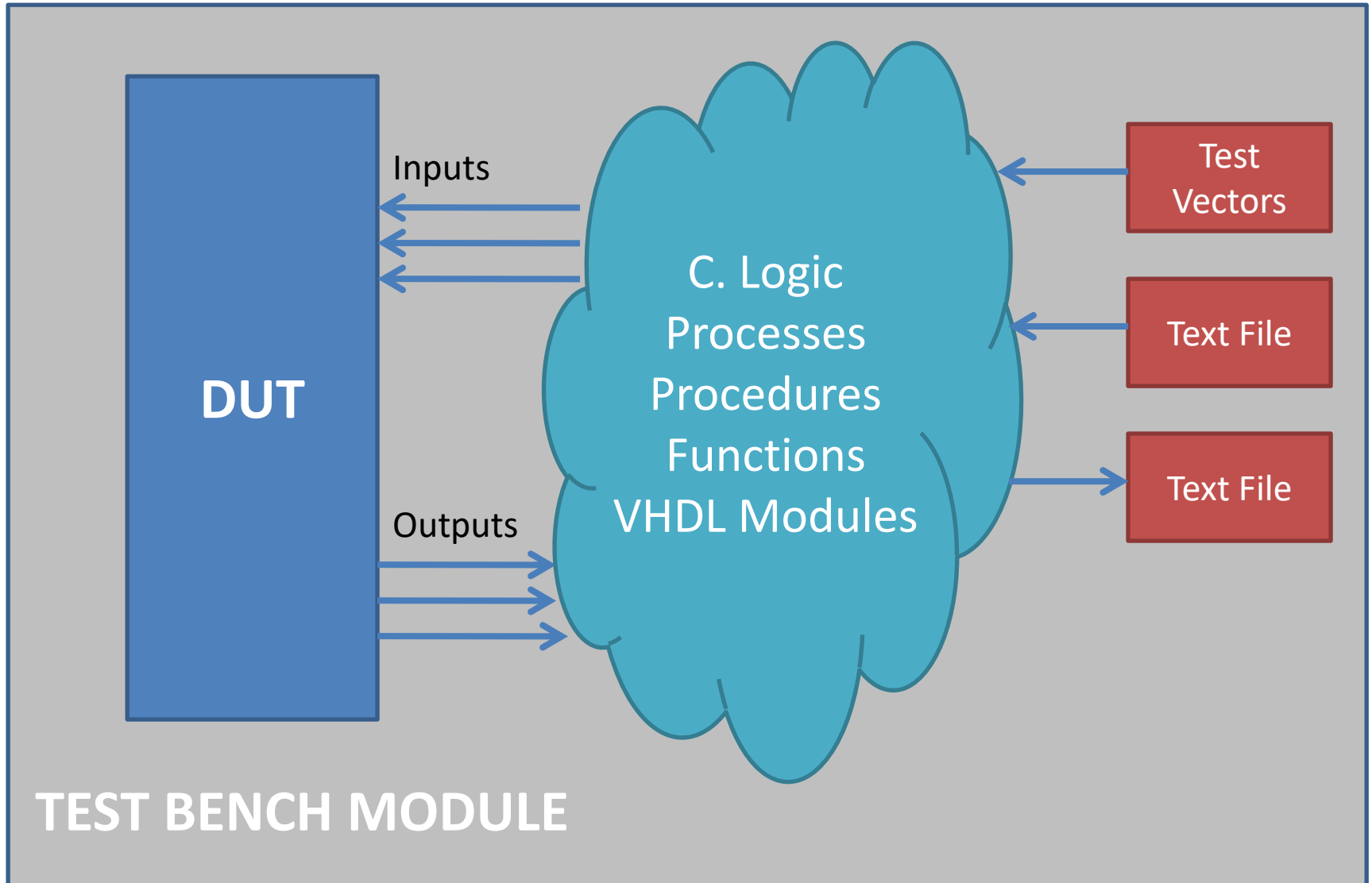

Generating Messages

- The Test Bench can print messages on the simulator console window.

Generating Messages

- The Test Bench can print messages on the simulator console window.

Syntax:

```
report message_string severity severity_level;
```


Generating Messages

- The Test Bench can print messages on the simulator console window.

Syntax:

```
report message_string severity severity_level;  
severity_level = note, warning, error, failure
```

Generating Messages

- The Test Bench can print messages on the simulator console window.

Syntax:

report message_string **severity** severity_level;

severity_level : note, warning, error, failure

e.g.:

report "This is a message"; -- **severity = note.**

Generating Messages

- The Test Bench can print messages on the simulator console window.

Syntax:

```
report message_string severity severity_level;
```

severity_level : note, warning, error, failure

e.g.:

```
report "This is a message"; -- severity = note.
```

```
report "This is a message" severity warning;
```

Assert Statement

- The assert statement tests a Boolean condition.
- If false, it outputs a message string to the simulator output console.

Assert Statement

- The assert statement tests a Boolean condition.
- If false, it outputs a message string to the simulator output console.

Syntax:

```
assert condition report string severity severity_level;
```

Assert Statement

- The assert statement tests a Boolean condition.
- If false, it outputs a message string to the simulator output console.

Syntax:

```
assert condition report string severity severity_level;
```

e.g.:

```
assert Overflow = '0'  
report "An overflow has occurred!" severity warning;
```

Using Text Files

- Must declare **Textio** package (“`use std.textio.all;`”)
- Allows for more complex testing.
- Input vectors can be read from text files.
- Output vectors can be written to text files.
- Data types stored in files can be anything (real numbers, strings, `std_logic_vectors`, integers etc).
- Basic operations with text files :
 - Declaration of a text file.
 - Opening and closing a file of a text file.
 - Reading and or writing to a file.

Declaring a Text File

Syntax :

```
file FileHandle : text;
```


Declaring a Text File

Syntax :

```
file FileHandle : text;
```

e.g.:

```
file File1 : text;
```

Declaring a Text File

Syntax :

`file` FileHandle : `text`;

e.g.:

`file` File1 : `text`;

Where to declare :

- Declarative region of the architecture
- Declarative region of a process

Opening a Text File

Syntax :

```
file_open(FileHandle, "FileName.txt", OpenMode);
```

Opening A Text File

Syntax :

```
file_open(FileHandle, "FileName.txt", OpenMode);
```

Open Mode :

1. read_Mode
2. write_Mode
3. append

Opening A Text File

Syntax :

```
file_open(FileHandle, "FileName.txt", OpenMode);
```

Open Mode :

1. read_Mode
2. write_Mode
3. append

E.g.:

```
file_open(File1, "InputVectors.txt", read_mode);
```

```
file_open(File2, "OutputVectors.txt", write_mode);
```

Closing A File

Syntax :

```
file_close(FileHandle);
```

Closing A File

Syntax :

```
file_close(FileHandle);
```

E.g.:

```
file_close(File1);
```

Test Benches

Writing Data to Text Files

Writing To a Text File

1. Open a text file in write mode.
2. Write to a line buffer:

```
write(LineBuffer, DataToWrite);
```

Writing To a Text File

1. Open a text file in write mode.

2. Write to a line buffer:

```
write(LineBuffer, DataToWrite);
```

3. Write line buffer to file:

```
writeline(FileHandle, LineBuffer);
```

Writing To a Text File

1. Open a text file in write mode.

2. Write to a line buffer:

```
write(LineBuffer, DataToWrite);
```

3. Write line buffer to file:

```
writeline(FileHandle, LineBuffer);
```

4. Close file.

```
1 library ieee;
2 use ieee.std_logic_1164.all;
3 use ieee.numeric_std.all;
4 library std;
5 use std.textio.all;
6
```

```
1 library ieee;
2 use ieee.std_logic_1164.all;
3 use ieee.numeric_std.all;
4 library std;
5 use std.textio.all;
6
7 entity TestBench is
8 end entity TestBench;
```

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4  library std;
5  use std.textio.all;
6
7  entity TestBench is
8  end entity TestBench;
9
10 architecture rtl of TestBench is
11
12     constant C : string := "This is a string";
13     signal X    : std_logic_vector(3 downto 0) := "1010";
14     signal Y    : integer:= 100;
15
16 begin
```

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4  library std;
5  use std.textio.all;
6
7  entity TestBench is
8  end entity TestBench;
9
10 architecture rtl of TestBench is
11
12     constant C : string := "This is a string";
13     signal X    : std_logic_vector(3 downto 0) := "1010";
14     signal Y    : integer:= 100;
15
16 begin
17
18     FileWriteProcess:process
19         file OutputFile          : text;
20         variable lineBuffer      : line;
21     begin
```

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4  library std;
5  use std.textio.all;
6
7  entity TestBench is
8  end entity TestBench;
9
10 architecture rtl of TestBench is
11
12     constant C : string := "This is a string";
13     signal X    : std_logic_vector(3 downto 0) := "1010";
14     signal Y    : integer:= 100;
15
16 begin
17
18     FileWriteProcess:process
19         file OutputFile          : text;
20         variable lineBuffer      : line;
21     begin
22         file_open(OutputFile, "OutputFile.txt",write_mode);
23

```



```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4  library std;
5  use std.textio.all;
6
7  entity TestBench is
8  end entity TestBench;
9
10 architecture rtl of TestBench is
11
12     constant C : string := "This is a string";
13     signal X    : std_logic_vector(3 downto 0) := "1010";
14     signal Y    : integer:= 100;
15
16 begin
17
18     FileWriteProcess:process
19         file OutputFile      : text;
20         variable lineBuffer   : line;
21     begin
22         file_open(OutputFile, "OutputFile.txt",write_mode);
23
24         write(lineBuffer,string'("Signal X is : "));

```

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4  library std;
5  use std.textio.all;
6
7  entity TestBench is
8  end entity TestBench;
9
10 architecture rtl of TestBench is
11
12     constant C : string := "This is a string";
13     signal X    : std_logic_vector(3 downto 0) := "1010";
14     signal Y    : integer:= 100;
15
16 begin
17
18     FileWriterProcess:process
19         file OutputFile      : text;
20         variable lineBuffer  : line;
21     begin
22         file_open(OutputFile, "OutputFile.txt",write_mode);
23
24         write(lineBuffer,string'("Signal X is : "));
25         write(lineBuffer,X);
```

```
1 library ieee;
2 use ieee.std_logic_1164.all;
3 use ieee.numeric_std.all;
4 library std;
5 use std.textio.all;
6
7 entity TestBench is
8 end entity TestBench;
9
10 architecture rtl of TestBench is
11
12     constant C : string := "This is a string";
13     signal X : std_logic_vector(3 downto 0) := "1010";
14     signal Y : integer:= 100;
15
16 begin
17
18     FileWriterProcess:process
19         file OutputFile : text;
20         variable lineBuffer : line;
21     begin
22         file_open(OutputFile, "OutputFile.txt",write_mode);
23
24         write(lineBuffer,string'("Signal X is : "));
25         write(lineBuffer,X);
26         writeline(OutputFile, lineBuffer);
```

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4  library std;
5  use std.textio.all;
6
7  entity TestBench is
8  end entity TestBench;
9
10 architecture rtl of TestBench is
11
12     constant C : string := "This is a string";
13     signal X    : std_logic_vector(3 downto 0) := "1010";
14     signal Y    : integer:= 100;
15
16 begin
17
18     FileWriterProcess:process
19         file OutputFile          : text;
20         variable lineBuffer      : line;
21     begin
22         file_open(OutputFile, "OutputFile.txt",write_mode);
23
24         write(lineBuffer,string'("Signal X is : "));
25         write(lineBuffer,X);
26         writeline(OutputFile, lineBuffer);
27
28         write(lineBuffer,string'("Signal Y is : "));
29         write(lineBuffer,Y);
30         writeline(OutputFile, lineBuffer);

```

```

1 library ieee;
2 use ieee.std_logic_1164.all;
3 use ieee.numeric_std.all;
4 library std;
5 use std.textio.all;
6
7 entity TestBench is
8 end entity TestBench;
9
10 architecture rtl of TestBench is
11
12     constant C : string := "This is a string";
13     signal X    : std_logic_vector(3 downto 0) := "1010";
14     signal Y    : integer:= 100;
15
16 begin
17
18     FileWriterProcess:process
19         file OutputFile          : text;
20         variable lineBuffer      : line;
21     begin
22         file_open(OutputFile, "OutputFile.txt",write_mode);
23
24         write(lineBuffer,string'("Signal X is : "));
25         write(lineBuffer,X);
26         writeline(OutputFile, lineBuffer);
27
28         write(lineBuffer,string'("Signal Y is : "));
29         write(lineBuffer,Y);
30         writeline(OutputFile, lineBuffer);
31
32         write(lineBuffer,string'("String C is : "));
33         write(lineBuffer,C);
34         writeline(OutputFile, lineBuffer);
35

```

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4  library std;
5  use std.textio.all;
6
7  entity TestBench is
8  end entity TestBench;
9
10 architecture rtl of TestBench is
11
12     constant C : string := "This is a string";
13     signal X    : std_logic_vector(3 downto 0) := "1010";
14     signal Y    : integer:= 100;
15
16 begin
17
18     FileWriterProcess:process
19         file OutputFile          : text;
20         variable lineBuffer      : line;
21     begin
22         file_open(OutputFile, "OutputFile.txt",write_mode);
23
24         write(lineBuffer,string'("Signal X is : "));
25         write(lineBuffer,X);
26         writeline(OutputFile, lineBuffer);
27
28         write(lineBuffer,string'("Signal Y is : "));
29         write(lineBuffer,Y);
30         writeline(OutputFile, lineBuffer);
31
32         write(lineBuffer,string'("String C is : "));
33         write(lineBuffer,C);
34         writeline(OutputFile, lineBuffer);
35
36         file_close(OutputFile);

```

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4  library std;
5  use std.textio.all;
6
7  entity TestBench is
8  end entity TestBench;
9
10 architecture rtl of TestBench is
11
12     constant C : string := "This is a string";
13     signal X    : std_logic_vector(3 downto 0) := "1010";
14     signal Y    : integer:= 100;
15
16 begin
17
18     FileWriterProcess:process
19         file OutputFile          : text;
20         variable lineBuffer      : line;
21     begin
22         file_open(OutputFile, "OutputFile.txt",write_mode);
23
24         write(lineBuffer,string'("Signal X is : "));
25         write(lineBuffer,X);
26         writeline(OutputFile, lineBuffer);
27
28         write(lineBuffer,string'("Signal Y is : "));
29         write(lineBuffer,Y);
30         writeline(OutputFile, lineBuffer);
31
32         write(lineBuffer,string'("String C is : "));
33         write(lineBuffer,C);
34         writeline(OutputFile, lineBuffer);
35
36         file_close(OutputFile);
37         wait;

```

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4  library std;
5  use std.textio.all;
6
7  entity TestBench is
8  end entity TestBench;
9
10 architecture rtl of TestBench is
11
12     constant C : string := "This is a string";
13     signal X    : std_logic_vector(3 downto 0) := "1010";
14     signal Y    : integer:= 100;
15
16 begin
17
18     FileWriterProcess:process
19         file OutputFile          : text;
20         variable lineBuffer      : line;
21     begin
22         file_open(OutputFile, "OutputFile.txt",write_mode);
23
24         write(lineBuffer,string'("Signal X is : "));
25         write(lineBuffer,X);
26         writeline(OutputFile, lineBuffer);
27
28         write(lineBuffer,string'("Signal Y is : "));
29         write(lineBuffer,Y);
30         writeline(OutputFile, lineBuffer);
31
32         write(lineBuffer,string'("String C is : "));
33         write(lineBuffer,C);
34         writeline(OutputFile, lineBuffer);
35
36         file_close(OutputFile);
37         wait;
38     end process;
39
40 end architecture rtl;

```



```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4  library std;
5  use std.textio.all;
6
7  entity TestBench is
8  end entity TestBench;
9
10 architecture rtl of TestBench is
11
12     constant C : string := "This is a string";
13     signal X    : std_logic_vector(3 downto 0) := "1010";
14     signal Y    : integer:= 100;
15
16 begin
17
18     FileWriterProcess:process
19         file OutputFile          : text;
20         variable lineBuffer      : line;
21     begin
22         file_open(OutputFile, "OutputFile.txt",write_mode);
23
24         write(lineBuffer,string'("Signal X is : "));
25         write(lineBuffer,X);
26         writeline(OutputFile, lineBuffer);
27
28         write(lineBuffer,string'("Signal Y is : "));
29         write(lineBuffer,Y);
30         writeline(OutputFile, lineBuffer);
31
32         write(lineBuffer,string'("String C is : "));
33         write(lineBuffer,C);
34         writeline(OutputFile, lineBuffer);
35
36         file_close(OutputFile);
37         wait;
38     end process;
39
40 end architecture rtl;

```

OutputFile.txt - Notepad

File Edit Format View Help

Signal X is : 1010
Signal Y is : 100
String C is : This is a string

Test Benches

Reading Data From Text Files

Reading From a Text File

1. Open a text file in read mode.

Reading From a Text File

1. Open a text file in read mode.
2. Read from a line from the text file:
`readline(FileHandle, LineBuffer);`

Reading From a Text File


1. Open a text file in read mode.
2. Read from a line from the text file:
`readline(FileHandle, LineBuffer);`
3. Read a data value from the line buffer to a signal:
`read(LineBuffer, SignalName);`

Reading From a Text File

1. Open a text file in read mode.
2. Read from a line from the text file:
`readline(FileHandle, LineBuffer);`
3. Read a data value from the line buffer to a signal:
`read(LineBuffer, SignalName);`
4. Repeat steps 2 and 3 until all lines of text file have been read.

Reading From a Text File

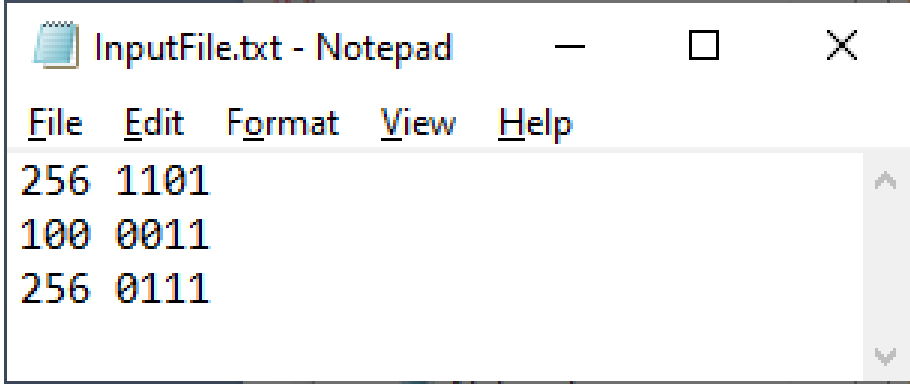
1. Open a text file in read mode.
2. Read from a line from the text file:
`readline(FileHandle, LineBuffer);`
3. Read a data value from the line buffer to a signal:
`read(LineBuffer, SignalName);`
4. Repeat steps 2 and 3 until all lines of text file have been read.
5. Close file.



InputFile.txt - Notepad

File Edit Format View Help

```
256 1101
100 0011
256 0111
```
 
```
40  FileReadProcess:process
41      file InputFile : text;
42      variable lineBuffer : line;
```

InputFile.txt - Notepad

File Edit Format View Help

256 1101
100 0011
256 0111


```
40  FileReaderProcess:process
41      file InputFile : text;
42      variable lineBuffer : line;
43      variable Char : character;
44      variable int : integer;
45      variable vector : std_logic_vector(3 downto 0) := "0000";
```

InputFile.txt - Notepad

File Edit Format View Help

256 1101
100 0011
256 0111
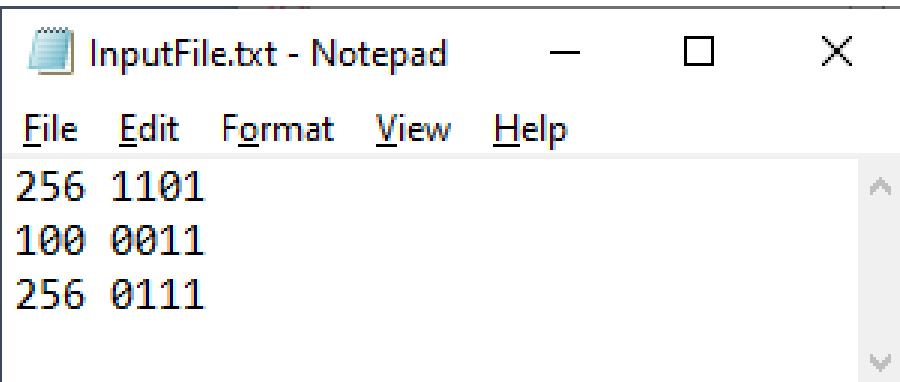
```
40 FileReadProcess:process
41     file InputFile : text;
42     variable lineBuffer : line;
43     variable Char : character;
44     variable int : integer;
45     variable vector : std_logic_vector(3 downto 0) := "0000";
46 begin
47     file_open(InputFile, "InputFile.txt", read_mode);
```



InputFile.txt - Notepad

File Edit Format View Help

256 1101
100 0011
256 0111

```
40  FileReadProcess:process
41      file InputFile : text;
42      variable lineBuffer : line;
43      variable Char : character;
44      variable int : integer;
45      variable vector : std_logic_vector(3 downto 0) := "0000";
46  begin
47      file_open(InputFile, "InputFile.txt", read_mode);
48
49      while not endfile(InputFile) loop
```

InputFile.txt - Notepad

File Edit Format View Help

```
256 1101
100 0011
256 0111
```

```
40 FileReadProcess:process
41     file InputFile : text;
42     variable lineBuffer : line;
43     variable Char : character;
44     variable int : integer;
45     variable vector : std_logic_vector(3 downto 0) := "0000";
46 begin
47     file_open(InputFile, "InputFile.txt", read_mode);
48
49     while not endfile(InputFile) loop
50         readline(InputFile, lineBuffer);
```

InputFile.txt - Notepad

File Edit Format View Help

```
256 1101
100 0011
256 0111
```

```
40 FileReadProcess:process
41     file InputFile : text;
42     variable lineBuffer : line;
43     variable Char : character;
44     variable int : integer;
45     variable vector : std_logic_vector(3 downto 0) := "0000";
46 begin
47     file_open(InputFile, "InputFile.txt", read_mode);
48
49     while not endfile(InputFile) loop
50         readline(InputFile, lineBuffer);
51         read(lineBuffer, int);
52         read(lineBuffer, Char);
53         read(lineBuffer, vector);
```

InputFile.txt - Notepad

File Edit Format View Help

256 1101
100 0011
256 0111

```
40 FileReadProcess:process
41     file InputFile : text;
42     variable lineBuffer : line;
43     variable Char : character;
44     variable int : integer;
45     variable vector : std_logic_vector(3 downto 0) := "0000";
46 begin
47     file_open(InputFile, "InputFile.txt", read_mode);
48
49     while not endfile(InputFile) loop
50         readline(InputFile, lineBuffer);
51         read(lineBuffer, int);
52         read(lineBuffer, Char);
53         read(lineBuffer, vector);
54     end loop;
```

InputFile.txt - Notepad

File Edit Format View Help

```
256 1101
100 0011
256 0111
```



```

40 FileReadProcess:process
41     file InputFile : text;
42     variable lineBuffer : line;
43     variable Char : character;
44     variable int : integer;
45     variable vector : std_logic_vector(3 downto 0) := "0000";
46 begin
47     file_open(InputFile, "InputFile.txt", read_mode);
48
49     while not endfile(InputFile) loop
50         readline(InputFile, lineBuffer);
51         read(lineBuffer, int);
52         read(lineBuffer, Char);
53         read(lineBuffer, vector);
54     end loop;
55
56     file_close(InputFile);

```

InputFile.txt - Notepad

File Edit Format View Help

```

256 1101
100 0011
256 0111

```


```
40 FileReadProcess:process
41     file InputFile : text;
42     variable lineBuffer : line;
43     variable Char : character;
44     variable int : integer;
45     variable vector : std_logic_vector(3 downto 0) := "0000";
46 begin
47     file_open(InputFile, "InputFile.txt", read_mode);
48
49     while not endfile(InputFile) loop
50         readline(InputFile, lineBuffer);
51         read(lineBuffer, int);
52         read(lineBuffer, Char);
53         read(lineBuffer, vector);
54     end loop;
55
56     file_close(InputFile);
57
58     wait;
59 end process;
```

InputFile.txt - Notepad

File Edit Format View Help

```
256 1101
100 0011
256 0111
```


```
40 FileReadProcess:process
41     file InputFile : text;
42     variable lineBuffer : line;
43     variable Char : character;
44     variable int : integer;
45     variable vector : std_logic_vector(3 downto 0) := "0000";
46 begin
47     file_open(InputFile, "InputFile.txt", read_mode);
48
49     while not endfile(InputFile) loop
50         readline(InputFile, lineBuffer);
51         read(lineBuffer, int);
52         read(lineBuffer, Char);
53         read(lineBuffer, vector);
54     end loop;
55
56     file_close(InputFile);
57
58     wait;
59 end process;
```

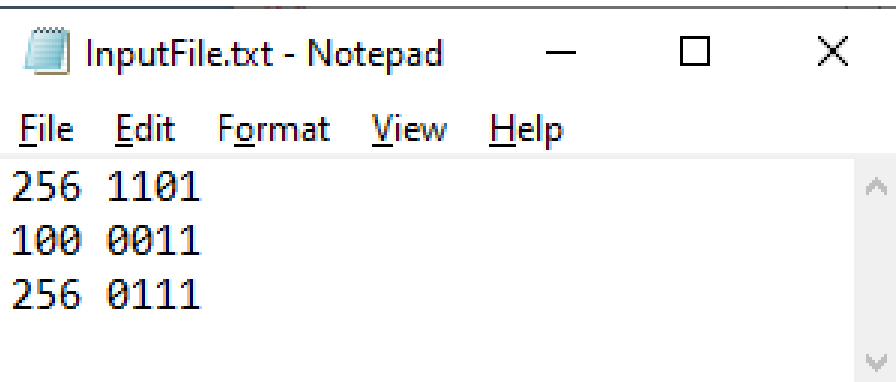


InputFile.txt - Notepad

File Edit Format View Help

```
256 1101
100 0011
256 0111
```

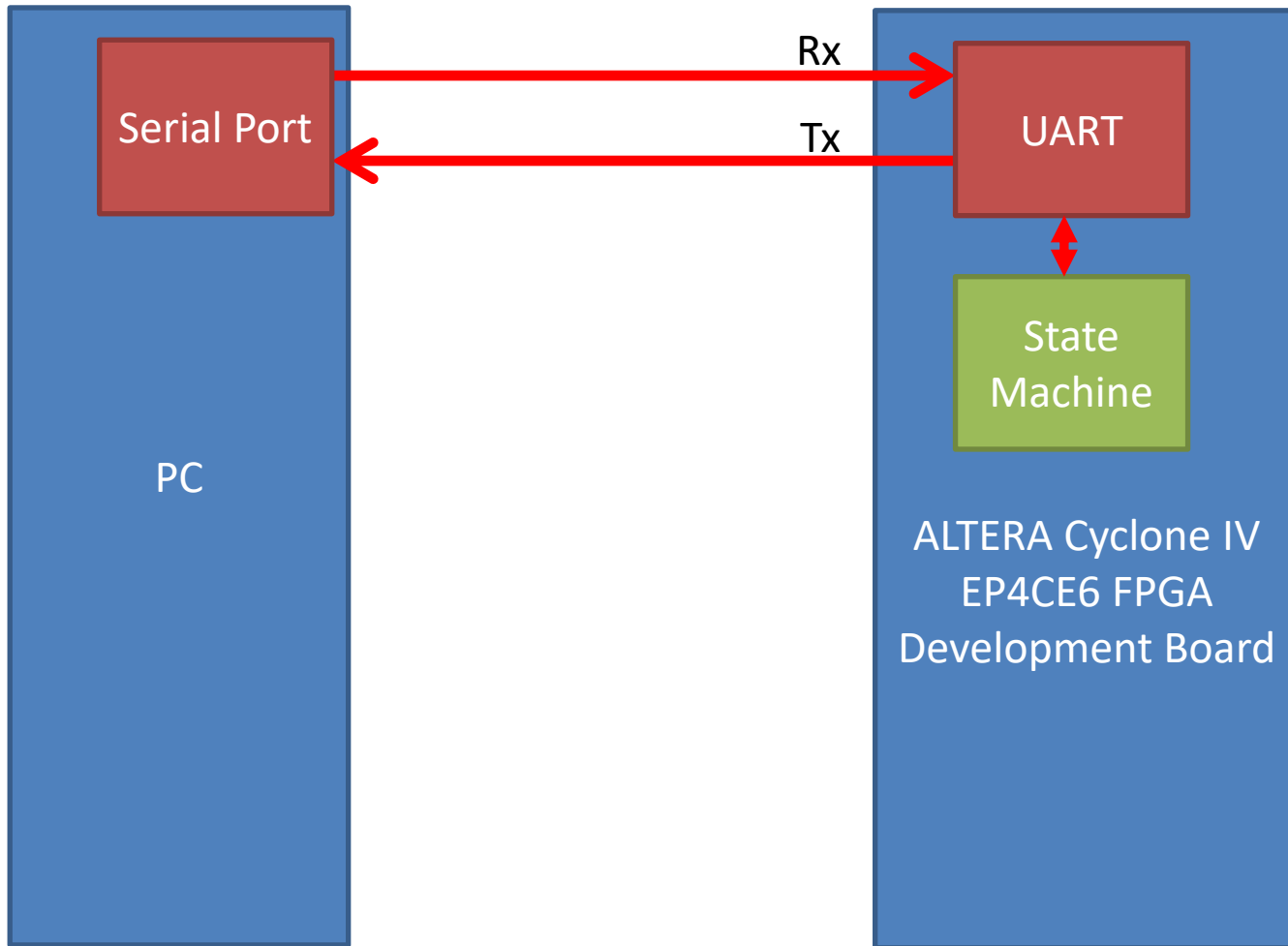

 

ALTERA Cyclone IV EP4CE6 FPGA Development Board Kit Altera EP4CE NIOSII FPGA Board and USB Downloader Infrared Controller

★★★★★ 19 Reviews | 8 answered questions ID: 1622523

£31.19 ~~£43.36~~ -28%

[Price alert](#)

\$20 for New User

♥ 309

Ship From:

CN

CZ

Shipping: £0.24

to United Kingdom via Banggood Express ▼

Shipping time: 8-10 business days ?

QTY:

- 1 +

Buy Now

Add to Cart



30-day refund or replacement
Money back guarantee




Secure Payment
Multiple payment options


Refer & earn 10% off any order 🎁




UART Transmitter

 


UART Receiver

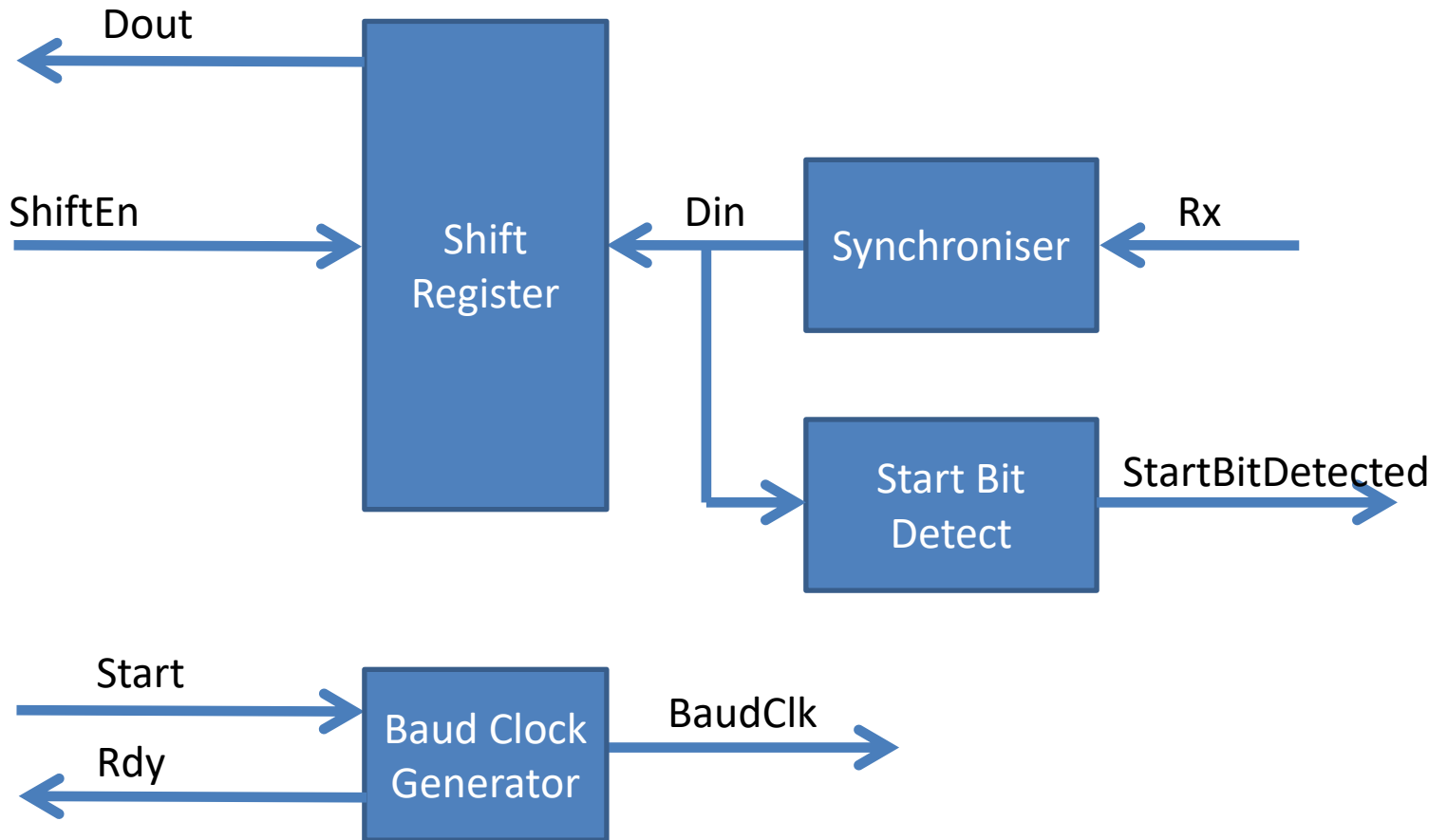


RS232 Protocol

 

RS232 Protocol

 

RS232 Protocol

 

RS232 Protocol

Start Bit	Data Bits	Parity Bit	Stop Bit(s)
-----------	-----------	------------	-------------

Start Bit = Supports 1 start bit. Logic 0.

Data Bits = Supports 5 to 9 data bits

Parity Bit = Optional (Even or Odd Parity)

Stop Bits = Supports 1, 1.5 or 2 stop bits. Logic 1.

RS232 Protocol

Start Bit	Data Bits	Parity Bit	Stop Bit(s)
-----------	-----------	------------	-------------

Start Bit = Supports 1 start bit. Logic 0.

Data Bits = Supports 5 to 9 data bits

Parity Bit = Optional (Even or Odd Parity)

Stop Bits = Supports 1, 1.5 or 2 stop bits. Logic 1.

RS232 Protocol

Start Bit	Data Bits	Parity Bit	Stop Bit(s)
-----------	-----------	------------	-------------


Start Bit = Supports 1 start bit. Logic 0.

Data Bits = Supports 5 to 9 data bits


Parity Bit = Optional (Even or Odd Parity)

Stop Bits = Supports 1, 1.5 or 2 stop bits. Logic 1.

Transmit Data Byte 0x69

 

Transmit Data Byte 0x69

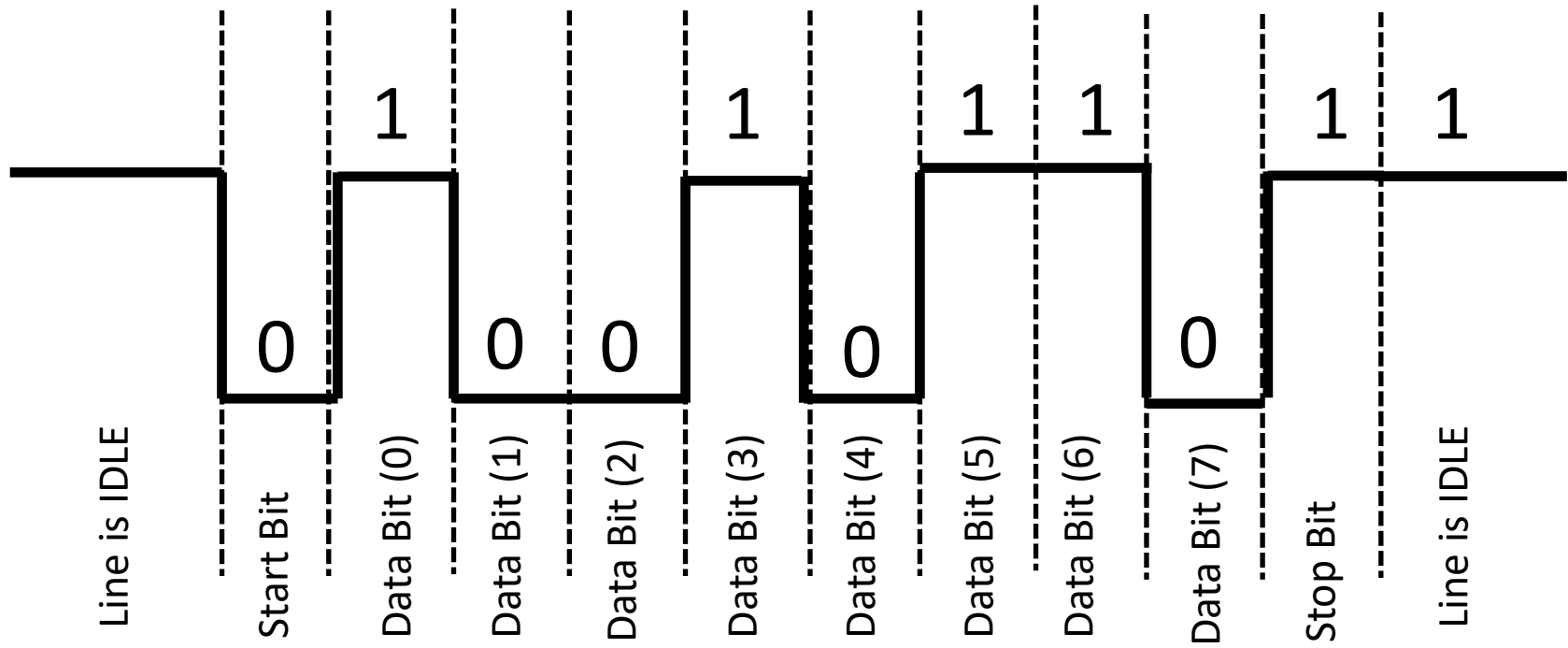

Buad Rates

- 115200
- 57600
- 38400
- 19200
- 14400
- 9600

Buad Rates

- 115200 (Bit period = $1/115200 = 8.7\mu\text{s}$)
- 57600
- 38400
- 19200
- 14400
- 9600